

## Module - 1

- \* Current :- Flow of charge.
- \* Intensity of current :- Rate of flow of charge (strength)  
 $I = Q/t$ ;  $A = C/s$ ; unit: Ampere (A)
- \* The flow of 1C of charge in 1s is known as 1A.  
( $1A = 1C/1s$ )
- \* Electric potential :- Capacity of charge to do work.  
 $V = W/Q$ ;  $V = J/C$ ; unit: volt (V).
- \* When 1C of charge posses an energy of 1J, then the body has an electric potential of 1V.
- \* Potential difference :- Force which causes the electric current flow in a closed circuit.  
 $V_{ba} = V_b - V_a$ .
- \* Electromotive Force :- Pressure or force which causes an electric current to flow.  
unit: volt (V).
- \* Power :- The rate of doing work.  
 $P = VI$ ;  $P = V^2/R$ ;  $P = I^2R$ ; unit: watts or hp or kilowatts.  
1 horse power = 746 watts.
- \* Energy :- Capacity to do work.  
unit: J or kwh  
kwh = power in kw  $\times$  time in hr.

- Resistance is property of a substance to oppose the flow of electric current.
- unit is ohm ( $\Omega$ )
- when 1A current flowing through a conductor produces a heat at the rate of 1J/s, then a conductor is said to have 1 $\Omega$  resistance.

(Q1) Consider a resistance which is connected to a 12V supply having resistance 2 $\Omega$ , then what will be the charge produced in Coulombs for 10 sec?

Ans)  $V = 12V$ ;  $R = 2\Omega$

$$V = IR$$

$$12 = I \times 2$$

$$I = 6A$$

$$Q = ?; t = 10s; I = 6A$$

$$Q = IT$$

$$= 10 \times 6$$

$$= 60C$$


          

\* Ohm's law: At a constant temperature, the ratio of potential difference ( $V$ ) between any two points on a conductor to the current ( $I$ ) flowing between them, is constant.

$$\frac{V}{I} = \text{constant}$$

$$= R$$

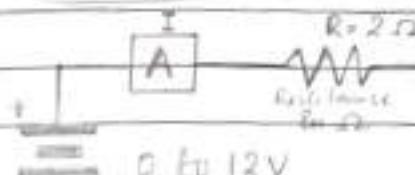
## \* Volt - Ampere Characteristics (VI characteristics)



$V$	$R$	$I = V/R$
0	2	0
4	2	2
10	2	5
12	2	6.

$$\begin{aligned} \text{Slope} &= y/x \\ &= 1/V \\ &= 1/R \end{aligned}$$

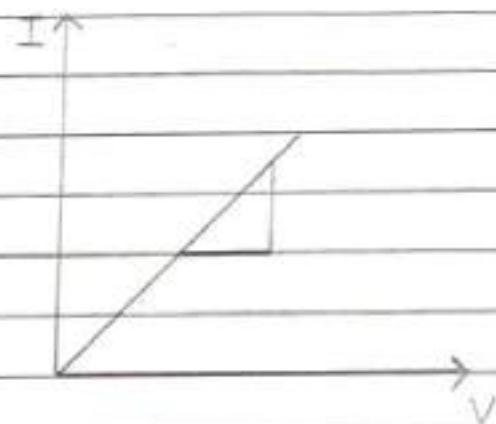- Conductance ( $1/R$ )
- VI characteristics
- $\Omega R$ : Shows how much current a resistor allows.




## \* Linear Resistance

- Resistance doesn't vary with the flow of current through it.
- The current through it, will always be proportional to the voltage applied across it.

- VI characteristic is linear

- eg: Rheostat, potentiometer

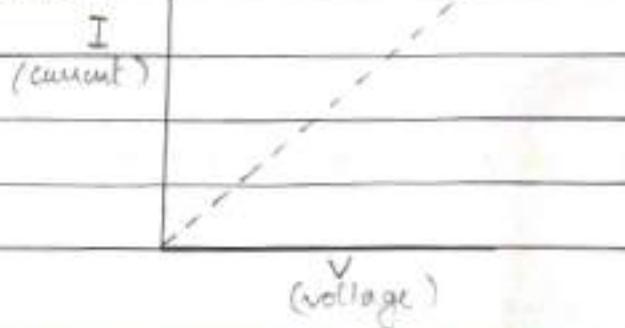

- \* Non linear Resistance
- \* Resistance varies with the flow of current through it.
- \* Non linear VI characteristics.

e.g. Tungsten filament, Thermistor.

### \* Laws of Resistance

- \* The resistance offered by a conductor depends on the following factors:

- varies directly as its length,  $l$
- varies inversely as cross sectional area,  $A$
- depends on the nature of material
- also depends on the temperature  $\theta$  of the conductor.

- \* For const temp

$$R \propto \frac{l}{A}$$

$$R = \rho \frac{l}{A}$$

- $\rho$  is the specific resistance or resistivity.
- when  $l = 1\text{m}$ ,  $A = 1\text{m}^2$  then  $R = \rho$

\*  $\rho$  is the resistance between the opposite faces of 1m cube of that material.

- \* Conductor of conductivity

- Reciprocal of resistance (conductance)
- Conductance is defined as the potential for a substance to conduct electricity.

$$G_1 = \frac{1}{R}$$

$$= \frac{A}{\rho l}$$

$$= \frac{\sigma A}{l}$$

- unit of  $\sigma$ : ohm<sup>-1</sup>m<sup>-1</sup> or mho/m
- unit of  $G_1$ : mho or  $\text{S}$

### \* Inductor

- Inductance ( $L$ ): property to oppose the change in flux.
  - Conductor is twisted like a coil - basic inductor
  - unit: Henry (H).
- \* Current through an inductor
- According to Faraday's Law

$$V = L \frac{di}{dt}$$

$$di = \frac{V}{L} dt$$

$$\int di = \int_{t_1}^{t_2} \frac{V}{L} dt$$

$$i(t) - i(0) = \frac{1}{L} \int_0^t v dt$$

$$i(t) = \frac{1}{L} \int_0^t v dt.$$

\*  $i(0)$  is the initial current.

\* Current through the inductor dependant upon the integral of the voltage of its terminals and initial current in the coil.

### \* Energy Stored in an Inductor

Power,

$$P = vi \quad (\text{Inductor} \rightarrow \text{instantaneous power})$$

$$= L \frac{di}{dt} \cdot i \quad v = L \frac{di}{dt} \quad (\text{Faraday's law})$$

Energy,

$$E = \int_0^t P dt$$

$$= \int_0^t L \frac{di}{dt} \cdot i \cdot dt$$

$$= L \int_0^t i \cdot di$$

changing limits,

$$\text{At } t=0; i=0$$

$t=t$ ;  $i=I$ , DC current

$$E = L \int_0^t P di$$

$$= \frac{1}{2} L [i^2]_0^t$$

$$= \frac{1}{2} L (I^2 - 0)$$

$$E = \frac{1}{2} L I^2$$

- If current through the inductor is constant, induced voltage = 0.  
(Inductor acts as a short-circuit)

- Small change in zero time will give infinite voltage. This is practically impossible. So impulsive change in inductor current is not possible.
- A pure inductor cannot dissipate energy. Hence it is known as non-dissipative passive element.

(Q) Show that,  $P = I^2 R = V^2/R$  using Ohm's law.

Ans)  $V = IR \quad \text{--- (1)}$

$P = VI \quad \text{--- (2)}$

From (1) Sub (1) in (2)

$$P = (IR)I$$

$$= I^2 R \quad \text{--- (3)}$$

Multiplying or dividing the 3<sup>rd</sup> eqn by  $R$

$$P = I^2 R \times \frac{R}{R}$$

$$= \frac{(IR)^2}{R} = \frac{V^2}{R}$$

Hence proved

Q2) Calculate the resistance of 100m length of a wire having a uniform cross-sectional area of  $0.1 \text{ mm}^2$ . If the wire is made of manganin having a resistivity of  $50 \times 10^{-8} \Omega\text{m}$ . If the wire is drawn out to three times its original length. By how many times would you expect the resistance to be increased?

$$\text{Ans}) \quad l_1 = 100\text{m}$$

$$A_1 = 0.1 \text{ mm}^2 \\ = 1 \times 10^{-7} \text{ m}^2$$

$$\rho = 50 \times 10^{-8} \Omega\text{m}$$

$$R_1 = \frac{\rho l_1}{A_1} \quad - \textcircled{1}$$

$$= \frac{50 \times 10^{-8} \times 100}{1 \times 10^{-7}}$$

$$= 50 \times 10^{-8} \times 10^9$$

$$= \underline{\underline{500 \Omega}}$$

$$R_2 = \frac{\rho l_2}{A_2} \quad - \textcircled{2}$$

$\therefore$  as the length is increased by 3 times, area decreases by 3 times.

$$l_2 = 3l_1 \quad - \textcircled{3}$$

$$A_2 = \frac{A_1}{3} \quad - \textcircled{4}$$

$\therefore$  Sub  $\textcircled{3}$  &  $\textcircled{4}$  in  $\textcircled{2}$

$$R_2 = \frac{\rho \times 3l_1}{A_1} = 9 \frac{\rho l_1}{A_1}$$

According to eqn ①

$$R_2 = 9R_1$$

.....

### \* Capacitor (C)

- Capacitors consist of 2 conducting surfaces separated by a layer of insulating medium called dielectric.
- Capacitor stores electrical energy in dielectric.

### \* Capacitance

- Ability to store electricity
- unit - Farad, F

$$C = \frac{Q}{V}$$

- One farad is amount of capacitance when 1C charge stored with 1V across the plate.

### \* Voltage Across Capacitor

$$C = \frac{Q}{V} \text{ or } C = \frac{I}{V}$$

$$I = C \frac{dV}{dt} \quad \left\{ I = \frac{dq}{dt} \right\}$$

$$dV = \frac{1}{C} dI$$

$$t \quad C \quad t$$

$$\int dV = \frac{1}{C} \int pdI$$

$$V(t) - V(0) = \frac{1}{C} \int_0^t Q dt$$

{ \$V(0)\$ is const.  
 - and 0

$$V(t) = \frac{1}{C} \int_0^t Q dt + V(0)$$

- Energy stored in Capacitor

$$P = VI = \frac{Q}{C} I = \frac{VC}{C} \frac{dV}{dt} = C \frac{dV}{dt}$$

Energy,  $W = \int pdt$

$$= \int_0^t C \frac{dV}{dt} \cdot dt$$

$$= C \int_0^t V dV = C \left[ \frac{V^2}{2} \right]_0^t$$

$$W = \frac{1}{2} CV^2$$

- Current in the capacitor is zero when voltage is constant.

- In a fixed capacitor, voltage cannot change abruptly


Capacitor can store finite amount of energy even if the current through it is zero.

Pure capacitor never dissipate energy - non-

dissipative passive element.


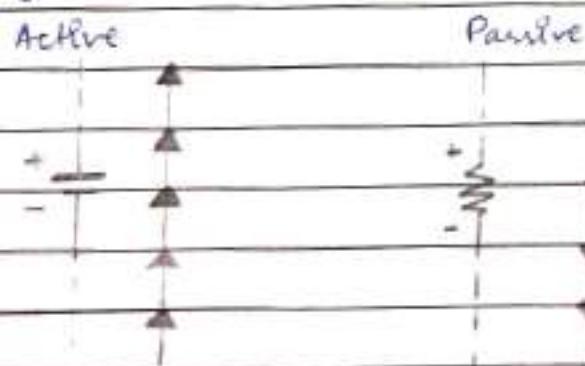
### Active and passive sign convention

- Active sign convention is used for the devices which deliver energy to the circuit  
e.g. battery
- Passive sign convention is commonly used for resistors.





### Energy Sources



- Ideal voltage and ideal current source

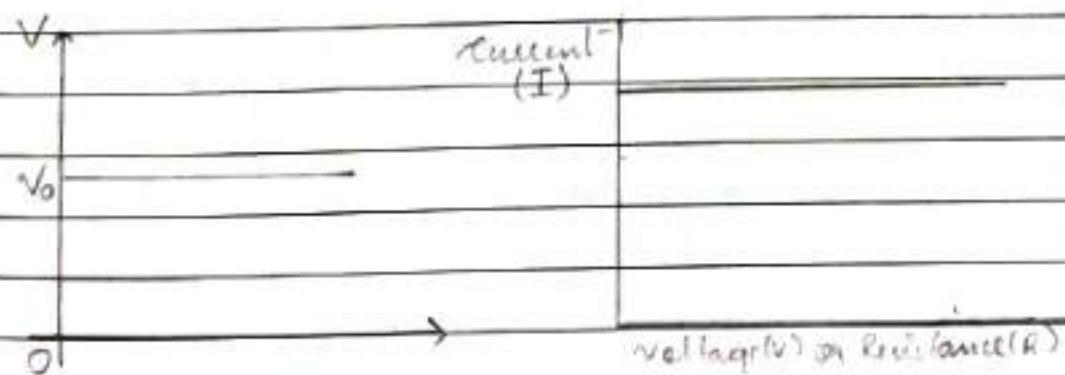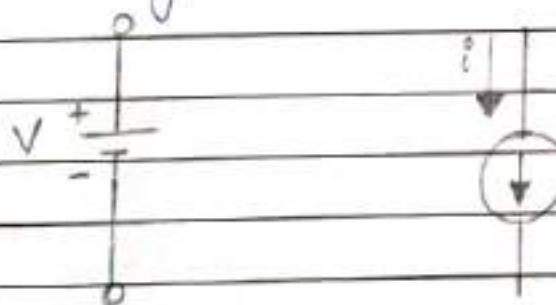

## \* Practical Energy Sources

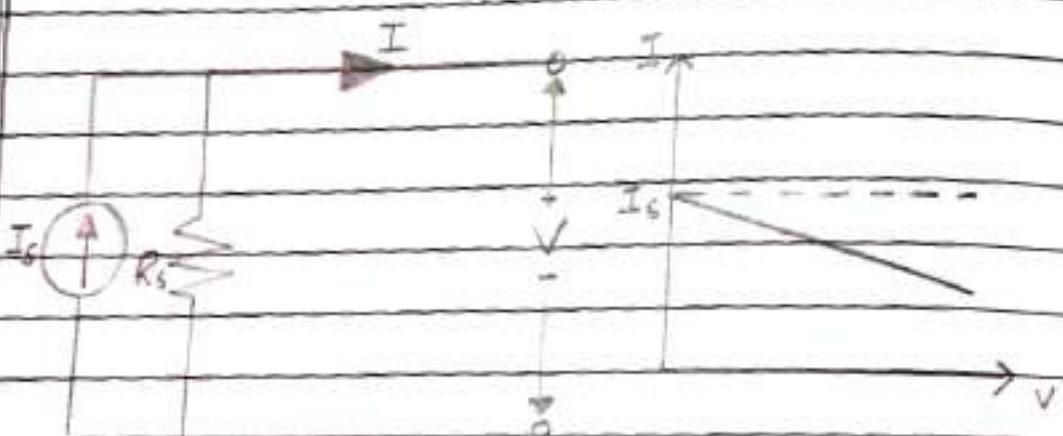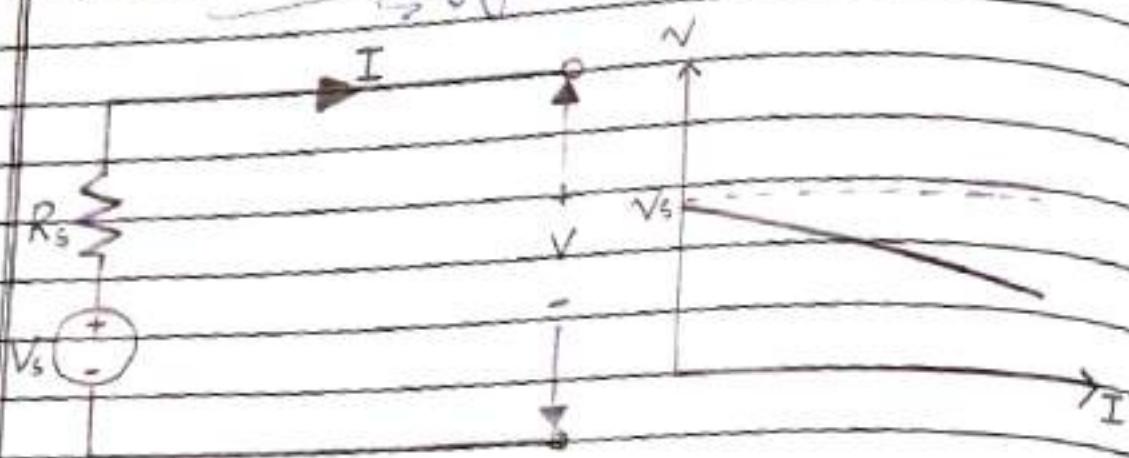

## \* Dependent Sources

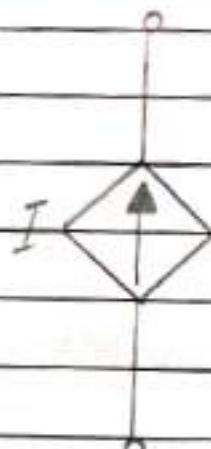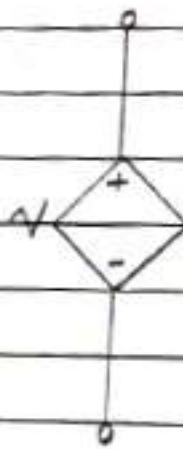

(a) Dependent voltage source

(b) Dependent current source

- Voltage controlled by voltage source.
- Voltage controlled by current source.

- Current controlled by voltage source.
- Current controlled by current source.


### \* Series Circuit

$$V = IR_s$$

But  $V = V_1 + V_2 + V_3$

$$\therefore TR_s = IR_1 + IR_2 + IR_3$$
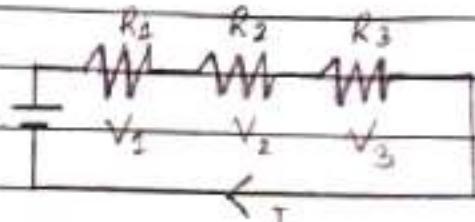
$$\text{e.c } IR_s = I(R_1 + R_2 + R_3)$$



$$R_s = R_1 + R_2 + R_3$$

### \* Voltage Divider Rule

$$R = R_1 + R_2 \quad \text{--- (1)}$$

$$I = \frac{V}{R} \quad \text{--- (2)}$$

$$V_1 = IR_1$$

$$V_1 = \frac{V R_1}{R} \quad \text{from (2)}$$

$$\frac{V_1}{R} = \frac{R_1}{R} V$$

$$= \frac{R_1}{R_1 + R_2} V \quad \text{from (1)}$$

### \* Parallel Circuit

$$\text{Total current} = I_1 + I_2 + I_3$$

$$I = \frac{V}{R}$$

$$\frac{V}{R_p} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$\left\{ V_1 = V_2 = V_3 = V \right\}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$G_p = \frac{1}{R_p}$$

$$\therefore G_p = G_1 + G_2 + G_3$$




### \* Two Resistors in Parallel

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

### \* Current division Rule

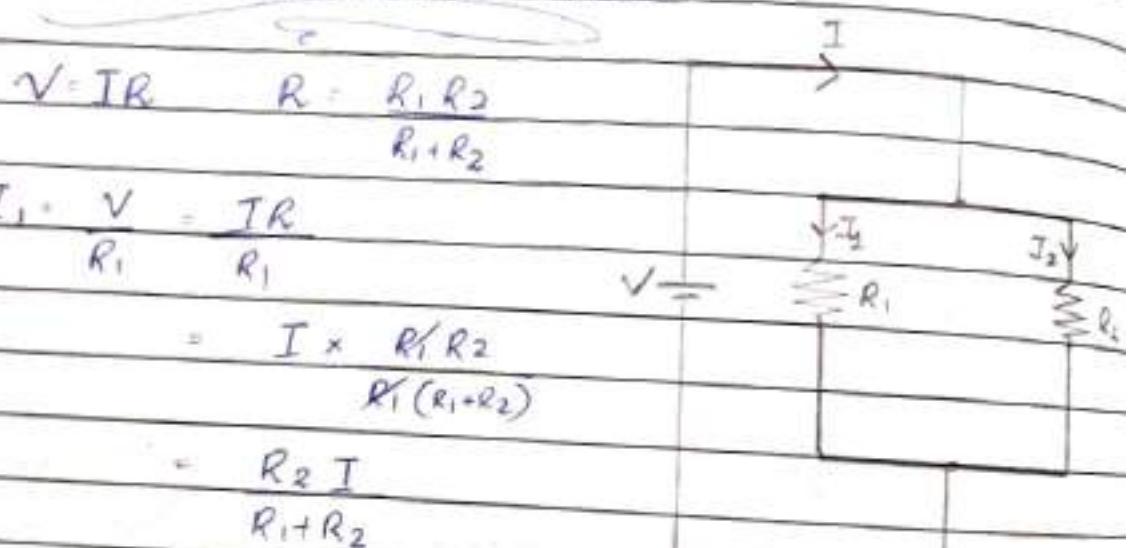

$$I_1 = \frac{V}{R_1}$$


$$= I \times \frac{R_1}{R_1 + R_2}$$

$$= \frac{R_2 I}{R_1 + R_2}$$

$$I_2 = \frac{V}{R_2}$$

$$= \frac{R_1 I}{R_1 + R_2}$$

$$\therefore I_x = \frac{V}{R_x}$$

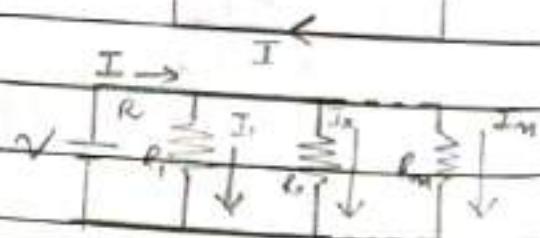

$$I_x = \frac{I}{R_x}$$

$$\{ V = IR \}$$

51) The resistivity of a ferric-chromium-aluminum alloy is  $51 \times 10^{-8} \Omega \text{m}$ . A sheet of the material is 8 cm long, 6 cm wide and 0.014 cm thick. Determine resistance between

- a) opposite ends and b) opposite sides.

$$\text{Ans}(a) l = 15 \text{ cm}$$

$$\frac{15}{100} = 0.15 \text{ m}$$

$$A = \frac{6}{100} \times \frac{0.014}{100} = 6 \times 10^{-7} \text{ m}^2$$

$$R = \rho \frac{l}{A}$$

$$= 51 \times 10^{-8} \times 0.15$$

$$\frac{6}{100} \times \frac{0.014}{100}$$

$$= 51 \times 10^{-8} \times \frac{15 \times 10000}{6 \times 100 \times 0.014}$$

$$= \frac{51 \times 15 \times 10^{-8} \times 10^3 \times 10^2}{26 \times 14}$$

$$= \underline{\underline{9.1 \times 10^{-3} \Omega}}$$



b)  $l =$

$$A = \frac{15 \times 6}{10000}$$

$$= 15 \times 6 \times 10^{-4} \text{ m}^2$$


$$R = \rho \frac{l}{A}$$

$$= 51 \times 10^{-8} \times \frac{0.014}{15 \times 6 \times 10^{-4}}$$

$$= 51 \times 10^{-8} \times \frac{14 \times 10^{-4}}{15 \times 6 \times 1000}$$

$$= \frac{51 \times 14 \times 10^{-8} \times 10^{-4}}{15 \times 6 \times 1000} = \underline{\underline{7.9 \times 10^{-9} \Omega}} = \underline{\underline{79.3 \times 10^{-10} \Omega}}$$

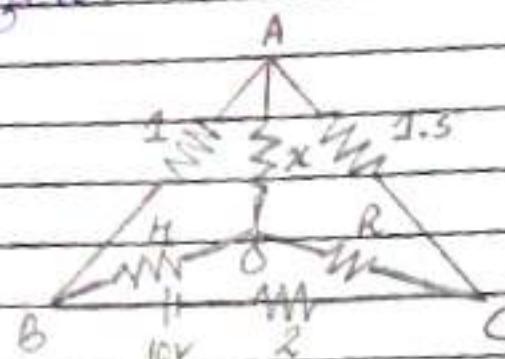(Q2) Determine the value of  $R$  and current through it, if current through branch  $AC$  is  $2\text{A}$ .



Ans)

$$R_1 = 1.5\Omega$$


$$R_2 = 1.5\Omega$$

$$R_3 = 4\Omega$$

$$R_H = R_{\text{Req}} = ?$$

$$V = 10\text{V}$$

$$R = 2\Omega$$

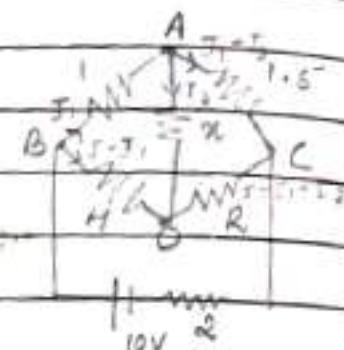

$$T_3 = 0$$

$$I - I_1 = 5 - I_1$$

$$R_1 = R_3$$

$$R_2 = R_4$$

$$\frac{1}{1.5} = \frac{H}{R_H}$$

$$R_H = H \times 1.5$$

$$= 6\Omega$$

$$R_{BC} = ?$$

$$\frac{1}{R_{BC}} = \frac{1}{25} + \frac{1}{10}$$

$$= \frac{10 + 2.5}{25}$$

$$R_{BC} = 25 = 250 - 25\Omega$$

$$\frac{12.5}{12.5} \quad \frac{12.5}{12.5}$$


$$\text{total resistance} = 2 + 2 = 4 \Omega$$

$$\text{total current} = \frac{V}{R_{\text{total}}}$$

$$I_0 = \frac{0.5A}{4} =$$

$$I_R = \frac{0.5}{2} \times \frac{0.5}{2} = \underline{\underline{0.5A}}$$

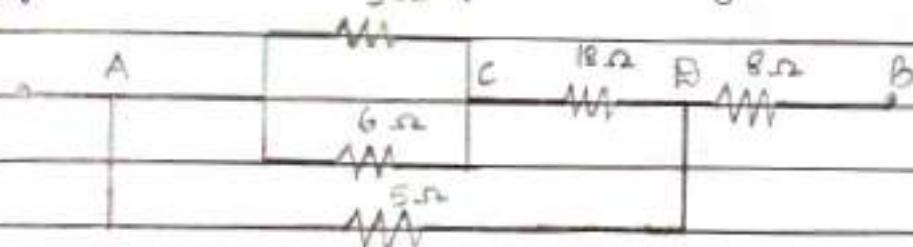- Q3) Calculate the effective resistance of the following combination of resistances and the voltage drop across each resistance when a p.d of 60V is applied between points A & B.




$$R_1 = 3 \Omega$$

$$R_2 = 6 \Omega$$

$$R_3 = 18 \Omega$$

$$R_4 = 5 \Omega$$

$$R_5 = 8 \Omega$$

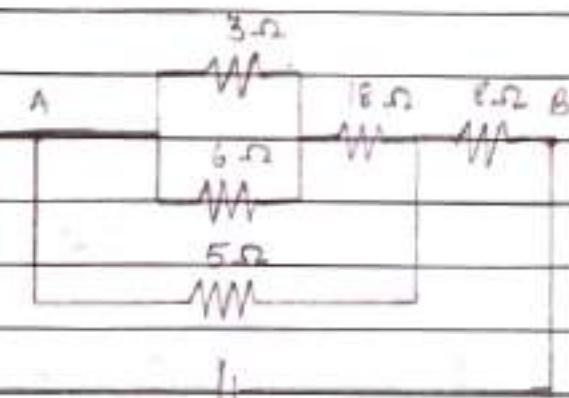

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{3} + \frac{1}{6}$$

$$= \frac{2+1}{6} = \frac{3}{6} = \frac{1}{2}$$

$$R_p = 2 \Omega$$

$$R_s = R_p + R_B$$

$$= 2 + 18 = 20 \Omega$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{20} + \frac{1}{5}$$

$$= \frac{1}{20} + \frac{4}{20}$$

$$= \frac{5}{20}$$

$$R_p = 4\ \Omega$$

$$R_s = R_p + R_3$$

$$= 4 + 8$$

$$= \underline{\underline{12\ \Omega}}$$

total effective resistance =  $\underline{\underline{12\ \Omega}}$

Voltage across AB is 60V

$$V = IR$$

$$60V = I \times 12$$

$$I = \frac{60}{12} = \underline{\underline{5A}}$$

current across  $5\ \Omega$  resistor

$$I_x = \frac{I \times R_2}{(R_1 + R_2)}$$

$$= \frac{5 \times 20}{25}$$

$$= \underline{\underline{4A}}$$

Current across  $20\ \Omega$  resistors  
( $R_1, R_2, R_3$ )

$$I_y = \frac{5 \times 5}{25} \quad \left\{ \begin{array}{l} I_x = I_y R \\ R_x \end{array} \right.$$

1A

i) voltage across across 3 ohm 3 ohm resistors

$$V = IR$$

$$V = 1A \times 2\Omega \quad (R_p = 2\Omega)$$

2V

ii) voltage across 5 ohm resistor

$$V = IR$$

$$V = 4 \times 5$$

$$= 20V$$

iii) voltage across 18 ohm resistor

$$V = IR$$

$$= 1 \times 18$$

$$= 18V$$

iv) voltage across 8 ohm resistor


$$V = IR$$

$$= 5 \times 8$$

$$= 40V$$

$$\left\{ \begin{array}{l} I = A + I = 5A \\ I = 5A \end{array} \right.$$

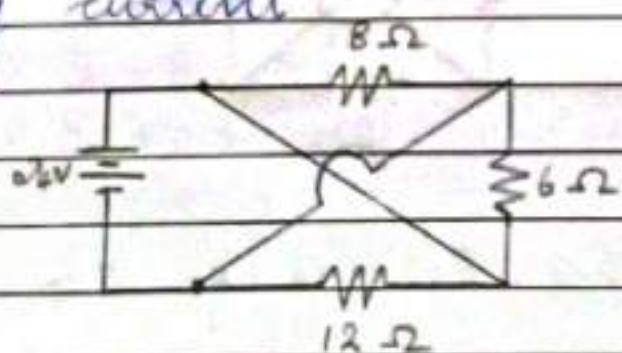Q4) Compute total circuit resistance and battery current



A)  $R_1 = 12\Omega, R_2 = 6\Omega, R_3 = 8\Omega, V = 24V$ .


$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{12} + \frac{1}{6} + \frac{1}{8}$$

$$= \frac{2+4+3}{24}$$

$$= \frac{9}{24}$$

$$R_p : 24 = \frac{8}{9}$$

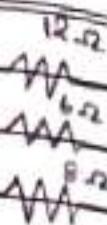

24V

$$V = IR$$


$$24 = I \times \frac{8}{3}$$

~~$$24 = I \times \frac{8}{3}$$~~

$$I = 24 \times \frac{3}{8}$$

~~$$I = 9A$$~~

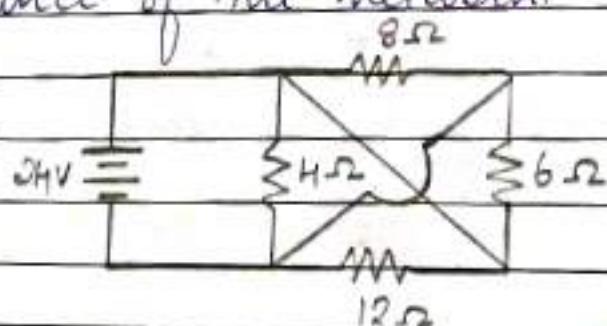
Q5) Calculate battery current and equivalent resistance of the network.



Ans)  $R_1 = 8\Omega, R_2 = 6\Omega, R_3 = 12\Omega, R_4 = 4\Omega, V = 24V$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$
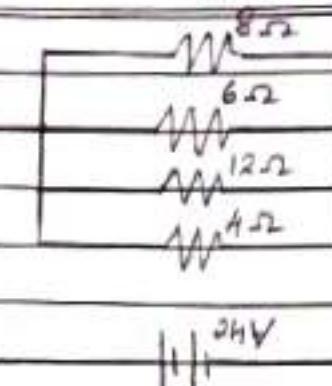
$$\begin{aligned}
 & I = \frac{I}{R_p} + \frac{I}{8} + \frac{I}{6} + \frac{I}{12} + \frac{I}{H} \\
 & = \frac{8+H+2+6}{2H} I \\
 & = \frac{15}{2H} I
 \end{aligned}$$



$$R_p = \frac{2H^2}{15} + \frac{8}{5} \Omega$$


$$V = IR$$

$$2H = I \times \frac{8}{5}$$

$$I = \frac{2H \times \frac{5}{8}}{=}$$

$$= 15A$$

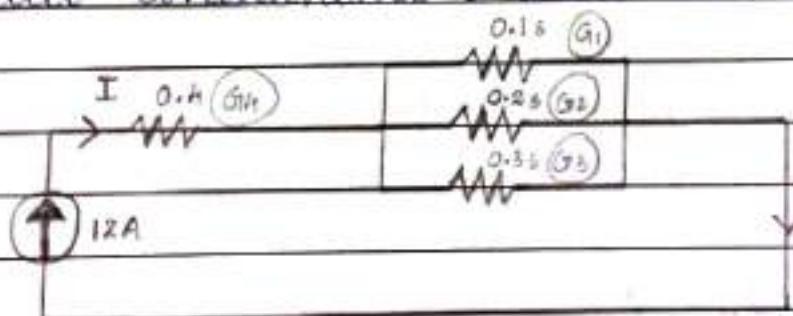Qb) Calculate the values of different currents for the circuit shown in the figure, what is the total circuit conductance? and resistance?



$$\text{Ans}) R = \frac{1}{G_1}$$

$$\begin{aligned}
 G_p &= G_1 + G_2 + G_3 \\
 &= 0.1 + 0.2 + 0.3 \\
 &= 0.6S
 \end{aligned}$$

$$\begin{aligned}
 I &= \frac{1}{G_1} + \frac{1}{G_p} + \frac{1}{G_3} \\
 G_1 & G_p & G_3
 \end{aligned}$$

$$\frac{I}{G_1} + \frac{I}{G_2}$$

$$= \frac{4+6}{2H}$$

$$\frac{I}{G_3} = \frac{10}{2H}$$

$$G_3 = \frac{2H}{10} = \underline{\underline{2.45}}$$

$$R = \frac{10^5}{\sqrt{2H}} = \frac{5}{12} \Omega$$

$$I_3 = I \times \frac{G_3}{G}$$

$$I_1 = I \times \frac{G_1}{G}$$

$$= 12 \times \frac{0.1}{0.6} \times 10^5$$

$$= 12 \times \frac{0.1}{0.6}$$

$$= \frac{12}{6} = \underline{\underline{2A}}$$

$$I_2 = I \times \frac{G_2}{G}$$

$$= 12 \times \frac{0.2}{0.6}$$

$$= \frac{12}{6} \times \frac{2}{6}$$

$$= \underline{\underline{4A}}$$


$$I_1 = I \times \frac{G_1}{G}$$

$$\begin{aligned} &= 12 \times 0.3 \\ &\quad 0.6 \end{aligned}$$

$$\begin{aligned} &= 12 \times 0.3 \\ &\quad 6 \end{aligned}$$


$$\begin{aligned} &= 6 \\ &= \underline{\underline{6}} \end{aligned}$$

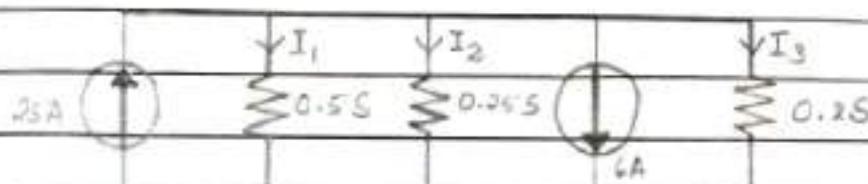Q1) Compute the values of 3 branch currents for the circuit shown. What is the P.d b/w points A & B.



Ans)  $I = 25 - 6$   
 $= \underline{\underline{19}}$
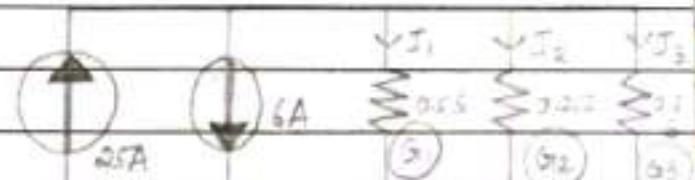
$$I_1 = \frac{I}{G_1} = \frac{19}{0.5} = 38$$



$G_1 = ?$

$$\begin{aligned} G_{\text{p}} &= G_1 + G_2 + G_3 \\ &= 0.5 + 0.25 + 0.2 \\ &= \underline{\underline{0.955}} \end{aligned}$$

$$\begin{array}{r} 19 \\ \times 0.5 \\ \hline 95 \\ 95 \\ \hline 95 \end{array}$$

$$I_1 = 19 \times \frac{0.5}{0.955}$$

$$= \frac{19 \times 50}{95.5}$$

$$= \underline{\underline{10}}$$

$$I_2 = \frac{I}{G_2}$$

$$= 19 \times \frac{0.25}{0.95}$$

$$= 19 \times \frac{25}{95} \Omega$$

$$= \underline{\underline{5\Omega}}$$

$$I_A = I \times \frac{G_3}{G_1}$$

$$= 19 \times \frac{0.2}{0.95}$$

$$= 19 \times \frac{20}{95} \Omega$$

$$= \underline{\underline{4\Omega}}$$

Q8) Find the equivalent resistance of the circuit shown.


(i) B/w A & B

(ii) B/w C & D

(iii) B/w E & F

(iv) B/w A & F

(v) B/w A & C.

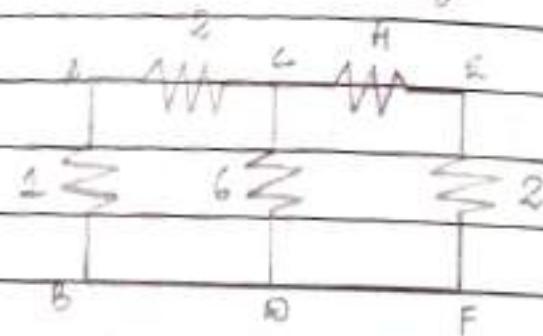


The number represents resistance in  $\Omega$ .

Ans) (i) B/w A & B.

$$R_S = R_1 + R_2$$

$$= 4 + 2$$

$$= \underline{\underline{6\Omega}}$$

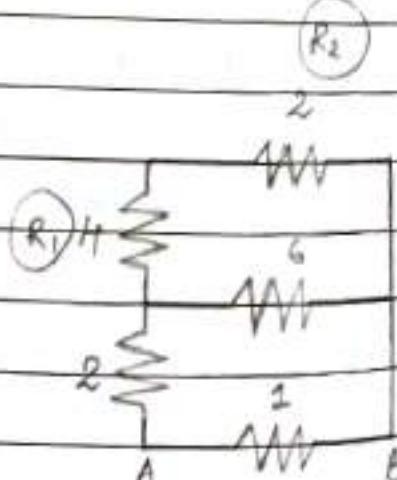

$$\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_4}$$

$$= \frac{2}{6} + \frac{2}{6}$$

$$= \frac{2}{6}$$

$$R_p = \underline{\underline{3\Omega}}$$

$$R_s = R_5 + R_6$$

$$= 2 + 3$$

$$= 5\Omega$$

$$\frac{1}{R_p} = \frac{1}{R_s} + \frac{1}{2}$$

$$= \frac{1}{5} + \frac{1}{2}$$

$$= \frac{6}{5}$$

$$R_p = \underline{\underline{5/6\Omega}}$$

iii) B/w C/gD

$$R_{s1} = R_1 + R_2$$

$$= 4 + 2$$

$$= \underline{\underline{6\Omega}}$$

$$R_{s2} = R_3 + R_4$$

$$= 2 + 1$$

$$= \underline{\underline{3\Omega}}$$



$$\frac{1}{R_p} = \frac{1}{R_{s1}} + \frac{1}{R_s} + \frac{1}{R_{s2}}$$

$$= \frac{1}{6} + \frac{1}{6} + \frac{1}{3}$$

$$= \frac{2}{6} + \frac{1}{3}$$

$$= \frac{4}{6}$$
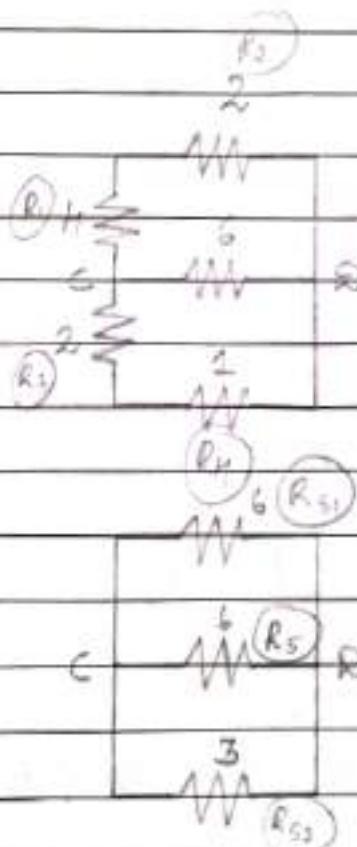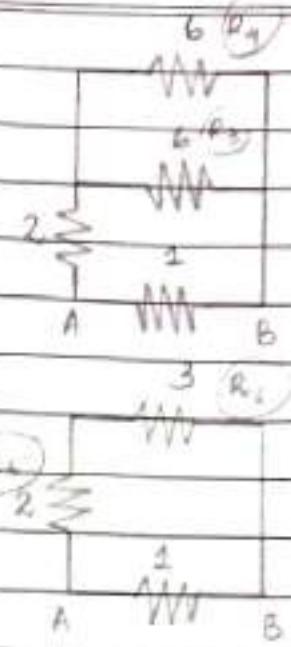
$$R_p = \frac{6}{4} = \underline{\underline{3\Omega}}$$



(iii) B/w E f F

$$R_S = R_1 + R_2$$

$$= 2 + 1$$

$$= \underline{3 \Omega}$$



$$\frac{1}{R_P} = \frac{1}{R_S} + \frac{1}{R_H}$$

$$= \frac{1}{3} + \frac{1}{6}$$

$$= \frac{2+1}{6}$$

$$= \frac{3}{6}$$


$$= \underline{\underline{3}}$$

$$R_P = \underline{\underline{2 \Omega}}$$

$$R_{S1} = R_P + R_H$$

$$= 2 + H$$

$$= \underline{\underline{6 \Omega}}$$

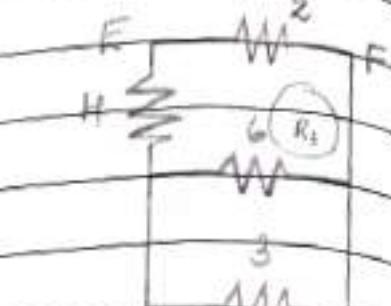

$$\frac{1}{R_{P1}} = \frac{1}{R_{S1}} + \frac{1}{R_S}$$

$$= \frac{1}{6} + \frac{1}{2}$$

$$= \frac{1}{6} + \frac{3}{2}$$

$$= \frac{4}{6}$$

$$= \underline{\underline{\frac{2}{3}}}$$

$$R_{P1} = \frac{6}{\frac{2}{3}} \Omega = \underline{\underline{3 \Omega}}$$


(iv) B/w A f F

$$R_S = R_1 + R_2$$

$$= H + 2$$

$$= \underline{\underline{6 \Omega}}$$

$$=$$

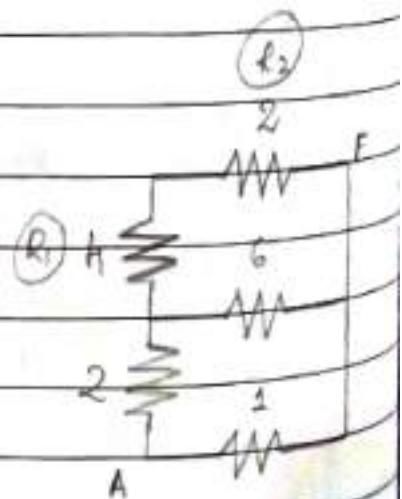

$$\frac{1}{R_p} = \frac{1}{R_6} + \frac{1}{R_3}$$

$$= \frac{1}{6} + \frac{1}{1}$$

$$= \frac{2}{6} = \frac{1}{3}$$

$$R_p = \underline{\underline{3\Omega}}$$

$$R_{S1} = R_p + R_H$$

$$= 3 + 2$$

$$= \underline{\underline{5\Omega}}$$



$$\frac{1}{R_{P1}} = \frac{1}{R_{S1}} + \frac{1}{R_5}$$

$$= \frac{1}{5} + \frac{1}{1}$$

$$= \underline{\underline{\frac{6}{5}}}$$

$$R_{P1} = \underline{\underline{5\Omega}}$$

$$6 =$$

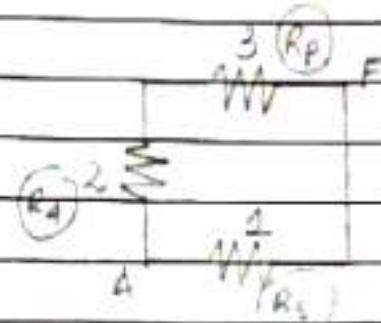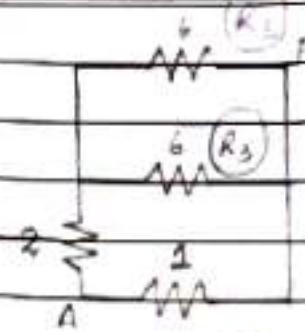


(v) B/w A &amp; C

$$R = R_1 + R_2$$

$$= 4 + 2$$

$$= \underline{\underline{6\Omega}}$$

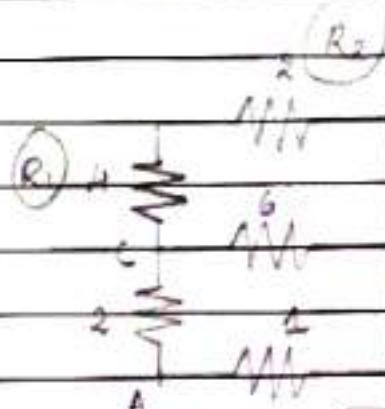


$$\frac{1}{R_p} = \frac{1}{R_5} + \frac{1}{R_3}$$

$$= \frac{1}{6} + \frac{1}{6}$$

$$= \underline{\underline{\frac{2}{6}}}$$

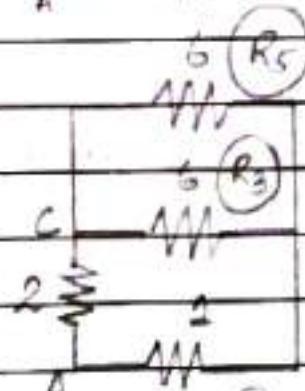
$$R_p = \underline{\underline{3\Omega}}$$



$$R_{S1} = R_p + R_H$$

$$= 3 + 1$$

$$= \underline{\underline{4\Omega}}$$

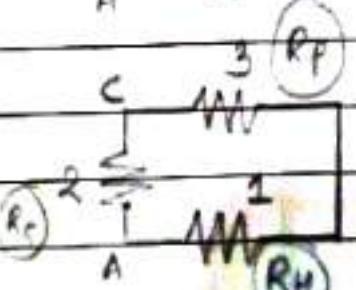

$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{H} + \frac{1}{2}$$

$$= \frac{3}{H}$$

$$R_P = \frac{H \cdot S}{3}$$

### \* Delta - Star Transformation




$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}}$$

### \* Star - Delta Transformation

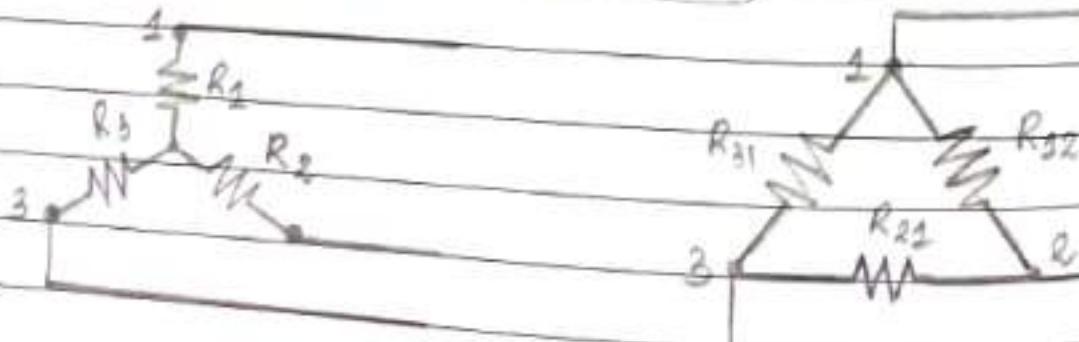

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$



$$= \frac{R_2 + R_2 R_3 + R_3}{R_1}$$

$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$= \frac{R_1 + R_3 + R_2 R_1}{R_2}$$

Kirchhoff's Point law or Current law (KCL)

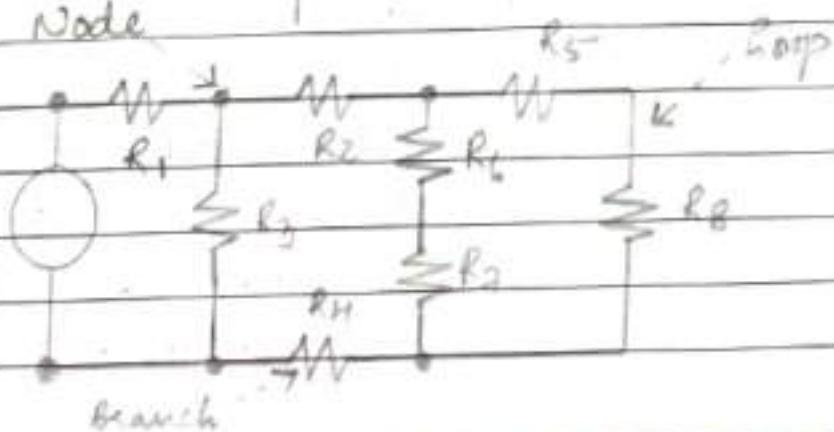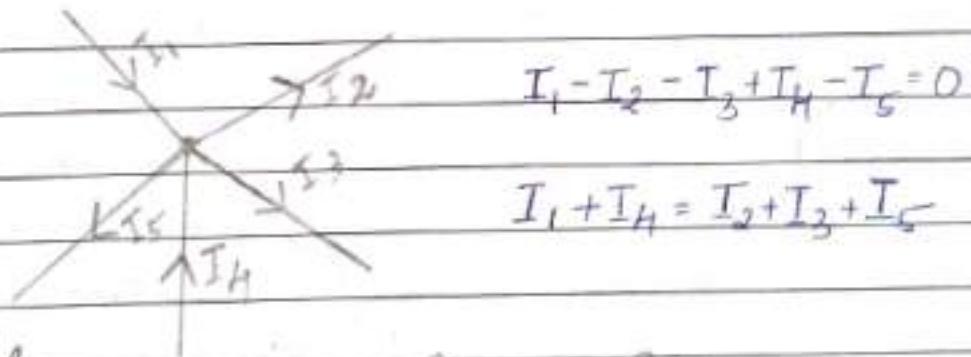
- In any electrical network, the algebraic sum of the currents meeting at a point (or junction) is zero.
- Incoming currents - Outgoing currents.



# Kirchhoff's Mesh Law or Voltage Law (KVL)


- The algebraic sum of the products of currents and resistances in each of the conductors in any closed path (or mesh) in a network plus the algebraic sum of the e.m.f.s in that path is zero.

- $\Sigma IR + \Sigma \text{e.m.f} = 0$

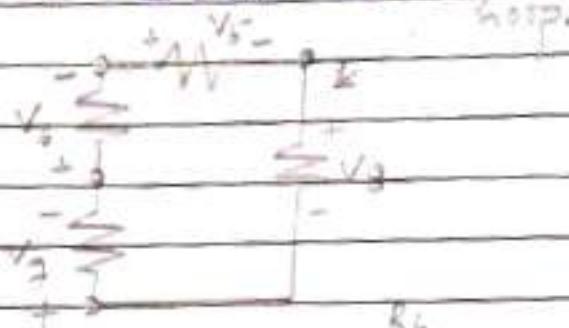

$$V_5 + V_6 + V_2 + V_3 = 0$$

(Q1)

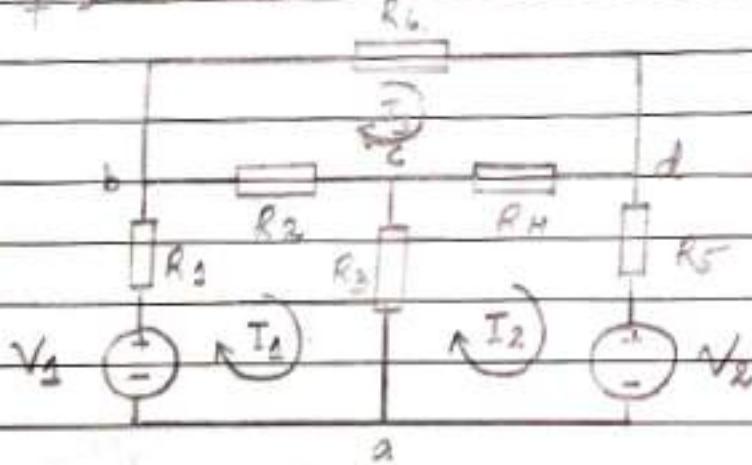

Ans)

Consider loop/mesh abca.

$$-I_1 R_1 - (I_1 - I_2) \cdot R_2 - (I_1 - I_2) \cdot R_3 + V_1 = 0$$

$$-I_1 R_1 - I_1 R_2 + I_2 R_2 - I_1 R_3 + R_3 I_2 + V_1 = 0$$

$$I_1 (R_1 + R_2 + R_3) - I_2 R_3 - I_3 R_2 = V_1$$

-①

Consider acda

$$\begin{aligned} -(I_2 - I_1)R_3 - (I_2 - I_3)(R_4) - I_2 R_5 - V_2 &= 0 \\ I_1 R_3 - I_2 (R_3 + R_H + R_5) + R_H I_3 &= V_2 \quad (2) \end{aligned}$$

Consider bdcb

$$\begin{aligned} -R_2(I_3 - I_1) - R_4(I_3) - R_4(I_3 - I_2) &= 0 \\ R_2 I_1 + R_H I_2 - I_3(R_2 + R_H + R_6) &= 0. \end{aligned} \quad (3)$$

$$I_1(R_1 + R_2 + R_3) - I_2 R_3 - I_3 R_2 = V_1 \quad (1)$$

$$I_1 R_3 - I_2 (R_3 + R_H + R_6) + R_H I_3 = V_2 \quad (2)$$

$$I_1 R_2 + I_2 R_H - I_3 (R_2 + R_H + R_6) = 0 \quad (3)$$

Matrix form:

$$\begin{array}{ccc|cc} (R_1 + R_2 + R_3) & -R_3 & -R_2 & I_1 & V_1 \\ -R_3 & (R_3 + R_H + R_6) & -R_H & I_2 & V_2 \\ -R_2 & -R_H & (R_2 + R_H + R_6) & I_3 & 0 \end{array}$$

\* Cramer's Rule

$$ax + by = c$$

$$dx + ey = f$$

i) Write the two equations in the matrix form as

$$\begin{bmatrix} a & b \\ d & e \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} c \\ f \end{bmatrix}$$

2) The common determinant is given as

$$\Delta = \begin{vmatrix} a & b \\ d & e \end{vmatrix}$$

$$ae - bd$$

3) For finding the determinant for  $x$ , replace the coefficients of  $x$  in the original matrix by the constants so that we get determinant  $\Delta_1$  given by

$$\Delta_1 = \begin{vmatrix} c & b \\ f & e \end{vmatrix}$$

$$= ce - bf.$$

4) For finding the determinant for  $y$ , replace coefficients of  $y$  by the constants so that we get.

$$\Delta_2 = \begin{vmatrix} a & c \\ d & f \end{vmatrix}$$

$$= af - cd.$$


5) Apply Cramer's rule to get the value of  $x$  and  $y$ .

$$x = \frac{\Delta_1}{\Delta} = \frac{ce - bf}{ae - bd}$$

$$y = \frac{\Delta_2}{\Delta} = \frac{af - cd}{ae - bd}$$

(illy for 3 variables)

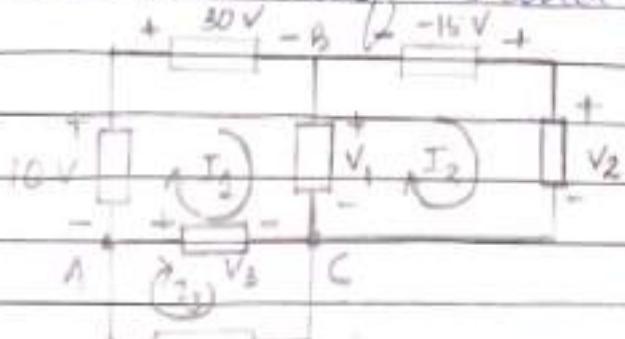- Q1) Applying Kirchhoff's law to different loops, find the values of  $V_1$  and  $V_2$ .



$$\text{Ans} ) \quad 10 - 30 - V_1 + V_3 = 0 \\ V_3 - V_1 = -20 \quad \text{--- (1)}$$

$$V_1 + 15 - V_2 = 0 \\ V_1 - V_2 = -15 \quad \text{--- (2)} \\ -V_3 + 5 = 0 \\ V_3 = 5 \quad \text{--- (3)}$$

Sub (3) in (1)


$$V_1 = -20 + V_3 \\ = -20 + 5 \\ = -15 \text{ V}$$

Sub  $V_1 = -15 \text{ V}$  in (2)

$$V_1 = -15 + V_2 \\ V_2 = +15 - 15 \\ = 0 \text{ V}$$

$$\therefore V_1 = -15 \text{ V} \quad \underline{V_2 = 0}$$

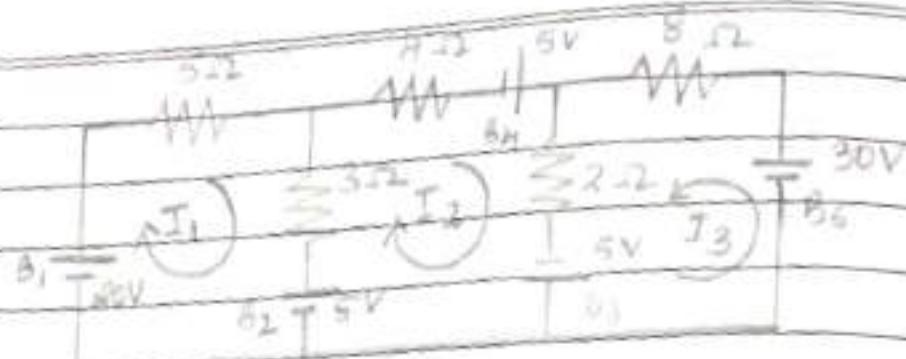- Q2) Determine the current supplied by each battery in the circuit shown in the fig.



Ans) Considering the 1<sup>st</sup> loop

$$20 - 5I_1 - 3(I_1 - I_2) - 5 = 0$$

$$15 = 5I_1 + 3I_1 - 3I_2$$

$$8I_1 - 3I_2 = 15 \quad \text{--- (1)}$$

Considering the 2<sup>nd</sup> loop

$$5 - 3(I_2 - I_1) - 4I_2 + 5 - 2(I_2 + I_3) + 5 = 0$$

$$15 - 3I_2 + 3I_1 - 4I_2 - 2I_2 - 2I_3 = 0$$

$$3I_1 - 9I_2 - 2I_3 = -15 \quad \text{--- (2)}$$

Considering the 3<sup>rd</sup> loop

$$30 - 8I_3 - 2(I_2 + I_3) + 5 = 0$$

$$-8I_3 - 2I_2 - 2I_3 + 35 = 0$$

$$2I_2 + 10I_3 = 35 \quad \text{--- (3)}$$

$$8I_1 - 3I_2 = 15$$

$$3I_1 - 9I_2 - 2I_3 = -15$$

$$2I_2 + 10I_3 = 35$$

8	-3	0	I <sub>1</sub>	=	15
3	-9	-2	I <sub>2</sub>	=	-16
0	2	10	I <sub>3</sub>	=	56

$$\begin{aligned}\Delta &= 8(-90+4) - (-3)(30) \\ &= 8 \times -86 + 90 \\ &= -688 + 90 \\ &= \underline{\underline{-598}}\end{aligned}$$

For finding I<sub>1</sub>

$$\Delta_1 = ?$$

15	-3	0	I <sub>1</sub>		
-15	-9	-2	I <sub>2</sub>		
35	2	10	I <sub>3</sub>		

$$\begin{aligned}\Delta_1 &= 15(-90+4) - (-3)(-150+70) \\ &= -1290 - 240 \\ &= \underline{\underline{-1530}}\end{aligned}$$

$$\begin{aligned}I_1 &= \frac{\Delta_1}{\Delta} = \frac{-1530}{-598} \\ &= \frac{1530}{598} \\ &= \underline{\underline{2.55A}}\end{aligned}$$

For finding I<sub>2</sub>

8	15	0
3	-25	-2
0	35	10

$$\Delta_2 = 8(-250 + 10) - 16(30)$$

$$= -640 - 480$$

$$= -1120$$

$$I_2 = \frac{\Delta_2}{\Delta}$$

$$= -1120$$

$$-598$$

$$= \underline{\underline{1.82A}}$$

for finding  $I_3$

8	-3	15	1
3	-9	-15	
0	2	35	

$$\Delta_3 = 8(-9(35) + 30) - (-3)((35)3) + 15(6)$$

$$= -2280 + 315 + 90$$

$$= -2280 + 405$$

$$= \underline{\underline{-1875}}$$

$$I_3 = \frac{\Delta_3}{\Delta}$$

$$1$$

$$= -1875$$

$$-598$$

$$= \underline{\underline{3.15A.}}$$

Current flowing through  $B_1 = I_1 = 2.55A$

Current flowing through  $B_2 = I_1 - I_2 = 0.73A$


Current flowing through  $B_3 = I_2 + I_3 = 4.95A$

Current flowing through  $B_4 = I_2 = 1.82A$

Current flowing through  $B$  -  $I_2 = 3.13 A$

J.W.

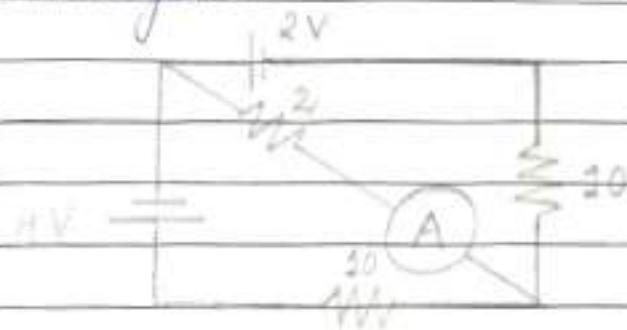- (ii) Find the ammeter current in the fig using loop analysis:



$$4 - 10I_1 - 2(I_1 - I_2) = 0$$

$$4 - 10I_1 - 2I_1 + 2I_2 = 0$$

$$-12I_1 + 2I_2 = -4$$

$$6I_1 - I_2 = +2 \quad \text{---(1)}$$

$$2 - 2(I_2 - I_1) - 10I_2 = 0$$

$$2 - 2I_2 + 2I_1 - 10I_2 = 0$$

$$2I_1 - 12I_2 = -2$$

$$I_1 - 6I_2 = -1 \quad \text{---(2)}$$

$$\begin{array}{|c c|} \hline & \\ \hline & \\ \hline \end{array}$$

$$\begin{array}{|c c|} \hline 6 & -1 \\ \hline 1 & -6 \\ \hline \end{array} \quad \begin{array}{|c|} \hline I_1 \\ \hline J_2 \\ \hline \end{array} \quad \begin{array}{|c|} \hline +2 \\ \hline -1 \\ \hline \end{array}$$

$$\Delta = -36 + 1$$

$$= -35$$

For calculating  $I_1$

$$\begin{array}{|c c|} \hline & \\ \hline & \\ \hline \end{array}$$

$$\begin{array}{|c c|} \hline 2 & -1 \\ \hline -1 & -6 \\ \hline \end{array}$$

$$\Delta_2 = -12 - 1$$

$$= -13$$

$$I_2 = \frac{\Delta_2}{\Delta}$$

$$= \frac{-13}{-35} = \frac{13}{35} A$$

For calculating  $I_2$

G	2
1	-1

$$\Delta_2 = -6 - 2$$

$$= -8$$

$$I_2 = \frac{\Delta_2}{\Delta}$$

$$= \frac{-8}{-35}$$

$$= \frac{8}{35} A$$

i.e. the current through ammeter =  $I_1 - I_2$


$$= \frac{13 - 8}{35} A$$

$$= \frac{5}{35} A$$


$$= \frac{1}{7} A$$

2)  $11 \text{ V} \text{ DC} \rightarrow 0$

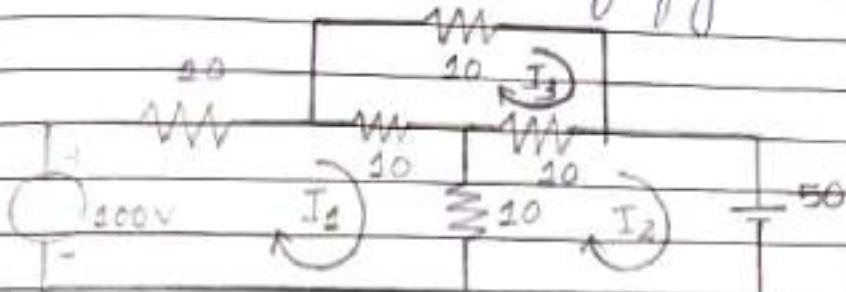(ii) Apply loop current method to find loop currents  $I_1, I_2, I_3$  in the circuit of fig. 2.



Ans) Considering loop 1

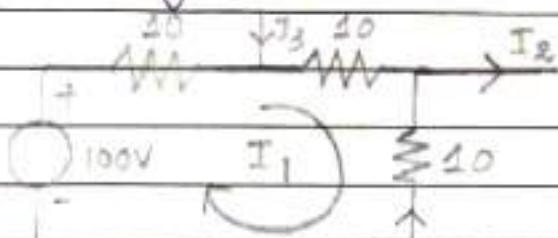


$$100 - 10(I_1) - 10(I_1 - I_3) - 10(I_1 - I_2) = 0$$

$$100 - 10I_1 - 10I_1 + 10I_3 - 10I_1 + 10I_2 = 0$$

$$30I_1 - 10I_2 - 10I_3 = 100$$

$$3I_1 - I_2 - I_3 = 10 \quad \text{--- (1)}$$

Considering loop 2

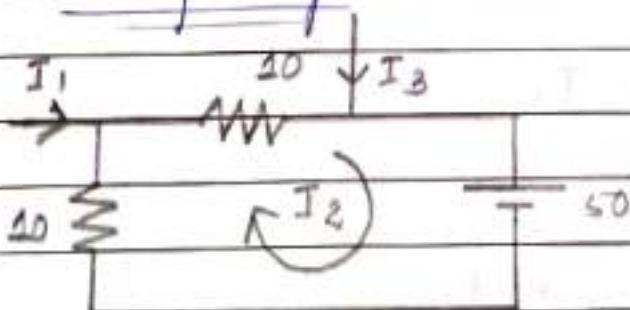


$$-50 - 10(I_2 - I_1) - 10(I_2 - I_3) = 0$$

$$-50 - 10I_2 + 10I_1 - 10I_2 + 10I_3 = 0$$

$$10I_1 - 20I_2 + 10I_3 = 50$$

$$I_1 - 2I_2 + I_3 = 5 \quad \text{--- (2)}$$

Considering loop 3

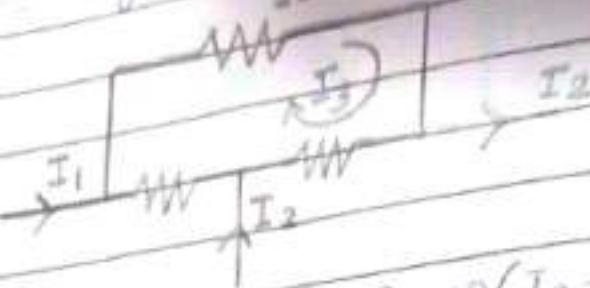

$$\begin{aligned} -10(I_3) - 10(I_3 - I_2) - 10(I_2 - I_1) &= 0 \\ -10I_3 - 10I_3 + 10I_2 - 10I_3 + 10I_1 &= 0 \\ 10I_1 + 10I_2 - 30I_3 &= 0 \\ I_1 + I_2 - 3I_3 &= 0 \quad \text{---(3)} \end{aligned}$$

Matrix representation

$$\left[ \begin{array}{ccc|c|c} 3 & -1 & -1 & I_1 & 10 \\ 1 & -2 & 1 & I_2 & 5 \\ 1 & 1 & -3 & I_3 & 0 \end{array} \right]$$

$$\begin{aligned} \Delta &= 3(6-1) - (-1)(-3-1) + (-1)(1+2) \\ &= 15 - 4 - 3 \\ &= 15 - 7 \\ &= 8 \end{aligned}$$

For finding  $I_1$

$$\left[ \begin{array}{ccc|c} 10 & -1 & -1 & \\ 5 & -2 & 1 & \\ 0 & 1 & -3 & \end{array} \right]$$

$$\begin{aligned} \Delta_1 &= 10(+6-1) - (-1)(-15) + (-1)(5) \\ &= 50 - 15 - 5 \\ &= 50 - 20 = \underline{\underline{30}} \end{aligned}$$

$$I_1 = \Delta_1$$

$$\Delta$$

$$= \frac{30}{8}$$

$$= \underline{\underline{3.75}}$$

$$3.75$$

$$8 \overline{) 180}$$

$$\quad \quad \quad 14$$

$$\quad \quad \quad \underline{\underline{60}}$$

$$\quad \quad \quad 56$$

$$\quad \quad \quad \underline{\underline{16}}$$

$$= \underline{\underline{3.75A}}$$

for finding  $I_2$

3	10	-1
1	5	1
1	0	-3

$$\Delta_2 = 3(-15) - (10)(3+2) + (-1)(-5)$$

$$= -45 + 40 + 5$$

$$= \underline{\underline{0}}$$

$$I_2 = \frac{\Delta_2}{\Delta}$$

$$= \frac{0}{8} = \underline{\underline{0A}}$$

for finding  $I_3$

3	-1	10
1	-2	5
1	1	0

$$1.25$$

$$\Delta_3 = 3(-5) - (-1)(-5) + 10(1+3)$$

$$8 \overline{) 20}$$

$$= -15 - 5 + 20$$

$$\quad \quad \quad 8$$

$$= \underline{\underline{20}}$$

$$\quad \quad \quad \underline{\underline{20}}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{20}{8} = \underline{\underline{2.5A}}$$

$$I_1 = 3.25 \text{ A}$$


$$I_2 = 0 \text{ A}$$

$$I_3 = 1.25 \text{ A}$$

## Mesh Analysis

- Identify the loops/meshes.
- Assign a current variable to each mesh/loop, using a consistent direction (clockwise or anti-clockwise).
- Write Kirchhoff's Voltage Law equations around each mesh.
- Solve the resulting system of equations for all mesh currents.
- Solve for other elements currents and voltages you want using Ohm's law.

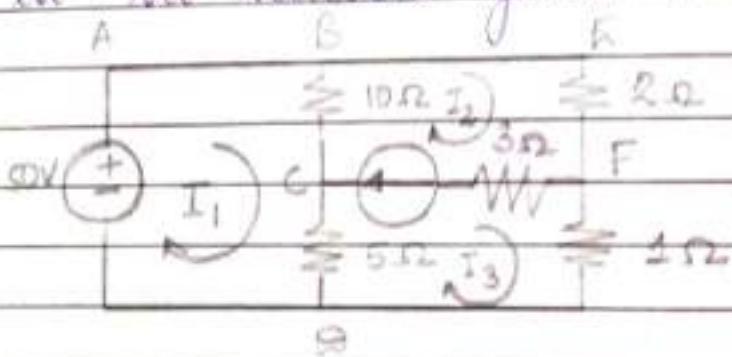Q4) Determine the current in the  $5\ \Omega$  resistor in the network given in fig:



ns) Considering loop abda

$$50 - 10(I_1 + I_2) - 5(I_1 - I_3) = 0$$

$$50 - 10I_1 + 10I_2 - 5I_1 + 5I_3 = 0$$

$$10I_1 + 5I_3 - 10I_2 - 5I_3 = 50$$

$$10I_1 - 10I_2 = 50$$

$$3I_1 - 2I_2 - I_3 = 10 \quad - \textcircled{1}$$

Considering loop bef dcb

$$-2(I_2) - 3(I_2 - I_3) - 10(I_2 - I_1) = 0$$

$$-2(I_2) - 1(I_3) - 5(I_3) - 10(I_2 - I_1) = 0$$

$$-2I_2 - I_3 - 5I_3 + 5I_1 - 10I_2 + 10I_1 = 0$$

$$15I_1 - 12I_2 - 6I_3 = 0$$

$$5I_1 - 4I_2 - 2I_3 = 0 \quad - \textcircled{2}$$

$$I_2 - I_3 = 2A. \quad - \textcircled{3}$$

$$\begin{array}{|ccc|c|c|} \hline & 3 & -2 & -1 & I_1 \\ \hline & 5 & -4 & -2 & I_2 \\ \hline & 0 & 1 & -1 & I_3 \\ \hline \end{array} \begin{array}{c} = \\ = \\ = \\ = \end{array} \begin{array}{c} 10 \\ 0 \\ 2 \end{array}$$

$$\begin{aligned} \Delta &= 3(4+2) - (-2)(-5) + (-1)(5) \\ &= 18 - 10 - 5 \\ &= 18 - 15 \\ &= 3 \end{aligned}$$

Considering  $I_1$

$$\begin{array}{|ccc|} \hline & 10 & -2 & -1 \\ \hline & 0 & -4 & -2 \\ \hline & 2 & 1 & -1 \\ \hline \end{array}$$

$$\begin{aligned} \Delta_1 &= 10(4+2) - (-2)(4) + (-1)(+8) \\ &= 60 + 8 - 8 \\ &= 60 \end{aligned}$$

$$I_1 = \frac{\Delta_1}{\Delta}$$

$$= \frac{60}{3}$$

$$= 20A$$

Considering  $I_2$

3	10	-1
5	0	-2
0	2	-1

$$\begin{aligned}\Delta_2 &= 3(4) - (10)(-5) + (-1)(10) \\ &= 12 + 50 - 10 \\ &= 12 + 40 \\ &= 52\end{aligned}$$

$$\begin{aligned}I_2 &= \frac{\Delta_2}{\Delta} \\ &= \frac{52}{3} = 17.33A\end{aligned}$$

$\frac{2}{3 \sqrt{52}}$   
 $\frac{36}{22}$

Considering  $I_3$

3	-2	10
5	-4	0
0	1	2

$$\begin{aligned}\Delta_3 &= 3(-8) - (-2)(10) + 10(5) \\ &= -24 + 20 + 50 \\ &= 70 - 24 \\ &= 46\end{aligned}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{46}{3} = 15.33A$$


$$\begin{aligned} \text{Current through } 5\Omega \text{ resistor} &= I_3 - I_1 \\ &= 16.33 - 20 \\ &= -4.67A \end{aligned}$$

### Node Analysis

Steps to determine node voltage:

- Select a node as the reference node. Assign voltages  $v_1, v_2, \dots, v_{n-1}$  to the remaining  $n-1$  nodes. The voltages are referenced with respect to the reference node.
- Apply KCL to each of the  $n-1$  nonreference nodes. Use Ohm's law to express the branch current in terms of node voltages.
- Solve the resulting simultaneous equations to obtain the unknown node voltages.

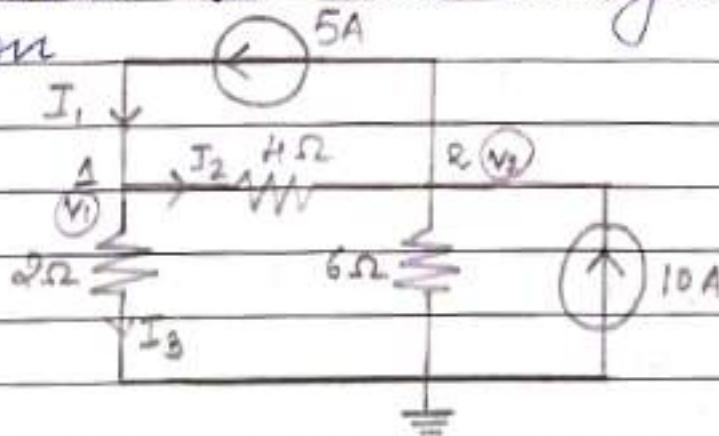a) Calculate the node voltages in the circuit shown



Ans) Consider node 1

$$I_1 = I_2 + I_3$$

$$5 = \frac{v_1 - v_2}{H} + \frac{v_1}{2}$$

$$5 = \frac{v_1 - v_2 + 2v_1}{H}$$

$$20 = 3v_1 - v_2 \quad - \textcircled{1}$$

Consider mode 2

$$5 - 10 + \frac{v_2 - v_1}{H} + \frac{v_2}{6} = 0$$

$$-5 + \frac{6v_2 - 6v_1 + Hv_2}{2H} = 0$$

$$10v_2 - 6v_1 = 120.$$

$$5v_2 - 3v_1 = 60 \quad - \textcircled{2}$$

Using Cramer's rule

3	-1	$v_1$	*	20
-3	5	$v_2$	*	60

$$\Delta = 15 - 3 = 12$$

Finding  $v_1$

20	-1
60	5

$$\Delta_1 = 100 + 60$$

$$= 160$$

$$v_1 = \frac{\Delta_1}{\Delta}$$

$$= \frac{160}{120} = \frac{40}{3} V$$

## Finding $V_e$

$$\begin{array}{r} 3 \quad 20 \\ -3 \quad 60 \end{array}$$


$$\Delta_2 = 180 + 60$$

$$\sqrt{2} = \frac{\Delta_2}{A}$$

$$= \frac{240}{12} = \underline{\underline{20}}.$$

Q2) Find the branch current in the circuit of fig by using

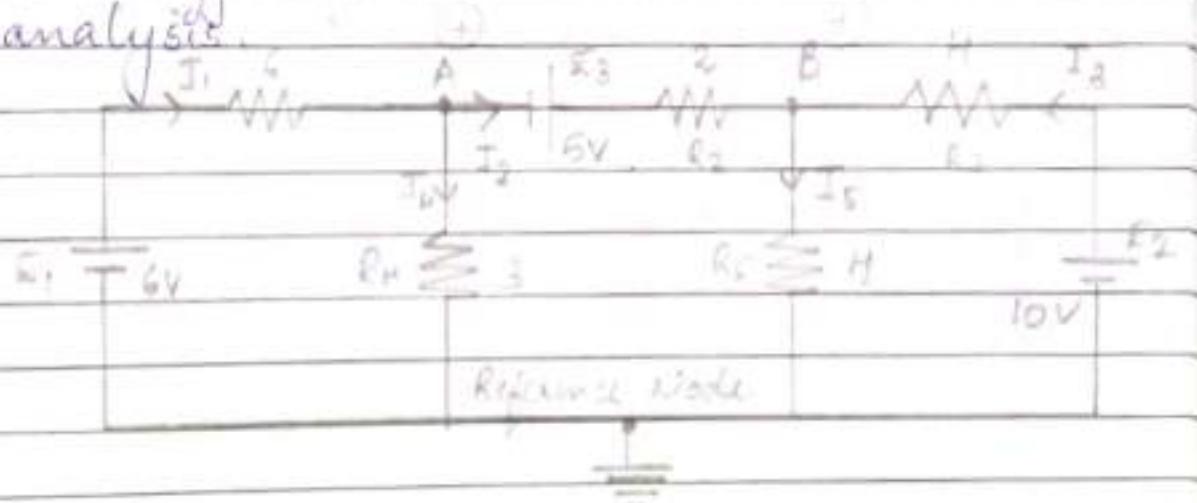- 1) Nodal analysis and
  - 2) Loop analysis.



Ans) i) Consider nodes 1 ( $v_1 > v_2$ )

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_A - 6}{6} + \frac{V_A + \epsilon - V_B}{2} + \frac{V_A - 0}{3} = 0$$

$$V_A - 6 + 3V_A + 15 - 2V_B + 2V_A = 6$$

$$6V_A - 3V_B + 9 = 0$$

$$2V_A - V_B + 3 = 0$$

$$V_B - 2V_A = 3 \quad - \textcircled{1}$$

Considering node 2 ( $V_2 > V_1$ )

$$\frac{V_B - 5 - V_A}{2} + \frac{V_B}{H} + \frac{V_B - 10}{H} = 0$$

$$2V_B - 10 - 2V_A + V_B + V_B - 10 = 0$$

$$4V_B - 2V_A = 20$$

$$2V_B - V_A = 10 \quad - \textcircled{2}$$

Using Cramer's rule

$$\begin{vmatrix} -2 & 1 \\ -1 & 2 \end{vmatrix} \begin{vmatrix} V_A \\ V_B \end{vmatrix} = \begin{vmatrix} 3 \\ 10 \end{vmatrix}$$

$$\Delta = -4 + 1 \\ = -3$$

Considering  $V_A$

$$\begin{vmatrix} 3 & 1 \\ 10 & 2 \end{vmatrix}$$

$$\Delta_1 = 6 - 10 \\ = -4$$

$$V_A = \frac{\Delta_1}{\Delta} = \frac{-4}{-3} = \frac{4}{3} V$$

Considering  $V_B$

-2	3
-1	10

$$\Delta_2 = -20 + 3 \\ = -17$$

$$V_B = \frac{\Delta_2}{\Delta} \\ = \frac{-17}{-3} = \underline{17 \text{ V}}$$

$$I_1 = ?$$

$$I_1 = \frac{-V_A + 6}{6} \\ = \frac{-4 + 6}{3} \\ = \underline{\underline{2}} \\ = \frac{-4 + 18}{18} \\ = \frac{+14}{18} A = \underline{\underline{\frac{7}{9} A}}$$

$$I_2 = ?$$

$$I_2 = \frac{V_A - V_B + 5}{2} \\ = \frac{4 - 17 + 5}{3} \\ = \frac{4 - 17 + 15}{6} = \frac{2}{6} = \underline{\underline{\frac{1}{3} A}}$$

$$I_3 = ?$$

$$I_H = \frac{V_A + 10}{H}$$

$$= \frac{-17 + 10}{3}$$

H

$$= \frac{-7 + 10}{12}$$

$$= \frac{+13}{12} A$$

$$I_H = ?$$

$$I_H = \frac{V_A}{3}$$

$$= \frac{4}{9} A$$

$$I_5 = ?$$

$$I_5 = \frac{V_B}{H}$$

$$= \frac{17}{3 \times 4}$$

$$= \frac{17}{12} A$$

Using loop current method:

Consider loop 1

$$-6I_1 - 5I_H + 6 = 0 \quad -6I_1 - 3(I_1 - I_2) + 6 = 0$$

$$-6I_1 - 3I_1 + 3I_2 + 6 = 0$$

$$9I_1 - 3I_2 = 6$$

$$3I_1 - I_2 = 2 \quad -\textcircled{1}$$

Considering loop 2

$$5 + (-2I_2) - 4(I_2 - I_3) - 3(I_2 - I_1) = 0$$

$$5 - 2I_2 - 4I_2 + 4I_3 - 3I_2 + 3I_1 = 0$$

$$5 + 3I_1 - 9I_2 + 4I_3 = 0$$

$$3I_1 - 9I_2 + 4I_3 = 5 \quad -\textcircled{2}$$

Considering loop 3

$$-4I_3 - 10 - 4(I_3 - I_2) = 0$$

$$-4I_3 - 10 - 4I_3 + 4I_2 = 0$$

$$-8I_3 + 4I_2 - 10 = 0$$

$$-4I_3 + 2I_2 = 10$$

$$-4I_3 + 2I_2 = 5 \quad -\textcircled{3}$$

From  $\textcircled{1}$

$$3I_1 - I_2 = 2$$

$$I_2 = 3I_1 - 2 \quad -\textcircled{4}$$

From  $\textcircled{3}$

$$2I_2 - 4I_3 = 5$$

$$4I_2 = 2I_2 - 5$$

$$I_3 = 2I_2 - 5 \quad -\textcircled{5}$$

Sub  $\textcircled{4}$  &  $\textcircled{5}$  in  $\textcircled{2}$

$$3I_1 - 9(3I_1 - 2) + 4(3I_2 - 5) = -5$$

$$3I_1 - 21I_1 + 18 + 2I_2 - 5 = -5$$

$$3I_1 - 21I_1 + 18 + 2 \times (3I_1 - 2) - 5 = -5$$

$$3I_1 - 21I_1 + 6I_1 + 18 - 4 - 5 = -5$$

$$-18I_1 + 19 = 0 \quad -18I_1 + 14 = 0$$

$$18I_1 = 19 \quad 18I_1 = 14$$

$$I_1 = \frac{1}{2} A$$

$$I_1 = \frac{14}{18} = \frac{7}{9} A$$

From (4)

$$I_2 = 3I_1 - 2$$

$$= 3 \times \frac{7}{9} - 2 = \frac{21 - 18}{9} = \frac{1}{3} A //$$

From (5)

$$I_3 = 2I_2 - 5$$

$$= 2 \times \frac{1}{3} - 5 = \frac{2 - 15}{12} = \frac{-13}{12} A$$

$$I_4 = I_1 - I_2$$

$$= \frac{7}{9} - \frac{1}{3} = \frac{4}{9} = \frac{2}{3} A //$$


$$I_5 = I_2 - I_3$$

$$= \frac{1}{3} + \frac{13}{12}$$

$$= \frac{4 + 13}{12}$$

$$= \frac{17}{12} //$$

# Nodal Analysis or Super node method

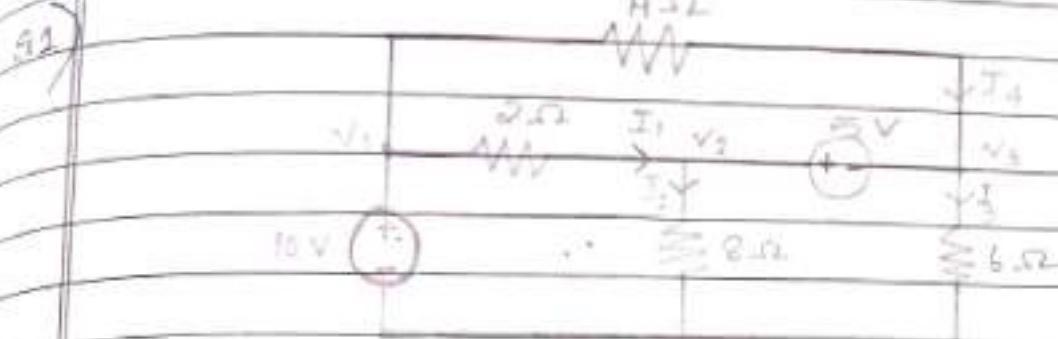

Find  $V_1$ ,  $V_2$  &  $V_3$

(i) Considering node 1

$$V_1 = 10V \quad \text{--- (1)}$$

Considering node 2

$$\frac{V_2}{8} + \frac{(V_2 - V_1)}{2} = 0 \quad \text{--- (2)}$$

Considering node 3

$$\frac{V_3}{6} + \frac{V_3 - V_1}{4} = 0 \quad \text{--- (3)}$$

Adding from (2) & (3)

$$\frac{V_2}{8} + \frac{(V_2 - V_1)}{2} + \frac{V_3}{6} + \frac{(V_3 - V_1)}{4} = 0 \quad \text{--- (4)}$$

$$6V_2 + 24V_2 - 24V_1 + 8V_3 + 12V_3 - 12V_1 = 0$$

$$-36V_1 + 30V_2 + 20V_3 = 0$$

$$36V_1 - 30V_2 - 20V_3 = 0$$

$$360 = 30V_2 + 20V_3$$

$$3V_2 + 2V_3 = 36 \quad - (5)$$

Considering the equation between  $V_2$  &  $V_3$

$$V_2 - V_3 = 5 \quad - (6)$$

$$\begin{array}{|c|c|c|c|c|} \hline & 3 & 2 & V_2 & = & 36 \\ \hline & 1 & -1 & V_3 & & 5 \\ \hline \end{array}$$

$$\Delta = -3 - 2$$

$$= -5$$

Finding  $V_1$

$$\begin{array}{|c|c|} \hline 36 & 2 \\ \hline 5 & -1 \\ \hline \end{array}$$

$$\Delta_1 = -36 - 10$$

$$= -46$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-46}{-5}$$

$$= \underline{\underline{9.2V}}$$

Finding  $V_2$


$$\begin{array}{|c|c|} \hline 3 & 36 \\ \hline 1 & 5 \\ \hline \end{array}$$

$$\Delta_2 = 15 - 36$$


$$= -21$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-21}{-5} = \underline{\underline{4.2V}}$$

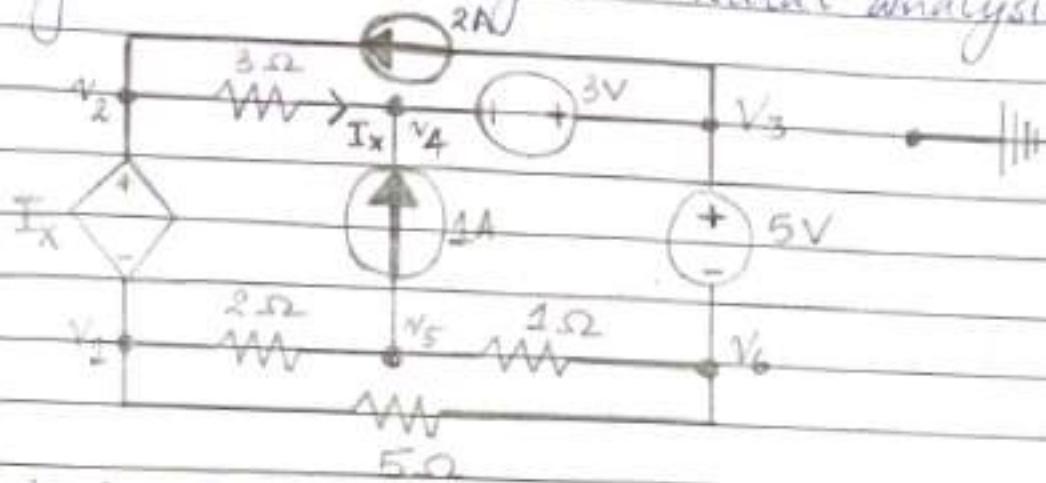Q2) Determine the power of each source after solving the circuit by the nodal analysis.



(ms) Let  $V_3$  be the reference node.

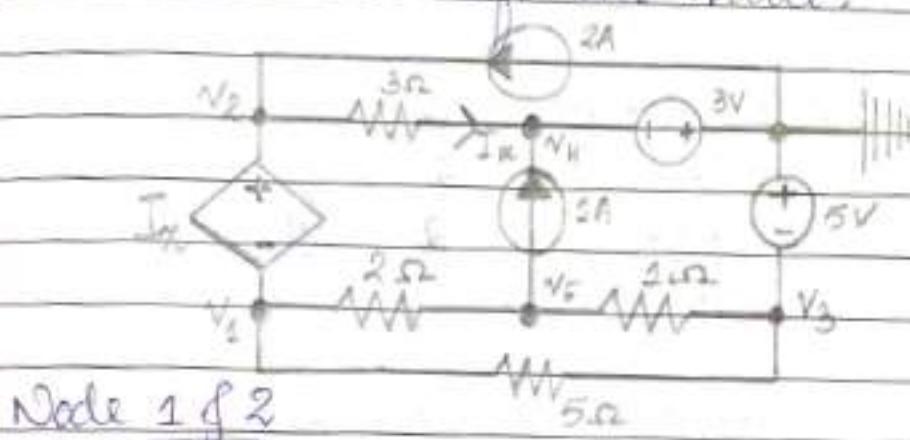

We cannot apply KCL to this node directly due to the presence of voltage source in the branch shown.

$\therefore$  consider 1 & 2 as supernode

$$\frac{V_1 - V_5}{2} + \frac{V_1 - V_3}{5} + \frac{V_2 - V_4}{3} - 2 = 0$$

$$\frac{3V_1 - 3V_5}{6} + \frac{2V_2 - 2V_H}{8} + \frac{V_1 - V_3}{5} - 2 = 0$$

$$15V_1 - 15V_5 + 10V_2 - 10V_H + 6V_1 - 6V_3 - 60 = 0$$

$$21V_1 + 10V_2 - 6V_3 - 10V_H - 15V_5 = 60 \quad \text{--- (1)}$$

Considering the node 3

$$V_3 = -5V \quad - (2)$$

Considering the node 4

$$V_4 = -3V \quad - (3)$$

Considering node 5

$$\begin{matrix} V_5 - V_1 & + \\ 2 & 1 \end{matrix} + \begin{matrix} V_5 - V_3 & + \\ 1 & 2 \end{matrix} + 1 = 0$$

$$V_5 - V_1 + 2V_5 - 2V_3 = -2$$

$$-V_1 - 2V_3 + 3V_5 = -2$$

$$V_1 + 2V_3 - 3V_5 = 2 \quad \cancel{-2}$$

Sub  $V_3$  in eqn.

$$V_1 + 2(-5) - 3V_5 = 2$$

$$V_1 - 10 - 3V_5 = 2$$

$$V_1 - 3V_5 = 12 \quad - (4)$$

Considering the supernode

$$I_X \Rightarrow V_2 - V_1 = 0$$

$$I_X \Rightarrow V_2 - V_4 = 0.$$

$$V_2 - V_1 = V_2 - V_4$$

$$BV_2 - BV_1 = V_2 - V_4$$

$$2V_2 - 3V_1 + V_4 = 0$$

$$3V_1 - 2V_2 - V_4 = 0$$

$$3V_1 - 2V_2 = -3 \quad - (5)$$

From eqn ①

$$21V_1 + 10V_2 + 30 + 30 - 15V_5 = 60$$

$$21V_1 + 10V_2 - 15V_5 = 0 \quad \text{---(6)}$$

Sub ④ & ⑤ in ⑥

$$\begin{matrix} 21V_1 + 10(3V_1 + 3) - 15(V_1 - 12) = 0 \\ \alpha \qquad \qquad \qquad \beta \end{matrix}$$

$$21V_1 + 15V_1 + 15 - 5V_1 + 60 = 0$$

$$31V_1 + 75 = 0$$

$$V_1 = \frac{-75}{31}$$

$$= -2.41 V$$

Sub  $V_1 = -2.41$  in ⑤

$$3(-2.41) - 2V_2 = -3$$

$$2V_2 = 3(-2.41) + 3$$

$$V_2 = (-7.23 + 3)/2$$

$$= -4.23 V/2 = -2.115 V$$

Sub  $V_1 = -2.41$  in ④

$$V_1 - 3V_5 = 12$$

$$3V_5 = -2.41 - 12$$

$$V_5 = \frac{-2.41 - 12}{3}$$

$$= -14.41 V = -4.803 V$$

$$V_1 = -2.115 \text{ V}$$

$$V_2 = -2.115 \text{ V}$$

$$V_3 = -5 \text{ V}$$

$$V_4 = -3 \text{ V}$$

$$V_5 = -4.803 \text{ V}$$

$$P_{2A} = ?$$

$$V_{RA} = -V_2$$

$$= -(-2.115) = 2.115 \text{ V}$$

$$P_{2A} = I_{2A} V_{RA}$$

$$= 2 \times -V_2$$

$$= 2 \times 2.115$$

$$= \underline{\underline{4.230 \text{ W}}}$$

$$P_{1A} = ?$$

$$V_{1A} = (V_5 - V_4)$$

$$= (-4.803 + 3)$$

$$= -1.803 \text{ V}$$

$$P_{1A} = I_{1A} \times V_{1A}$$

$$= 1 \times -1.803$$

$$= \underline{\underline{-1.803 \text{ W}}}$$

$$P_{5V} = ?$$

$$I_{SV} = I_{1\alpha} + I_{3\alpha}$$

$$= V_3 - V_5 + V_3 - V_1$$

$$= \frac{5V_3 - 5V_5 + V_3 - V_1}{5}$$

$$= \frac{6V_3 - 5V_5 - V_1}{5}$$

$$= \frac{6(-5) - 5(-4.803)}{5} = (-20.41)$$

$$= \frac{-30 + 24.015}{5} = 0.41$$

$$= \frac{-16.985}{5} = -3.575 A$$

$$P_{5V} = V_{5V} \times I_{5V}$$

$$= 5 \times \frac{-3.575}{5}$$

$$= -3.575 W$$

$$P_{3V} = ?$$

$$I_{3V} = I_{3\Omega} \neq 1A$$

$$= \frac{V_H - V_2}{3} \neq 1$$

$$= \frac{V_H - V_2}{3} \neq 3$$

$$= -3 + 2.115 \neq 3$$

$$= \frac{-6 + 2.115}{3} A$$

$$P_{3V} = V_{3V} I_{3V}$$

$$= 3 \times \frac{2.115 - 6}{3}$$

$$= -3.885 W$$

$$P_x = V_x I_x$$


$$\begin{aligned}V_x &= V_2 - V_1 \\&= -2.115 + 2.41 \\&= \underline{-0.295 \text{ V}}\end{aligned}$$

$$\begin{aligned}I_x &= I_{2A} + I \\&= 2 + (V_2 - V_1) \\&= 2 + (-0.295) \\&= 1.705 \text{ A}\end{aligned}$$

$$\begin{aligned}P_x &= V_x I_x \\&= 0.295 \times 1.705 \\&= \underline{\underline{0.502 \text{ W}}}\end{aligned}$$
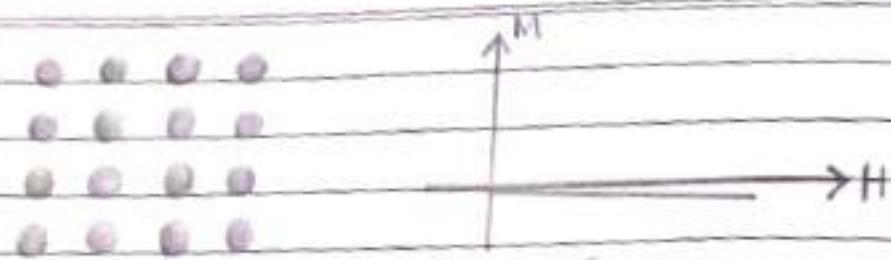
## Module - 2 Elementary Concept of Magnetic Materials

- \* A magnetic is a material or object that produces a magnetic field.
  - ↳ Iron, steel, nickel, cobalt
- \* Classified into 3 types
  - Diamagnetic material
  - Paramagnetic material
  - Ferromagnetic material
- \* Diamagnetic materials
  - Diamagnetic substances are composed of atoms which have no net magnetic moments.
  - i.e. all the orbital shells are filled and there are no unpaired electrons.
  - When exposed to a field, a negative magnetization is produced and thus the susceptibility is negative.
  - Susceptibility is measure of how much a material will become magnetized in an applied magnetic field.



Magnetization and magnetic field intensity.

### \* Paramagnetic materials


Some of the atoms or ions in the materials have a net magnetic moment due to unpaired electrons.

When placed in a magnetic field, magnetic field within the material gets enhanced.

When placed in a non uniform MF, it tends to move from low to high field region.

Have permanent dipole moment.


e.g. Aluminium, Sodium, Copper chloride.

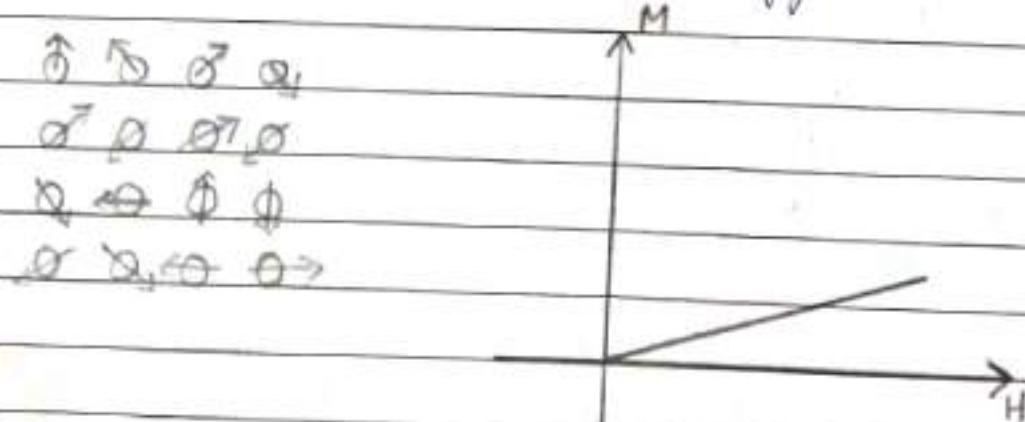

## Ferromagnetic Materials

- Gets magnetized even by weak magnetic field.
- Ferromagnetic materials exhibit parallel alignment of moments resulting in large net magnetization even in the absence of a magnetic field.

e.g. Fe, Ni, Co.

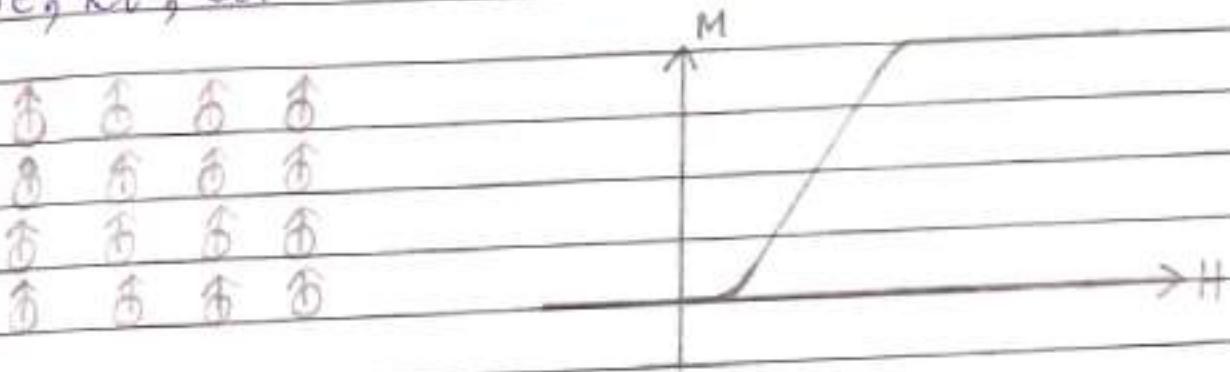

## Classification of magnets

- Permanent magnet -  
Retain magnetism even after removing the external magnetic field.
- An retain their magnetism and magnetic properties for a longer time. Strongly magnetized hard materials make up permanent magnets.  
Hardened steel and alloy of steel can be transformed into paramagnetic permanent

## magnets - artificial magnets.

- A permanent magnet does not require a continuous supply of electrical energy to maintain its magnetic field.

### \* Electromagnet

- Magnetization is done by passing electric current in a coil surrounding the material. It is called electromagnet.
- Strength of electromagnet varies according to the flow of electric current into it.
- An electromagnetic magnet only displays magnetic properties when an electric current is applied to it.
- An electromagnet's magnetic field can be rapidly manipulated over a wide range by controlling the amount of electric current supplied to the electromagnet.

### \* Magnetic Induction

- Phenomenon of changing magnetic substance to magnet.
- Two properties  
i) Attraction

## 2) Repulsion

- Magnet has 2 end-poles

North pole

South pole.

## • Magnetic field

Space around a magnet where magnetic effect can be detected.

## • Magnetic flux

Represents total number of magnetic lines of force in a magnetic field.

Denoted by  $\phi$

Unit: Weber (Wb)

## • Magnetic Flux Density

Flux passing per a unit area.

B

Wb/m<sup>2</sup> or Tesla (T)

$$B = \phi/A$$

## • Permeability / Absolute Permeability

Ability of a material to pass/conduct magnetic flux.

$$\mu = \mu_0 \times 10^{-6} \text{ H/m}$$

### Relative permeability

Permeability with resp. to free space

$$\mu_r$$

$$\mu_r = \mu/\mu_0$$

Relative permeability of air is 1.

### Magnetic field intensity

Force experienced in a unit north pole placed at that point.

$$H$$

$$\text{N/Wb}$$

$$B = \mu H \quad (\mu = \mu_0 \mu_r)$$

### Magneto motive force (mmf)

Magnetic pressure that sets up magnetic flux in a magnetic circuit.

MMF - no of turns in of coil  $\times$  current in it  
Unit AT (ampere turns).

### Reluctance

Opposition offered to magnetic lines of force in a magnetic circuit.

$$S$$

$$\text{AT/Wb}$$

6/14

- $L$  - length of magnetic path
- $A$  - cross sectional area.

### Permeance

### Reciprocal of reluctance

 $\text{Wb/AT}$ 

## \* Electric and Magnetic Circuit - comparison

### Electric circuit

### Magnetic circuit

- Path traced by the current path traced by the magnetic field is known as electric current. flux is called as magnetomotive force.
- EMF is the driving force MMF is the driving force in the electric circuit. in the magnetic circuit. The unit is ampere turns.
- There is a current in there is a flux  $\Phi$  in the electric circuit which magnetic circuit which is measured in amperes. is measured in webers.
- The flow of electrons decides the current in the lines of force decides the flux.
- Resistance ( $R$ ) oppose the Reluctance ( $S$ ) is opposed flow of the current. by magnetic path to the flux. The unit is Atmuls.
- The unit is Ohm.
- $R = \rho \frac{l}{A}$

Directly proportional to  $l$   
Inversely proportional to  $A$   
Depends on nature of material.

$S = \mu_0 \frac{l}{A} \text{ Atmuls}$

$S = \mu_0 / Directly proportional to l. Inversely proportional to A. Directly proportional to u - N.A. Inversely proportional to A$

- The current  $I$  - MMF relation


The flux - MMF / Reluctance

- The current density
- Kirchhoff current law
- Faraday's law is applicable to the electric circuit.


The flux density  
Kirchhoff mmf law &  
flux law is applicable to  
the magnetic flux.
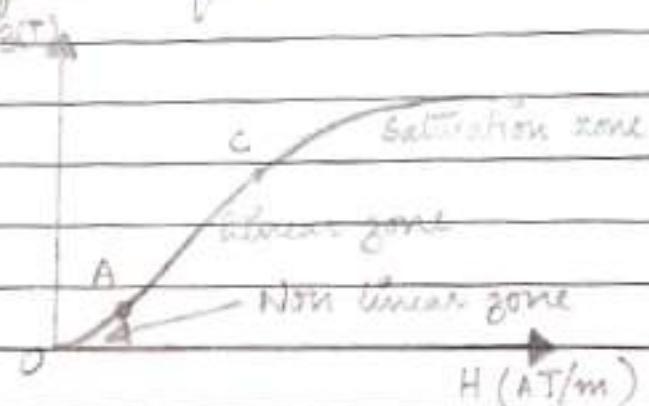
## Magnetization Curve (BH Curve)

- Graph between magnetic flux density ( $B$ ) and magnetic field ( $H$ ).



## Magnetic Hysteresis

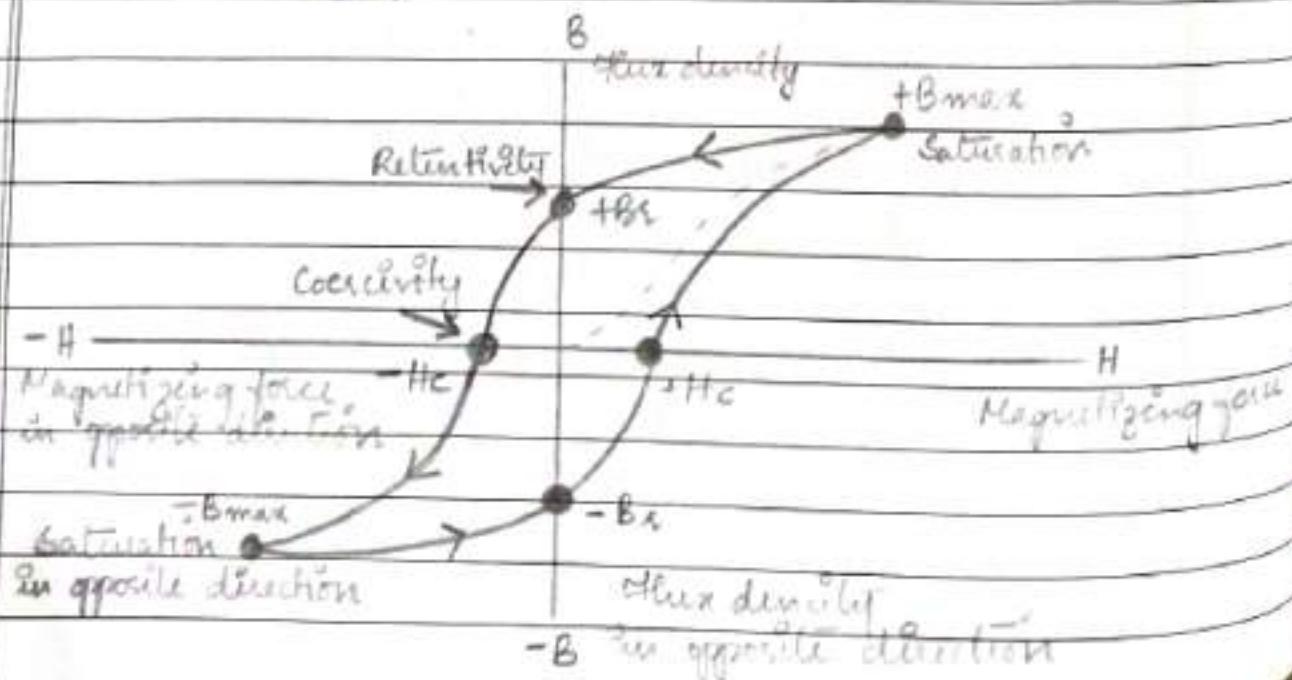


## Reluctivity

It is defined as the degree to which a magnetic material gains its magnetism after magnetizing force ( $H$ ) is reduced to zero.
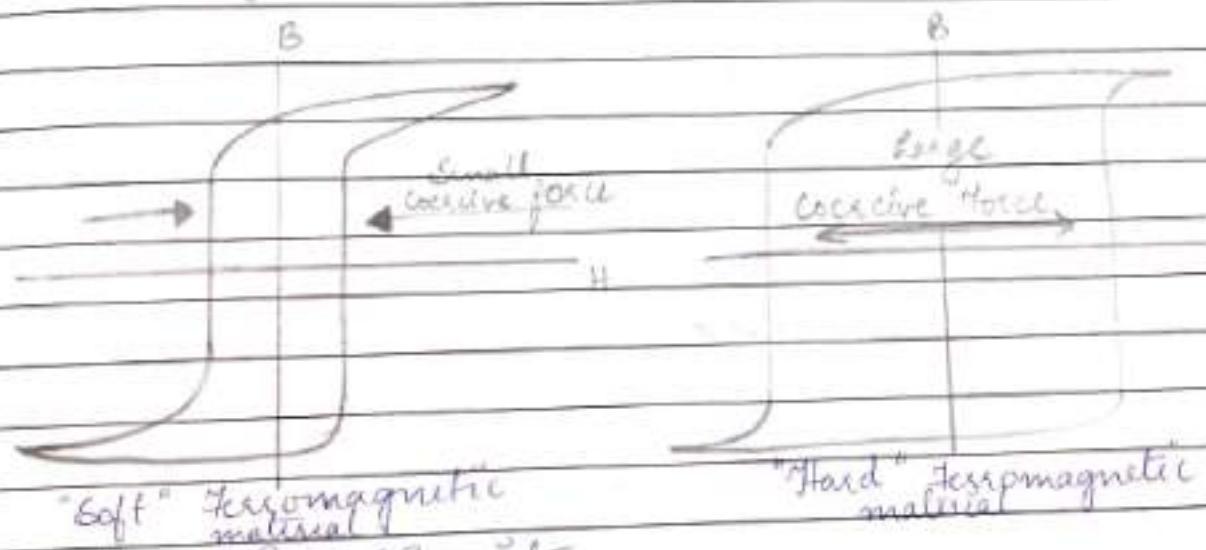
## Cores

The amount of reverse driving field required to demagnetize it is called its coercivity.



## Magnetic Circuit

Closed path followed by magnetic lines of force.

$$\frac{B}{H} = \frac{l}{\mu_0 A}$$

$l$  is the length in 'm'.

$\mu_0$  is the permeability of vacuum, equal to  $4\pi \times 10^{-7}$  henry/metre.

- $\mu_r$  is the relative permeability of the material
- $\mu$  is the permeability of the material ( $\text{H} \cdot \text{A}/\text{Vs}$ )
- $A$  is the cross-sectional area of the circuit in square meters.

### \* Composite magnetic circuit

$$\therefore S = \frac{l_1}{\mu_0 M_{11} A_1} + \frac{l_2}{\mu_0 M_{12} A_2} + \frac{l_3}{\mu_0 M_{23} A_3}$$

total MMF - flux  $\times$  reluctance ( $S$ )

$$\therefore \phi = \left[ \frac{l_1}{\mu_0 M_{11} A_1} + \frac{l_2}{\mu_0 M_{12} A_2} + \frac{l_3}{\mu_0 M_{23} A_3} \right] \left\{ \begin{array}{l} \{\text{Vs}\} \\ (\text{air}) \end{array} \right\}$$

Magnetic flux density,

$$B = \frac{\phi}{A}$$

$$\therefore \text{total MMF} = \frac{B_1 l_1}{\mu_0 M_{11}} + \frac{B_2 l_2}{\mu_0 M_{12}} + \frac{B_3 l_3}{\mu_0 M_{23}} =$$

- (Q) An iron ring having cross-sectional area of  $400 \text{ mm}^2$  and mean circumference of  $500 \text{ mm}$  carries a coil of 250 turns wound uniformly around it. Calculate

- Resistance of the ring.
- Current required to produce a flux of  $100 \text{ mWb}$  in the ring.

Relative permeability of iron is 400

$$l_1 = l$$

$$= 4\pi \times A$$

$$l = 500 \times 10^{-3} \text{ m}$$

$$A = 400 \times 10^{-6} \text{ m}^2$$

$$n = 250$$

$$N_s = 1100$$

$$M_0 = H\pi \times 10^{-7}$$

$$S = 500 \times 10^{-3}$$

$$H\pi \times 10^{-7} \times 400 \times 1100 \times 10^{-6}$$

$$= \frac{500 \times 10^{-3}}{16 \times H \times 10^4 \times \pi} \times 10^4 \times 10^6$$

$$= \frac{500 \times 10^{10}}{64\pi \times 10^4}$$

$$= \frac{500 \times 10^6}{64\pi}$$

$$\underline{S = 2.48 \times 10^6 \text{ AT/Wh}}$$

b)  $I = ?$

$$\phi = 1000 \text{ mwb} = 1000 \times 10^{-6} \text{ wb}$$

$$\text{mmf} = \phi \times S$$

$$NI = \phi \times S$$

$$I = \frac{\phi \times S}{N}$$

$$= \frac{1000 \times 10^{-6}}{825\phi} \times 2.48 \times 10^6$$

$$= \frac{2.48}{825\phi}$$

$$= \frac{2.48}{825\phi}$$

$$= \underline{9.92 \text{ A}}$$

92) A mild steel ring has a mean circumference of 500 mm and a uniform cross-sectional

area of  $300 \text{ mm}^2$ . Calculate the mmf required to produce a flux of  $500 \mu\text{wb}$ ? Assume  $\mu_s = 1200$ .

Ans)

$$\begin{aligned}l &= 500 \text{ mm} \\&= 500 \times 10^{-3} \text{ m} \\A &= 300 \text{ mm}^2 \\&= 300 \times 10^{-6} \text{ m}^2 \\H_s &= 1200 \\M_o &= 4\pi \times 10^{-7}\end{aligned}$$

$$S = l$$

$$H_0 M_o A$$

$$= \frac{500 \times 10^{-3}}{4\pi \times 10^{-7} \times 1200 \times 300 \times 10^{-6}}$$

$$= \frac{500 \times 10^{-3} \times 10^7 \times 10^6}{144 \pi \times 10^4}$$

$$= \frac{500}{144 \pi} \times 10^6$$

$$= 1.10 \times 10^6 \text{ AT/wb}$$

$$\text{mmf} = \phi \times S$$

$$= 500 \times 10^{-6} \times 1.1 \times 10^6$$

$$= 550 \text{ AT}$$

- 23) An iron ring of mean length 60 cm has an air gap of 2mm and a winding of 300 turns. If the relative permeability of iron used in the ring is 400 when a current of 1.5 A flows through it, find

The flux density?

$$l = 60\text{ cm}$$

$$= 60 \times 10^{-2} \text{ m}$$

$$l_2 = 2\text{ mm}$$

$$= 2 \times 10^{-3} \text{ m}$$

$$n = 300$$

$$U_s = 400$$

$$I = 1.5 \text{ A}$$

$$B = ?$$

$$\text{mmf} = Hl$$

$$\text{mmf}_1 = H_1 l_1$$

$$B = \mu H$$

$$H = \frac{B}{\mu_0 M_r}$$

$$\therefore \text{mmf}_1 = \frac{B}{\mu_0 M_r} \times l_1$$

$$\begin{aligned} \text{mmf}_2 &= \frac{B l_2}{\mu_0 M_r} \quad \left\{ U_s = 1 \text{ m} \right\} \\ &= \frac{B l_2}{M_r} \end{aligned}$$

$$\text{total mmf} = \text{mmf}_1 + \text{mmf}_2$$

$$N \times I = \frac{B l_1}{\mu_0 M_r} + \frac{B l_2}{M_r}$$

$$300 \times 1.5 = \frac{B}{M_r} \left\{ l_1 + l_2 \right\}$$

$$300 \times 1.5 \times M_r = B \left\{ \frac{60 \times 10^{-2}}{400} + \frac{2 \times 10^{-3}}{} \right\}$$

$$450 \times 4\pi \times 10^{-7} = B \left\{ \frac{60 \times 10^{-2} + 8 \times 10^{-3}}{400} \right\}$$

$$450 \times 400 \times 4\pi \times 10^{-7} = B$$


$$60 \times 10^{-2} + 8 \times 10^{-3}$$

$$B = \frac{2260800 \times 10^{-7}}{1.4}$$

$$= 161.1854 \cdot 10^{-7}$$

$$= 0.1615 \text{ (approx) T}$$

## \* Parallel Magnetic Circuit

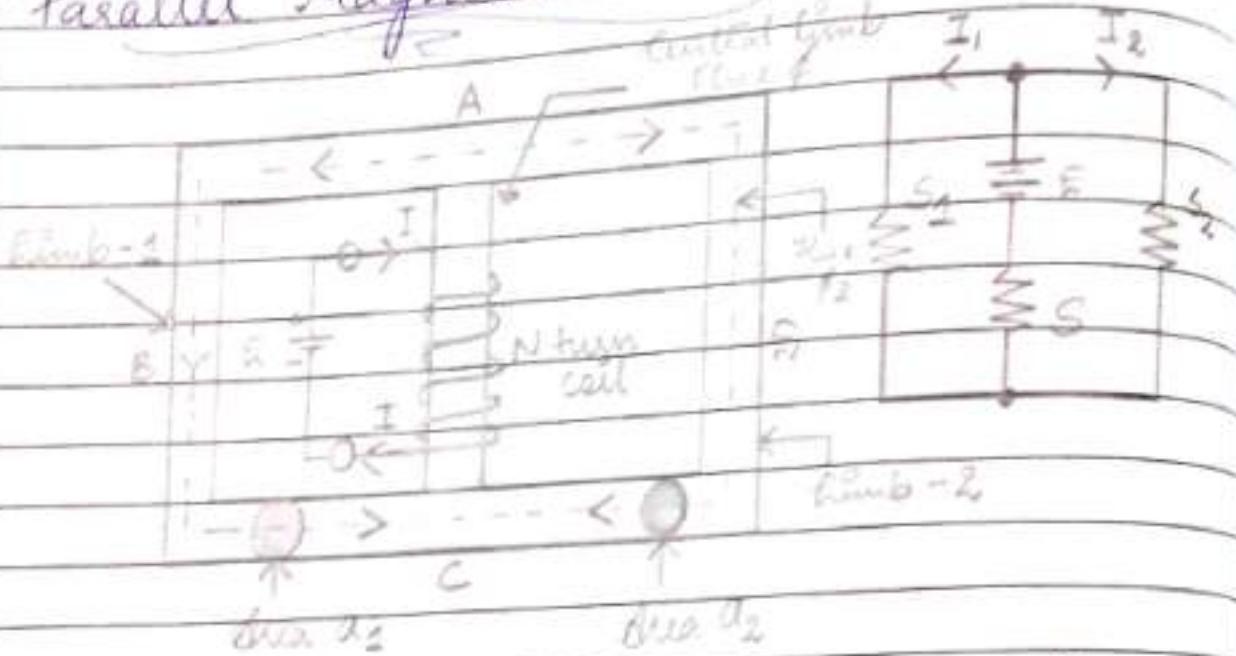

The total m.m.f produced by the coil of N turns is,

$$\text{Total mmf} = N \times I \text{ (AT)}$$

Total m.m.f can also be expressed as,

$$\text{total m.m.f} = \text{total reluctance} * \text{Total flux}$$

$$\text{m.m.f for path ABCA : } F = \text{MMF of path ABC} + \text{MMF of path AC}$$

Thus total MMF = MMF of central limb + MMF of limb - 1 or 2

$$\therefore S \times \phi = NI = \phi_s s_c + |I_1 s_1 \text{ or } I_2 s_2|$$

The reluctances  $S_1, S_2$ , and  $S_c$  are given by

$$S_1 = \frac{l_1}{\mu a_1}, S_2 = \frac{l_2}{\mu a_2}, S_c = \frac{l_c}{\mu a_c}$$

Assuming the cross sectional area of the three limbs to be same i.e.

$$a_1 = a_2 = a_c = a.$$

The expression for  $S_1, S_2, S_c$  gets modified as

$$S_1 = \frac{l_1}{\mu a}, S_2 = \frac{l_2}{\mu a}, S_c = \frac{l_c}{\mu a}$$

Substituting these values in equations

Total MMF,

$$F = \frac{\phi_1 \times l_1}{\mu a} + \frac{\phi_c \times l_c}{\mu a}$$

$$\therefore F = \frac{B_1 l_1}{\mu} + \frac{B_c l_c}{\mu}$$

$$= \frac{B_1 l_1 + B_c l_c}{\mu}$$

$$\text{and } F = \frac{B_2 l_2}{\mu} + \frac{B_c l_c}{\mu}$$

$$= \frac{B_2 l_2 + B_c l_c}{\mu}$$

$$\text{But } (B/\mu) = H$$

$$\therefore \text{for loop ABCA, MMF}(F) = H_1 l_1 + H_c l_c$$

$$\text{and for loop ADCA, MMF}(F) = H_2 l_2 + H_c l_c$$

## \* Energy stored in a magnetic field

$$e = L \frac{di}{dt}$$

$$V = iR + L \frac{di}{dt}$$

Multiplying through out by  $i \cdot dt$

$$Vi \cdot dt = i^2 R dt + L di$$

Switch

## \* Energy absorbed by the magnetic field during time $dt$

$$= L i \frac{di}{dt} \text{ Joules}$$


$$\text{Total energy} = \int_0^1 L i \cdot di$$

$$= L \int_0^1 i \frac{di}{dt}$$

$$= L \left[ \frac{i^2}{2} \right]_0^1$$

$$= \frac{1}{2} L i^2$$

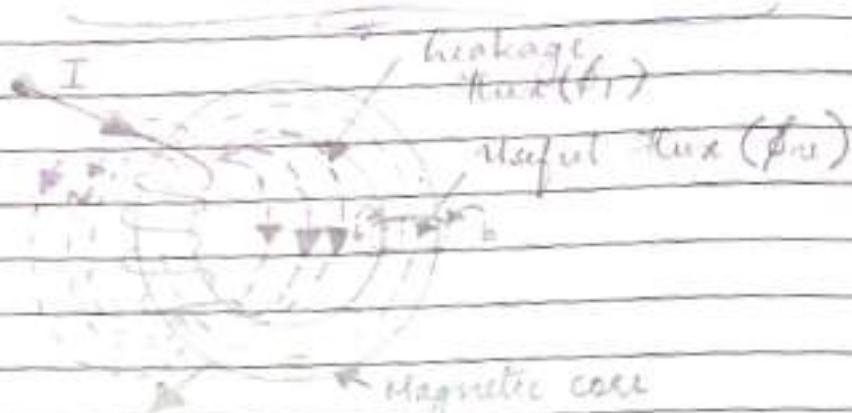- Leakage and fringing in magnetic circuit



- Total flux = useful flux + leakage flux

- leakage factor

$$\lambda = \frac{\text{total flux}}{\text{useful flux}}$$

- Force experienced by a current-carrying conductor in a magnetic field


$$\bullet F = B i l \text{ (newton)} ; F = B i l s i n \theta$$

$B \rightarrow$  flux density

$i \rightarrow$  current through the conductor

(A)

$l \rightarrow$  conductor length

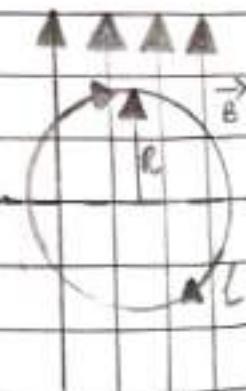

- Q1) A circular iron ring having cross sectional area of  $20 \text{ cm}^2$  and length 30 cm in iron has an airgap of 2 mm made by saw cut.

Relative permeability of iron is 900. The ring is wound with a coil of 2500 turns and current in the coil is 3A. Determine air gap flux. Given leakage coefficient is 1.1.

$$\text{Ans} \quad A = 20 \text{ cm}^2$$

$$= 20 \times 10^{-4} \text{ m}$$

$$l = 30 \text{ cm}$$

$$= 30 \times 10^{-2} \text{ m}$$

$$l_a = 2 \text{ mm}$$

$$= 2 \times 10^{-3} \text{ m}$$

$$\mu_R = 900$$

$$n = 2500$$

$$I = 3 \text{ A}$$

$$\lambda = 1.1$$

$$\lambda = \frac{\text{total flux}}{\text{useful flux}}$$

$$1.1 = \frac{\phi_{\text{total}}}{\phi_g}$$

$$\phi_g = \frac{\phi_{\text{total}}}{1.1}$$

$$NI = \phi_{\text{total}} \times S_{\text{total}}$$

$$S_{\text{total}} = S_I + S_A$$

$$= \frac{l_I + l_A}{\mu_0 \mu_R A}$$

$$= \frac{30 \times 10^{-2} + 2 \times 10^{-3} \times 900}{4\pi \times 10^{-7} \times 900 \times 20 \times 10^{-4}}$$

$$= \frac{30 \times 10^{-2} + 18 \times 10^{-1}}{4 \times 9 \times 2 \times 3.14 \times 10^{-11}}$$

$$= \frac{0.30 + 1.8}{22608 \times 10^{11}}$$

$$S = \frac{2.1 \times 10^{-11}}{22608}$$

$$\text{So } S = 2.26 \times 10^{-11} \text{ A}$$

$$\phi_{\text{total}} = NI$$

$N_{\text{total}}$

$$= \frac{2500 \times 3}{2500 \times 3 \times 22608} = 2.1$$

$$= \frac{2500 \times 3 \times 10^{16}}{9.288} = 807428571.4 \times 10^{11}$$

$$\phi_g = \frac{\phi_{\text{total}}}{1.1}$$

$$= \frac{807428571.4 \times 10^{11}}{1.1}$$

$$= 7.34025974 \times 10^{16}$$

$$\phi_g = 7.340 \times 10^{-3} \text{ wb}$$

### \* Induced e.m.f.

- Two types :
- Dynamically induced e.m.f
- Statically induced e.m.f
- Dynamically Induced emf

By moving a conductor in a uniform magnetic field and e.m.f produced in this way is known as dynamically induced e.m.f.

Area swept by conductor =  $l dx$

Flux cut by the conductor = flux density  $\times$   
area

$$= B \cdot l \cdot dx \text{ (weber)}$$

According to Faraday's law

$e$  = rate of change of flux linkage


$$= \frac{B l dx}{dt} \quad \text{conductor}$$

$$= Blv \text{ (volt)}$$

where  $v = \frac{dx}{dt} \rightarrow \text{velocity}$ .

Dynamically induced e.m.f =  $Blv$  (volt)

$$e = Blvsin\theta \text{ (volt)}$$

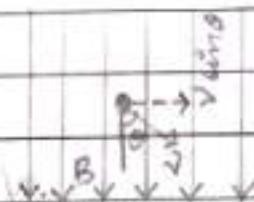


\* Statically Induced e.m.f

By changing the magnetic flux

eg: transformer

Magnitude and direction can be changed

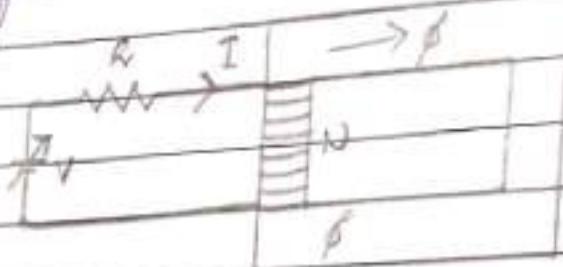- Two types
- Self induced e.m.f
- Mutually induced e.m.f
- \* Self induced emf
- Self-induced emf is the e.m.f induced in the coil due to the change of its own flux linked with it.



- The property of coil, which opposes a change of current or flux through it, is called its self inductance,  $h$ .

- \* Self inductance of the coil

$$e = -N \frac{d\phi}{dt} - 0$$

$$N \phi \propto I$$

$$= -\frac{d(N\phi)}{dt}$$

$$e = -\frac{dI}{dt} \times h - 0 \quad \text{if } h \text{ is the self inductance}$$

- \* Unit of inductance - Henry

$$h = -\frac{e}{di/dt}$$

1 Henry = 1 volt  
1 ampere/second.

1 Henry is the amount of inductance of a coil in which rate of change of current of one ampere induces an e.m.f. of one volt.

Comparing eqns ① and ②

$$N \frac{d\phi}{dt} = - L \frac{dI}{dt}$$

Integrating

$$N\phi = L I$$


$$L = N\phi$$


I

Self inductance of the coil is the flux linkage per ampere.

Mutually induced e.m.f

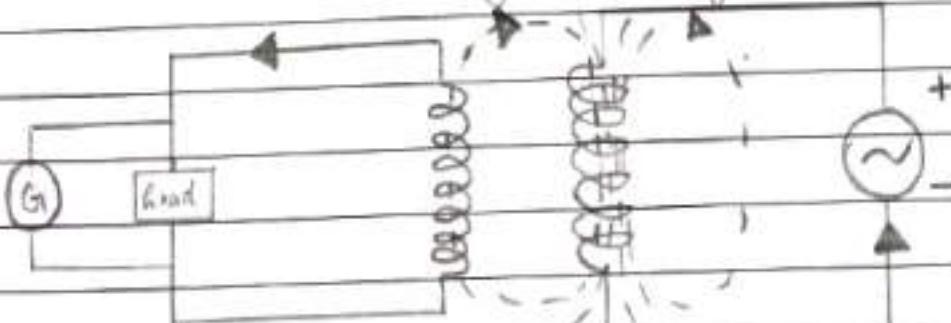Mutual induction : Generation of induced emf in a circuit by changing the current in the neighbouring circuit



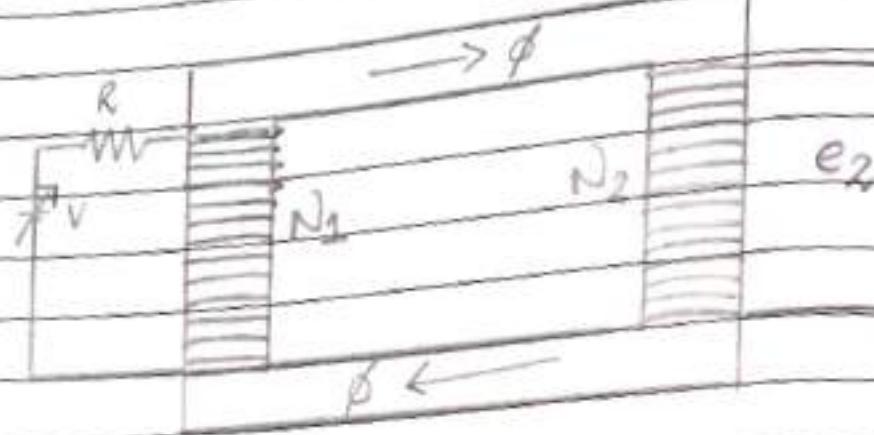

$$e_2 = -N_2 \frac{d\phi}{dt} \quad \text{--- (1)}$$

But  $\frac{d\phi}{dt} \propto \frac{dI_1}{dt}$

$$e_2 \propto -\frac{dI_1}{dt}$$

$$e_2 = -M \frac{dI_1}{dt} \quad \text{--- (2)}$$

Equating (1) and (2)

$$N_2 \frac{d\phi}{dt} = M \frac{dI_1}{dt}$$

Integrating,

$$N_2 \phi = MI_1$$

$$M = \frac{N_2 \phi}{I_1}$$

Similarly,

$$M = \frac{N_1 \phi}{I_2}$$

## Coefficient of coupling.

$$\phi_2 = k_1 \phi_1$$

$$M = \frac{N_2 \phi_2}{I_1} = \frac{N_2 k_1 \phi_1}{I_1} - ①$$

$\phi_2$  produced in second coil.

$$M = \frac{N_1 \phi_1}{I_2} = \frac{N_1 k_2 \phi_2}{I_2} - ②$$

Multiplying ① & ②

$$M^2 = \frac{N_2 k_1 \phi_1 \times N_1 k_2 \phi_2}{I_1 \times I_2}$$

$$M^2 = k_1 k_2 B_1 B_2$$

$$\{k = \sqrt{k_1 k_2}\}$$

$$k = \frac{M}{\sqrt{B_1 B_2}}$$

$\{k$  is called coefficient  
of coupling.

## Self Inductance of a solenoid

$l \rightarrow$  length of the solenoid

$N \rightarrow$  number of turns

$I \rightarrow$  current through the solenoid

$A \rightarrow$  Area of cross-section of the solenoid

$L \rightarrow$  Self Inductance of the solenoid.

$$\text{Flux } (\phi) = \frac{\text{MMF}}{\text{Reluctance}}$$

$$\phi = \frac{N_2 I}{R / \text{Molal}} - ①$$

$$\text{But } h = \frac{N\Phi}{I}$$

$$\therefore \Phi = \frac{NI}{N} - \textcircled{2}$$

Comparing equations (1) and (2)

$$NI = N I$$

$$N = l/A \text{ (mole)}$$

$$h = \frac{N^2 A}{l} \text{ (mole)}$$

$$\text{But resistance } (S) = \frac{l}{A \text{ (mole)}}$$

$$\therefore h = \frac{N^2}{S}$$

Q) Derive the expression for effective Inductance when 2 coils are connected in

- 1) Series
- 2) parallel

Ans) (9) Consider induced emf across each conductor

a) aiding

$$N_1 \cdot h_1 \frac{dI}{dt} - \textcircled{1}$$

$$N_1 = h_1 \frac{dI}{dt} + M \frac{dI}{dt} - \textcircled{2}$$

$$N_2 = h_2 \frac{dI}{dt} + M \frac{dI}{dt} - \textcircled{3}$$

$$\text{total voltage} = N_1 + N_2$$

$$(2) + (3) = h_1 \frac{dI}{dt} + M \frac{dI}{dt} + h_2 \frac{dI}{dt} + M \frac{dI}{dt}$$

$$N = -(h_1 + h_2 + 2M) \frac{dI}{dt}$$

∴ from ①

$$L' = h_1 + h_2 + 2M$$

Effective inductance when 2 coils are connected in series.

b) opposing.

$$V = L'' \frac{dI}{dt} - ①$$

$$N_1 = h_1 \frac{dI}{dt} - M \frac{dI}{dt} - ②$$

$$N_2 = h_2 \frac{dI}{dt} - M \frac{dI}{dt} - ③$$

$$(2) + (3) = h_1 \frac{dI}{dt} + h_2 \frac{dI}{dt} - 2M \frac{dI}{dt}$$

$$= (h_1 + h_2 - 2M) \frac{dI}{dt}$$

∴ from ①

$$L'' = h_1 + h_2 - 2M$$

Effective inductance when 2 coils are connected in series.

(iii) Parallel connection

$$V = h_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt} - \textcircled{1}$$

$$V = h_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt} - \textcircled{2}$$

From  $\textcircled{1}$

$$V - M \frac{dI_2}{dt} = \frac{dI_1}{dt} - \textcircled{3}$$

$h_1$

Sub  $\textcircled{3}$  in  $\textcircled{2}$

$$V = h_2 \frac{dI_2}{dt} + M \left( V - M \frac{dI_2}{dt} \right)$$

$h_1$

$$V = h_1 h_2 \frac{dI_2}{dt} + M V - M^2 \frac{dI_2}{dt}$$

$h_1$

$$V h_1 - M V = (h_1 h_2 - M^2) \frac{dI_2}{dt}$$

$$\frac{dI_2}{dt} = \frac{V(h_1 - M)}{h_1 h_2 - M^2} - \textcircled{4}$$

Sub  $\textcircled{4}$  in  $\textcircled{3}$

$$\frac{dI_1}{dt} = V - M \times \frac{V(h_1 - M)}{h_1 h_2 - M^2}$$

$h_1$

$$= \frac{V(h_1 h_2 - M^2) - M V h_1 + M^2 V}{h_1 (h_1 h_2 - M^2)}$$

$$= \frac{V h_1 h_2 - V M^2 - M V h_1 + M^2 V}{h_1 (h_1 h_2 - M^2)}$$

$$= \frac{N B_1 (L_2 - M)}{4\pi (L_1 L_2 - M^2)}$$

$$\cdot \frac{dI_1}{dt} = \frac{N (L_2 - M)}{L_1 L_2 - M^2}$$

$$\therefore \frac{dI}{dt} = \frac{dI_1}{dt} + \frac{dI_2}{dt}$$

$$= \frac{N (L_2 - M)}{L_1 L_2 - M^2} + \frac{N (L_1 - M)}{L_1 L_2 - M^2}$$

$$\frac{dI}{dt} = \frac{N (L_1 + L_2 - 2M)}{L_1 L_2 - M^2}$$

$$N = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \frac{dI}{dt}$$

$$N = L_p \frac{dI}{dt}$$

$$L_p = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

Effective inductance when 2 coils are connected in parallel.

- Q) Two coupled coils connected in series have an equivalent inductance of 0.725H, when aiding and 0.425H when opposing. Find self and mutual inductance when  $K = 0.42$ .

Ans)  $L' = 0.725H ; L'' = 0.425H$

$$K = 0.42$$

$$\frac{M}{\sqrt{h_1 h_2}} = 0.42$$

$$0.725 = h_1 + h_2 + 2M \quad -①$$

$$0.425 = h_1 + h_2 - 2M \quad -②$$

$$① + ②$$

$$0.575 = h_1 + h_2 \quad - ③$$

$$② - ①$$

$$0.03 = 2M$$

$$M = 0.015$$

$\therefore$  Sub  $M = 0.015$  and ③ in K

$$0.42 = 0.015$$

$$\sqrt{(0.575 - h_2) h_2}$$

$$h_2^2 - 0.575 h_2 + 0.03188 = 0$$

$$\begin{aligned} D &= b^2 - 4ac = \sqrt{(-0.575)^2 + 4(1)(0.03188)} \\ &= \sqrt{0.203055} = 0.4506 \end{aligned}$$

$$h_2 = -b \pm D$$

$$2a$$

$$h_2 = -(-0.575) + 0.4506 ; h_2 = 0.575 - 0.4506$$


$$\therefore \text{when } h_2 = 0.5126 ; h_1 = 0.0624$$

$$\text{and when } h_2 = 0.0624 ; h_1 = 0.5126$$

$$M = 0.015$$

## Alternating e.m.f.

### Production of alternating e.m.f.

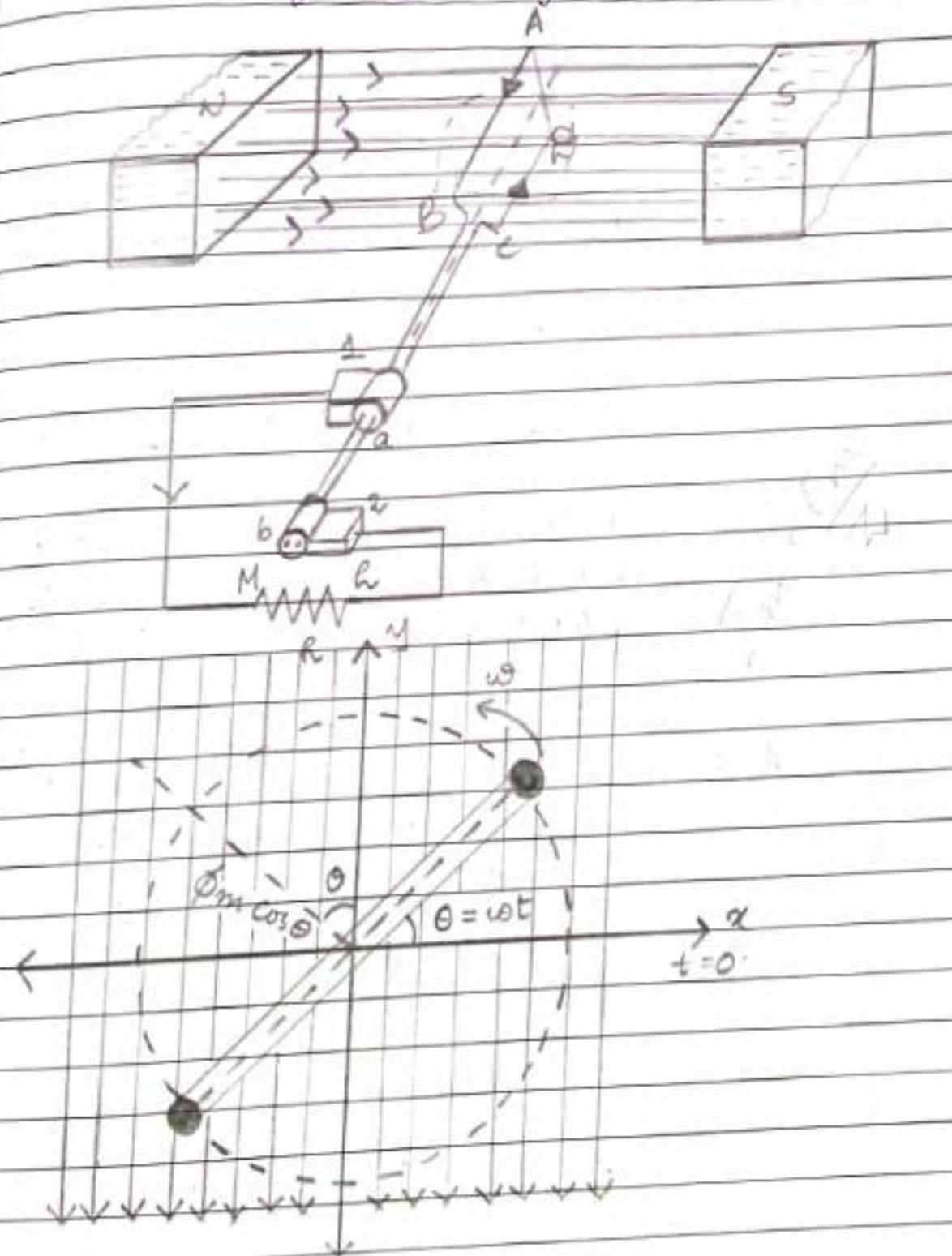

$$\theta = \omega t - \theta_0$$

$$\phi = \phi_m \cos \omega t$$

$$N\phi = N\phi_m \cos \theta$$

{ from ① }

$$e = - \frac{d(N\phi)}{dt}$$

$$= - \frac{d(N\phi_m \cos \theta)}{dt}$$

$$= - N \frac{d(\phi_m \cos \theta)}{dt}$$

$$= - N\phi_m \omega (-\sin \theta) \text{ volt}$$

$$= N\phi_m \sin \omega t$$

$$e = N\phi_m \sin \omega t \text{ volt} \quad - ②$$

$$E_m = \omega \phi_m$$

$$= \omega N B_m A$$

$$= 2\pi f N B_m A \text{ volt} \quad - ③$$

$$\left. \begin{array}{l} \omega = 2\pi f \\ \phi_m = B_m A \end{array} \right\}$$

$$\left. \begin{array}{l} \omega = 2\pi f \\ \phi_m = B_m A \end{array} \right\}$$

$B_m$ : maximum flux density in  $\text{Wb/m}^2$

$A$ : area of the coil in  $\text{m}^2$

$f$ : frequency of rotation of the coil in  $\text{rev/second.}$

∴ from ② & ③



$$e = E_m \sin \omega t$$

$$e = E_m \sin \omega t \quad \{ \text{from ②} \}$$

My,

$$i = I_m \sin \omega t$$
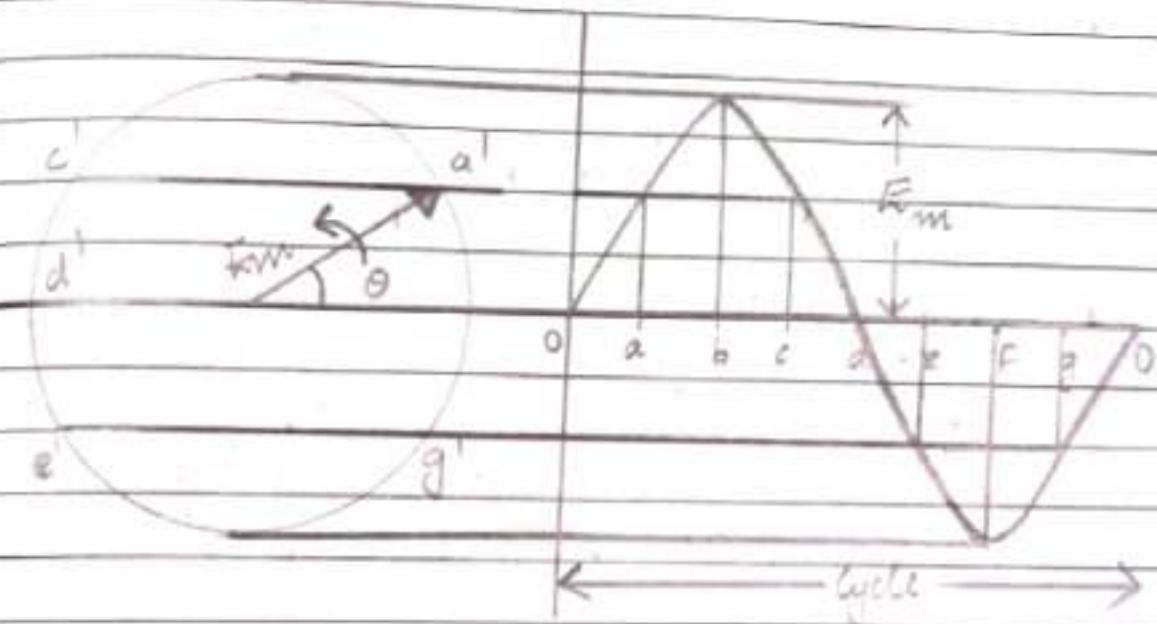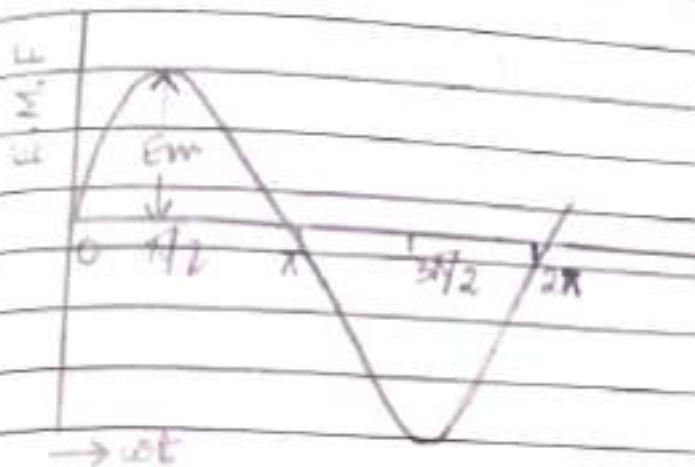
$$\left. \begin{array}{l} I_m = \bar{I}_m \\ z \end{array} \right\}$$



### Cycle

One complete set of positive and negative values of alternating quantity is known as cycle.

One complete cycle is said to spread over  $360^\circ$  or  $2\pi$

### Time period

The time taken by an alternating

quantity to complete one cycle is called its time period. ( $T$ )

e.g. 50 Hz alternating current has a time period of  $\frac{1}{50}$  seconds.

- \* frequency

- \* The number of cycles/second is known as frequency.

- \* unit hertz ;  $f = \frac{1}{T}$

- \* amplitude

- \* The maximum value, positive or negative, of an alternating quantity is known as amplitude.

- \* Instantaneous value

- $\text{It is the value at a particular instant.}$

- \* Average value

- $\text{It is the arithmetic mean of the ordinates at equal interval over a half cycle of a wave.}$

Methods :

1) Mid-ordinate method : Graphical method  
2) Analytical method.

Mid-ordinate method

Analytical method

$$\text{avg. Area} = \frac{1}{\pi} \int_0^{\pi} i^2 dt \quad i = I_m \sin \omega t$$

RMS Value (Root mean square value)

RMS Value is that value of DC current which when flows through a given conductor produces same amount of heat as that produced by the alternating current passing through the same conductor for the same time.

$$i = I_m \sin \omega t$$
$$I_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} i^2 dt}$$

$$\text{RMS value of sine wave} = \frac{I_m}{\sqrt{2}}$$

$$\text{Average value of sine wave} = \frac{\omega I_m}{\pi}$$

\* Form Factor

$$\text{Form factor} = \frac{\text{RMS value}}{\text{Avg value}}$$

\* Peak factor

$$\text{Peak factor} = \frac{\text{Max. value}}{\text{RMS value}}$$

\* Form factor of sine wave =  $\frac{I_m/\sqrt{2}}{\omega I_m/\pi}$

$$= \frac{\pi}{2\sqrt{2}}$$

$$= 1.11$$

\* Peak factor of sine wave =  $\frac{I_m}{I_m/\sqrt{2}}$

$$= \frac{1}{\sqrt{2}}$$

# Module : 3

## Phasors


4 types of phasors are:

- 1) Rectangular form
- 2) Trigonometric form
- 3) Exponential form
- 4) Polar form

$j = \sqrt{-1}$ ,  $j$  is an operator. It is used to express the  $90^\circ$  operation in counter clockwise direction.


### Rectangular Form

$$\cdot v = x + jy$$

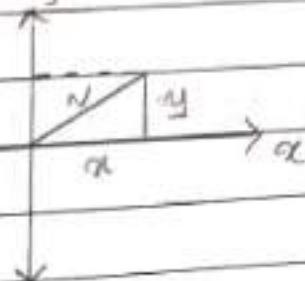

{j = i · F1}

### Trigonometric form

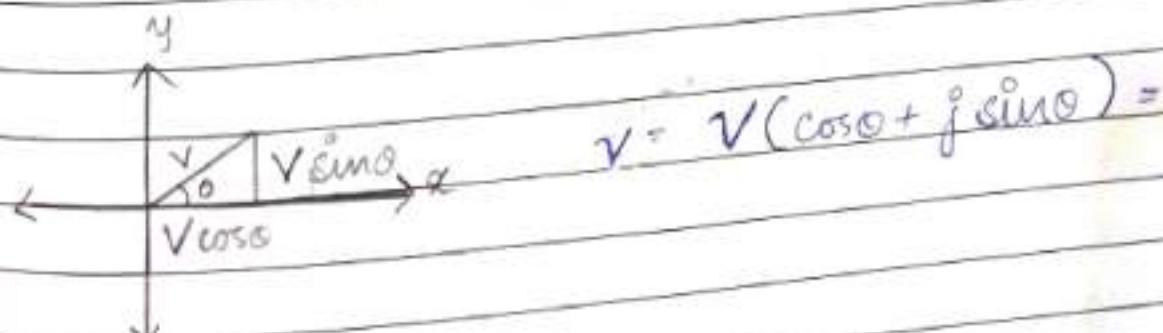

$$v = V(\cos\theta + j\sin\theta) =$$

→ Exponential Form ( $e^{j\theta}$ )

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$e^{-j\theta} = \cos\theta - j\sin\theta$$

$$V = V e^{-j\theta}$$

→ Polar Form

$$V = V \angle \theta$$

{ $\theta$  - angle of}

→ Addition & Subtraction

(most suitable for rectangular form)

$$V_1 = x_1 + jy_1$$

$$V_2 = x_2 + jy_2$$

$$V_1 + V_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$V_1 - V_2 = (x_1 - x_2) + j(y_1 - y_2)$$


→ Multiplication and division (polar form)

$$V_1 = V_1 \angle \theta_1$$

$$V_2 = V_2 \angle \theta_2$$

$$V_1 \cdot V_2 = V_1 V_2 \angle (\theta_1 + \theta_2)$$
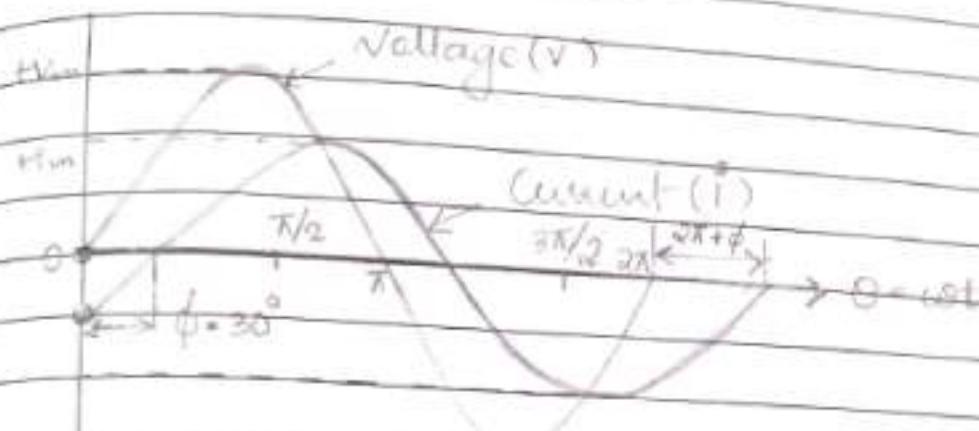
$$\frac{V_1}{V_2} = \frac{V_1}{V_2} \angle (\theta_1 - \theta_2)$$




{out of phase?}

$$v = V_m \sin(\omega t)$$

reference wave

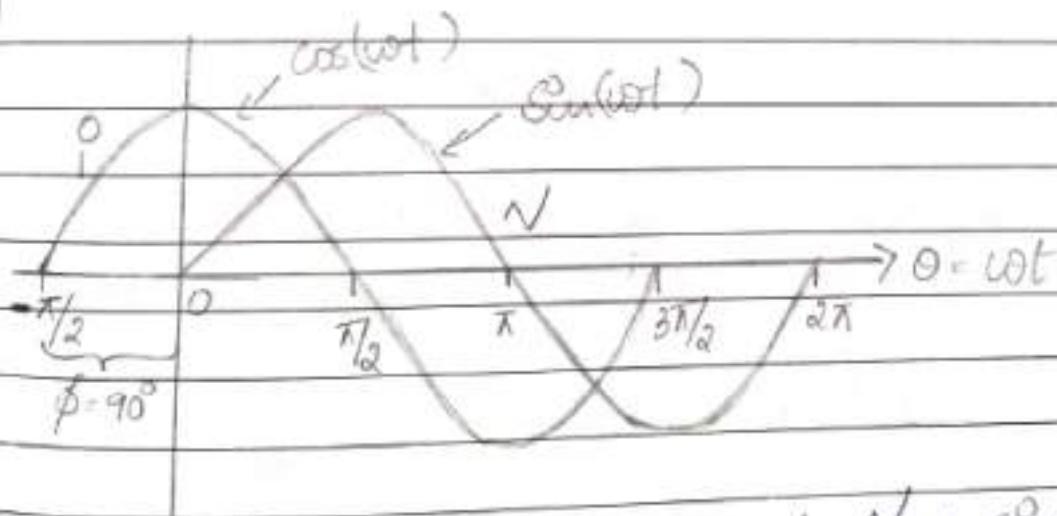i.  $I_m \sin(\omega t - \phi)$   
lagging by  $\phi$  degree



$$v = V_m \cos(\omega t)$$

reference wave

q.  $I_m \sin(\omega t + \phi)$   
leading wave  
leading by  $\phi$  degree

DC Circuit with resistance only



$$v = V_m \sin \omega t$$

$$- V_m \sin(\omega t)$$

$$\sqrt{I^2 R}$$

$$V_m \sin(\omega t) - I^2 R$$

$$I^2 = \frac{V_m \sin(\omega t)}{R}$$

$$\therefore I_m = \frac{V_m}{R}$$

$$(I = I_m \sin(\omega t))$$

Instantaneous power,

$$P = VI$$

$$= V_m I_m \sin^2(\omega t)$$

$$= V_m I_m (1 - \cos 2\omega t)$$

$$= V_m^2 I_m^2 - V_m^2 I_m^2 \cos^2(\omega t)$$

$$P = V_m I_m \sin^2(\omega t)$$

$$I = I_m \sin(\omega t)$$


Power consist of a constant part:

$$\Rightarrow V_m^2 I_m^2$$

and a fluctuating part:

$$\Rightarrow V_m^2 I_m^2 \cos^2(\omega t)$$

frequency is double that of voltage

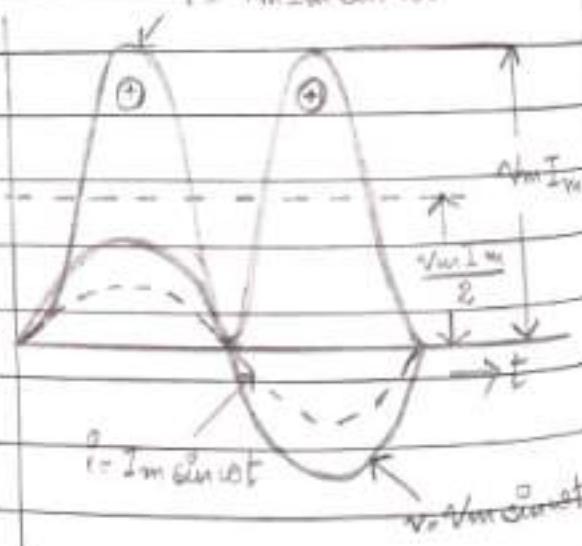

in current waves.

Hence, power for the whole cycle is

$$P = \frac{V_m I_m}{2} = \frac{V_m \times I_m}{\sqrt{2} \sqrt{2}}$$

$$\text{or } P = V \times I \text{ (Wt)}$$

where,

$V$  = rms value of applied voltage.

$I$  = rms value of the current.

AC through Pure Inductive Circuit

$$v = L \frac{di}{dt}$$

$$\text{Now, } v = V_m \sin(\omega t)$$

$$\therefore V_m \sin(\omega t) = L \frac{di}{dt}$$

$$\therefore di = \frac{V_m \sin(\omega t)}{L} dt$$


Integrating both sides  
we get,

$$i = \frac{V_m}{L} \int \sin(\omega t) dt$$

$$= \frac{V_m}{L} \cos \omega t$$

$$\therefore P = \frac{V_m}{L} \sin^2 \left( \omega t - \frac{\pi}{2} \right)$$

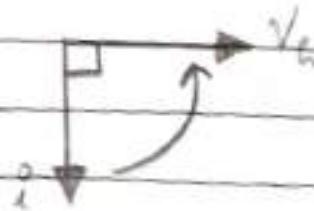
$$= \frac{V_m}{L} \sin^2 \left( \omega t - \frac{\pi}{2} \right)$$



Max value of  $i$  is  $I_m = \frac{V_m}{j\omega R}$  (when)

$\sin(\omega t - \frac{\pi}{2})$  is unity)
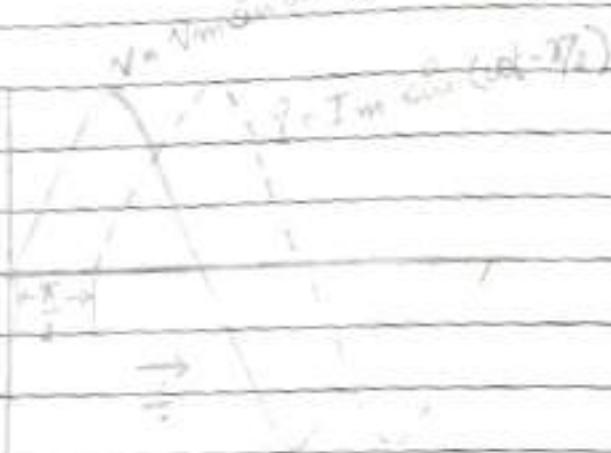
$$i = I_m \sin(\omega t - \frac{\pi}{2})$$



### Power


$$\text{Instantaneous power} = N_i = V_m I_m \sin \omega t \sin \left( \omega t - \frac{\pi}{2} \right)$$

$$= V_m I_m \sin(\omega t) \cos(\omega t)$$

$$= \frac{V_m I_m}{2} \sin(2\omega t)$$

$$\text{Power for whole cycle is } P = \frac{V_m I_m}{2} \int_0^{2\pi} \sin^2 \omega t dt = 0$$

Power wave

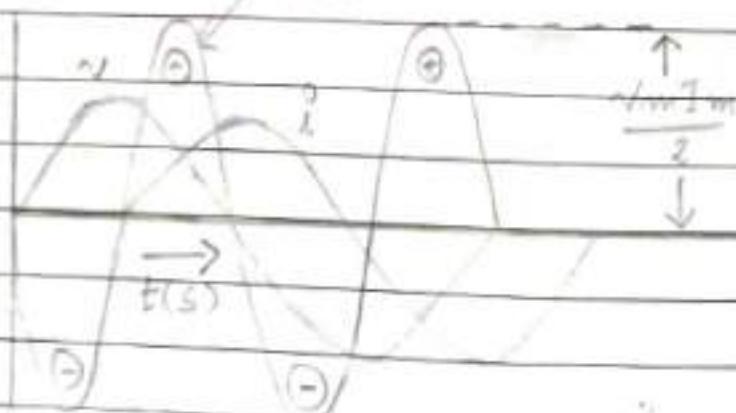

# AC through Pure Capacitive Circuit

- v = p.d developed between plates at any instant.
- charge on plates
- at that instant

$$q = Cv \quad \left\{ \begin{array}{l} \text{where } C \text{ is } \\ \text{the capacitance} \end{array} \right\}$$

$$= C V_m \sin(\omega t) \quad \left\{ \begin{array}{l} \text{sub } v = V_m \sin(\omega t) \\ \text{v = } V_m \sin(\omega t) \end{array} \right\}$$

current  $i$  is given by the rate of flow of charge.

$$\therefore i = \frac{dq}{dt}$$

$$= \frac{d(C V_m \sin \omega t)}{dt}$$

$$= C V_m \omega \cos \omega t \text{ or } I$$


$$I = \frac{V_m \sin(\omega t + \frac{\pi}{2})}{1/C\omega}$$

$$I_m = \frac{V_m}{1/C\omega} = \frac{V_m}{X_C}$$


$$q = I_m \sin(\omega t + \frac{\pi}{2})$$

$$P = VI$$


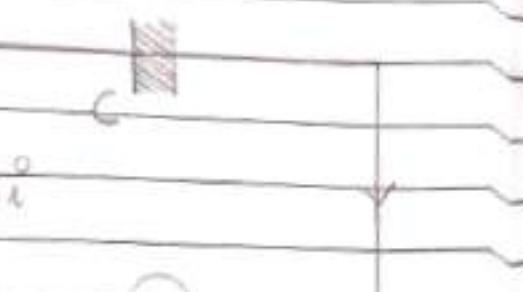
$$= V_m \sin(\omega t) \cdot I_m \sin(\omega t + \frac{\pi}{2})$$



$$V = V_m \sin(\omega t)$$

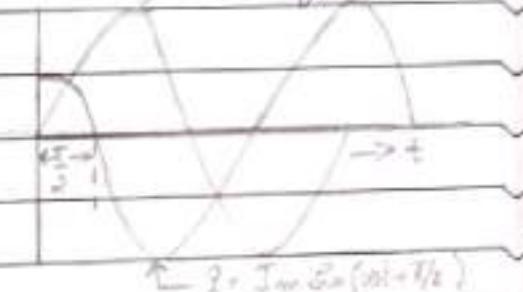
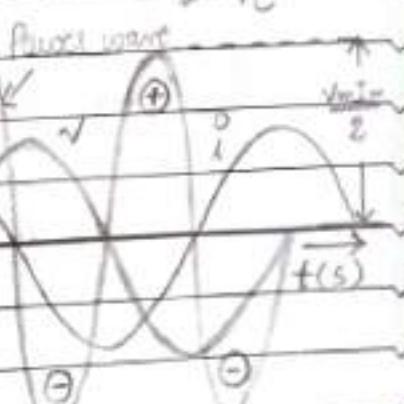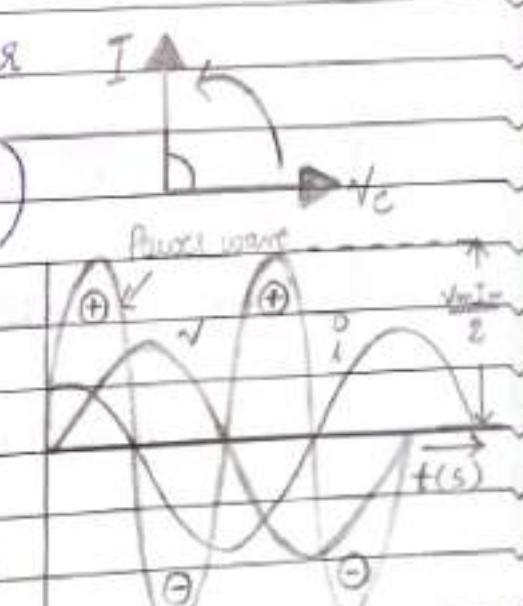
$$I = I_m \sin(\omega t + \frac{\pi}{2})$$



$V_m I_m \sin \omega t$

-  $V_m I_m \sin \omega t$

Power for the whole cycle

$$= V_m I_m \int_0^{\pi} \sin^2 \omega t dt$$

$$= 0$$


AC through RL circuit

$$V = \sqrt{V_R^2 + V_L^2}$$

$$= \sqrt{(I R)^2 + (I \cdot X_L)^2}$$

$$= I \sqrt{R^2 + X_L^2}$$

$$I = \frac{V}{\sqrt{R^2 + X_L^2}}$$

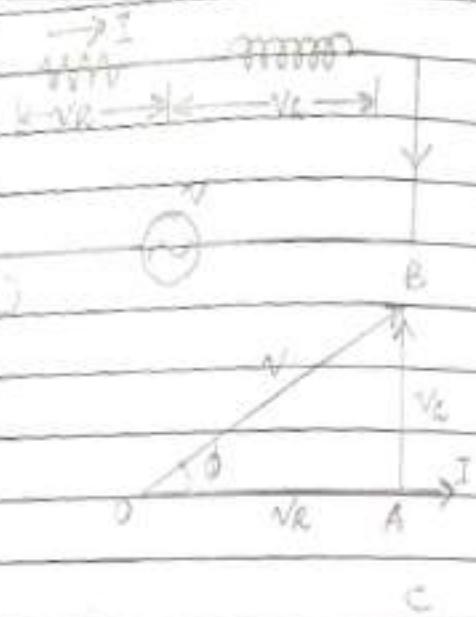

The quantity  $\sqrt{R^2 + (X_L)^2}$

is known as the

impedance ( $Z$ ) of the


circuit.

$$Z^2 = R^2 + X_L^2$$

the applied voltage  $V$

leads current  $I$  by

an angle  $\phi$  such that

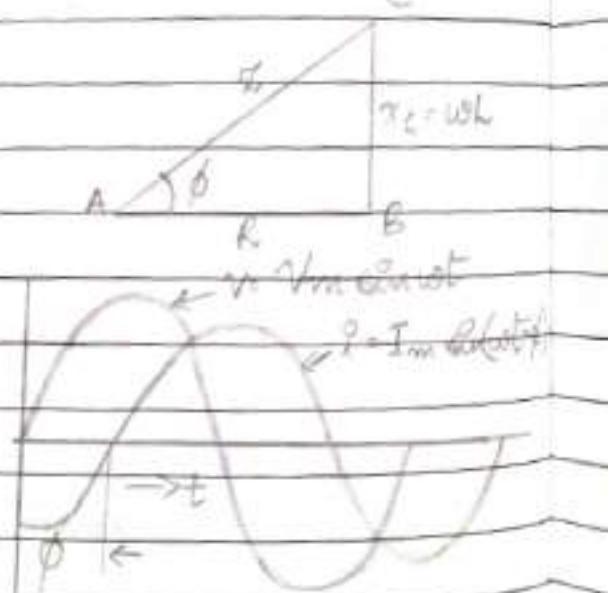

$$\begin{aligned}\tan \phi - \frac{V_R}{V_R} &= \frac{I \cdot X_L}{I \cdot R} \\ &= \frac{X_L}{R} \\ &= \frac{\omega L}{R}\end{aligned}$$

Reactance  
Resistance

$$\phi = \tan^{-1} \frac{X_L}{R}$$

I has been resolved into its two mutually perpendicular components,  $I \cos \phi$  along the applied voltage  $V$  and  $I \sin \phi$  in quadrature.

The mean power consumed by the circuit is given by the product of  $V$  and that component of the current  $I$  which is in phase with  $V$ .

$$\begin{aligned}P &= V \times I \cos \phi \\ &= \text{rms voltage} \times \text{rms current} \times \cos \phi\end{aligned}$$

Q-factor of a coil

$$\text{Q-factor} = \frac{1}{\text{power factor}}$$

$$= \frac{1}{\cos \phi} = \frac{Z}{R}$$

$$Q = \frac{1}{\cos \phi} = \frac{Z}{R}$$

$Q = 2\pi \times \frac{\text{maximum energy stored}}{\text{energy dissipated per cycle}}$

## Power Factors

cosine of the angle of lead or lag

The ratio  $\frac{R}{Z}$  • resistance  
impedance

$$\text{The ratio } \frac{\text{true power}}{\text{apparent power}} = \frac{\text{watts}}{\text{volt-amperes}} = \frac{W}{VA}$$

## Active and Reactive Components of Circuit Current I

- Active component is that which is in phase with the applied voltage  $V$  i.e  $I \cos\phi$ .
  - It is also known as 'wattful' component.
  - Reactive component is that which is quadrature with  $V$  i.e  $I \sin\phi$
  - It is also known as 'wattless' or 'idle' component.

## Active, Reactive and apparent Power.

- ## Apparent power (s)

It is given by the product of a.m.s values of applied voltage and circuit

current.

$$S = VI$$

$$= (IZ) \cdot I$$

$$S = (IZ) \cdot I = I^2 Z \text{ volt-amperes (VA)}$$

active power (P or W)

Active component which is obtained by multiplying kVA by  $\cos\phi$  and this gives power P in kW.

$$P = I^2 R$$

$$= VI \cos\phi \text{ watts.}$$

Reactive power (Q)

The reactive component known as reactive kVA and is obtained by multiplying kVA by  $\sin\phi$ .

It is written as kVAR (kilo VAR)

$$Q = I^2 X_C$$

$$= I^2 \times Z \sin\phi$$

$$= I \times (IZ) \sin\phi$$


$$= VI \sin\phi \text{ volt-amperes-reactive (VAR)}$$

d.c through RC series circuit

$$V = \sqrt{V_R^2 + (-V_C)^2}$$

$$= \sqrt{(IR)^2 + (-IX_C)^2}$$

$$= I \sqrt{R^2 + X_C^2}$$

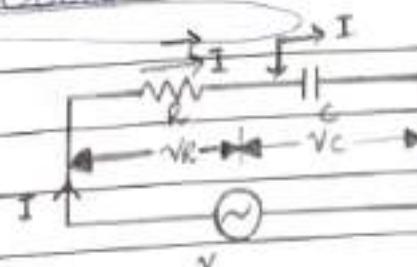


$$I = \frac{V}{\sqrt{R^2 + X_C^2}}$$

$$= \frac{V}{Z}$$

$$Z = \sqrt{R^2 + X_C^2}$$

Current leads voltage by  $\phi$

$$\tan \phi = -\frac{X_C}{R}$$

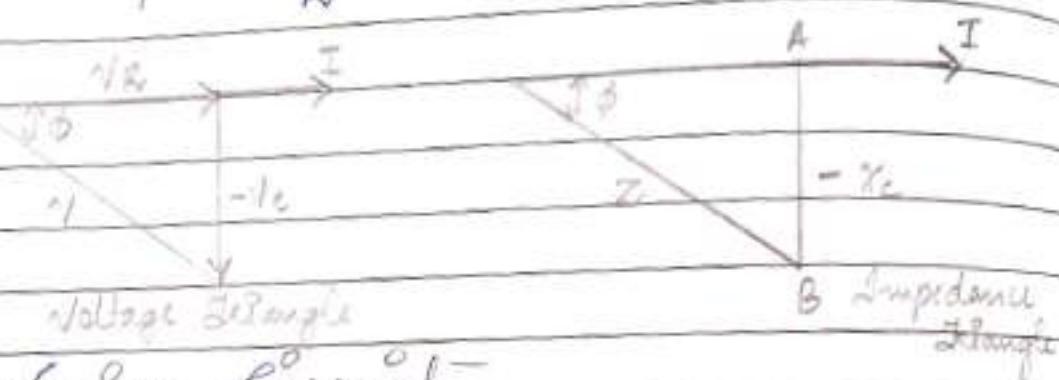


### R.L.C Series Circuit

$V_R = IR$  - voltage drop across  $R$  - in phase with  $I$

$V_L = I \cdot X_L$  - voltage drop across  $L$  - leading  $I$  by  $\frac{\pi}{2}$

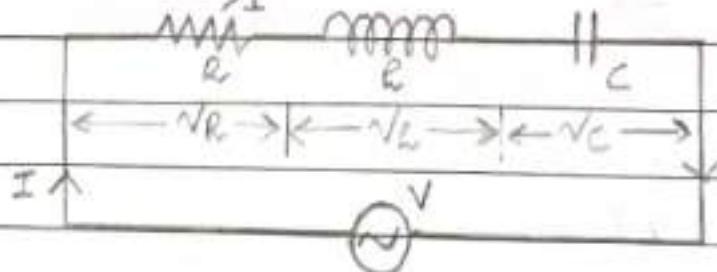$V_C = I \cdot X_C$  - voltage drop across  $C$  - lagging  $I$  by  $\frac{\pi}{2}$



$$OQ = \sqrt{OA^2 + AD^2}$$

or


$$V = \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

$$= I \sqrt{R^2 + (X_L - X_C)^2}$$

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$= \frac{V}{\sqrt{R^2 + X^2}} = \frac{V}{Z}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

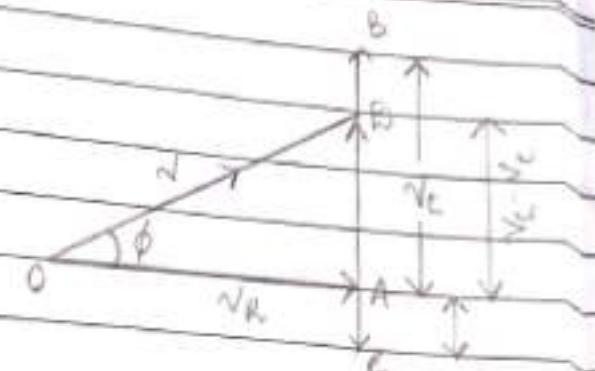

(Impedance)<sup>2</sup> = (Resistance)<sup>2</sup> + (net reactance)<sup>2</sup>

$$Z^2 = R^2 + (X_L - X_C)^2$$

$$Z = \sqrt{R^2 + X^2}$$

phase angle  $\phi$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$= \frac{X}{R}$$

- net reactance  
resistance

Power factor is  $\cos \phi = \frac{R}{Z}$

$$= \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$= \frac{R}{\sqrt{R^2 + X^2}}$$

resulting current in an R-L-C circuit is given by  $I = I_m \sin(\omega t \pm \phi)$

The +ve sign is to be used when current

leads i.e.  $x_L > x_C$

The -ve sign is to be used when current lags i.e. when  $x_L > x_C$ .

Symbolic notation :  $Z = R + j(x_L - x_C)$

$$Z = \sqrt{R^2 + (x_L - x_C)^2}$$

If phase angle is  $\phi = \tan^{-1} \left[ \frac{x_L - x_C}{R} \right]$

$$Z = Z \left[ \tan^{-1} \left[ \frac{x_L - x_C}{R} \right] \right]$$

$$\cdot Z \left[ \tan^{-1} \left[ x/L \right] \right]$$

if  $V = V_{L0}$

$$\text{then } I = \frac{V}{Z}$$

### Summary of Results of Series AC Circuits

Type of impedance	Value of impedance	phase angle for current	Power factor
Resistance only	R	0°	1
Inductance only	jwL	90° lag	0
Capacitance only	1/jwC	90° lead	0
Resistance and Inductance	$\sqrt{R^2 + (wL)^2}$	$0 < \phi < 90^\circ$ lag	$1 > p.f > 0$
Resistance & Capacitance	$\sqrt{R^2 + (-1/wC)^2}$	$0 < \phi < 90^\circ$ lead	$1 > p.f > 0$
R, L, C	$\sqrt{R^2 + (wL - 1/wC)^2}$	btw 0° $90^\circ$ lag or lead	b/w 0 and unity lag or lead

# Three Phase System


comparison between polyphase system  
and single phase system

Poly phase system	single phase system
Power generation is cheaper.	Power generation is costly.
High pf of efficiency	Low pf of efficiency
Uses less material for a given capacity.	Uses more material.
Apparatus are economical.	Apparatus are costly.
Polyphase motors have uniform torque.	Pulsating torque
Parallel operation is very smooth.	Not smooth.
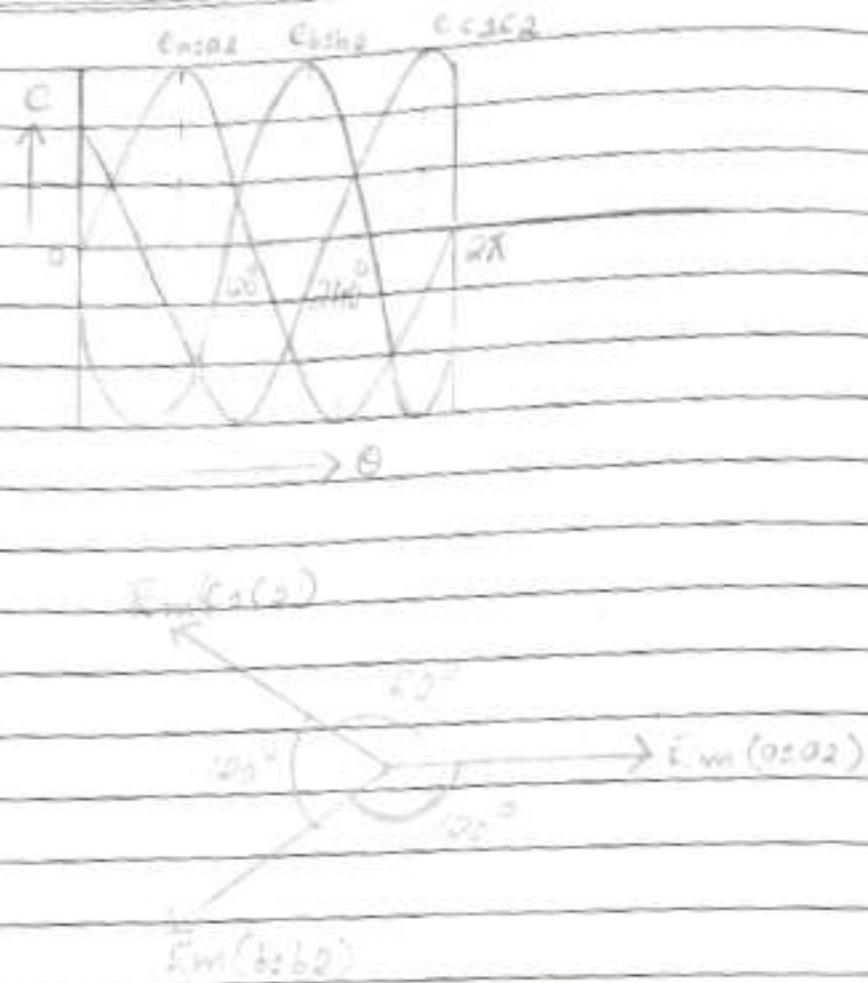
## Production of Three Phase voltage




- E<sub>1</sub> = E<sub>m</sub> sin Θ
- E<sub>2</sub> = E<sub>m</sub> sin (Θ - 120)
- E<sub>3</sub> = E<sub>m</sub> sin (Θ - 240)



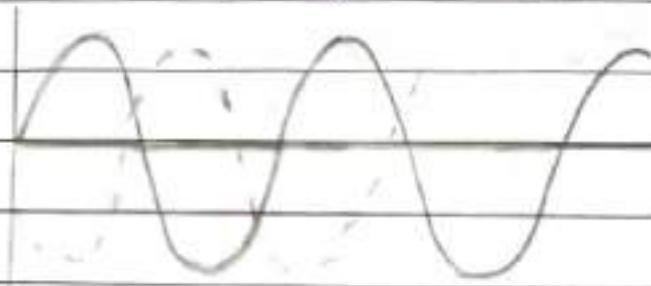
## Phase Sequence or phase order

- phase sequence is meant the order in which the three phases attain their peak or maximum positive values.
- The phase sequence can be reversed by interchanging any pair of lines.




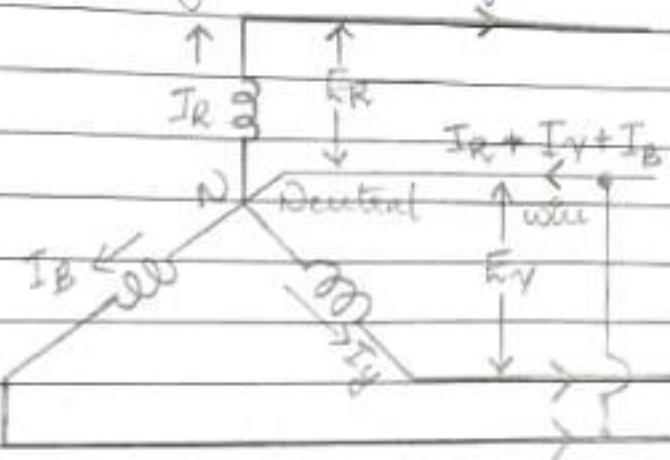
## Star Connected System

The similar ends 'start' ends of three coils (it could be 'finishing' ends also) are joined together at point N.



## Phase Voltage and line voltage

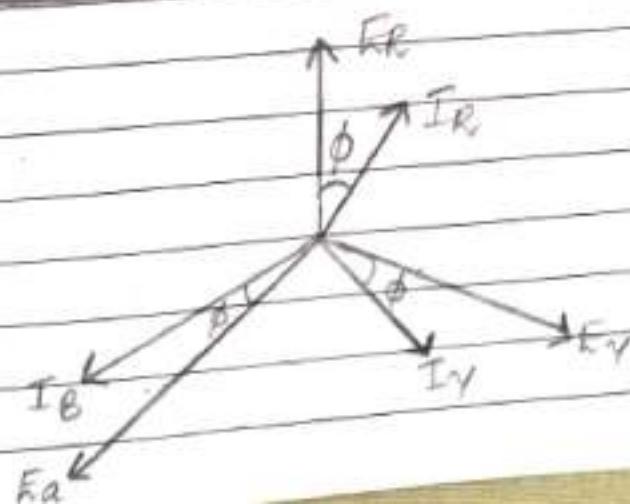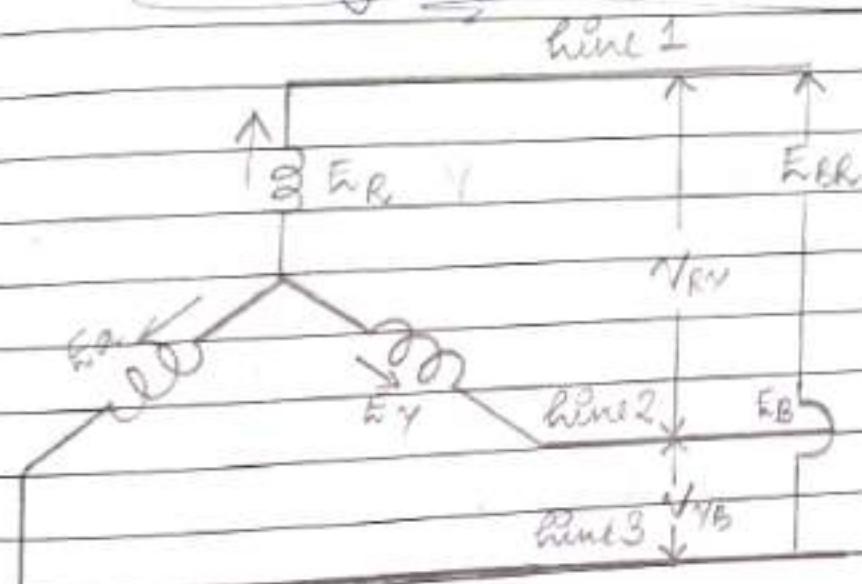

If  $E_R = E_Y - E_B$   
let  $E_{ph}$  be the phase e.m.f.,

$$V_{RY} = \sqrt{3} \cdot E_{ph} \times \cos(60^\circ)$$

$$= \sqrt{3} \cdot E_{ph} \times \cos 30^\circ$$

$$= \sqrt{3} \cdot E_{ph} \times \frac{\sqrt{3}}{2}$$

$$= \sqrt{3} \cdot E_{ph}$$

Similarly,

$$V_{YB} = E_Y - E_B$$

$$= \sqrt{3} \cdot E_{ph}$$
 factor difference?

$$\text{if } V_{BR} = E_B - E_R \\ = \sqrt{3} \cdot E_{ph}$$


where  $V_{RY}$ ,  $V_{YB}$ ,  $V_{BR}$  are line voltages,  
generally represented as  $V_a$

Hence star connection.

$$V_a = \sqrt{3} \cdot E_{ph}$$


Note:

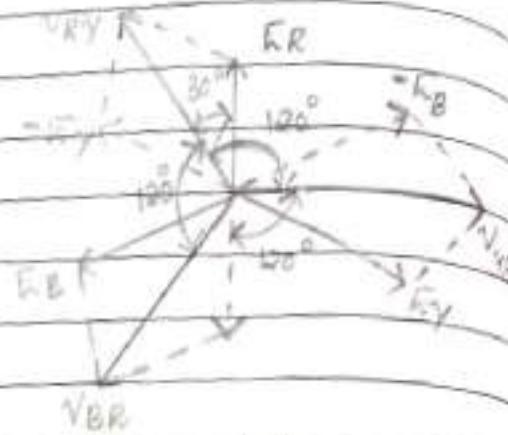- Line voltages are  $120^\circ$  apart.
- Line voltages are  $30^\circ$  ahead of their respective phase voltages.
- The angle between the line currents and the corresponding line voltages is



$(30 + \phi)$  with current lagging.

line currents and phase currents

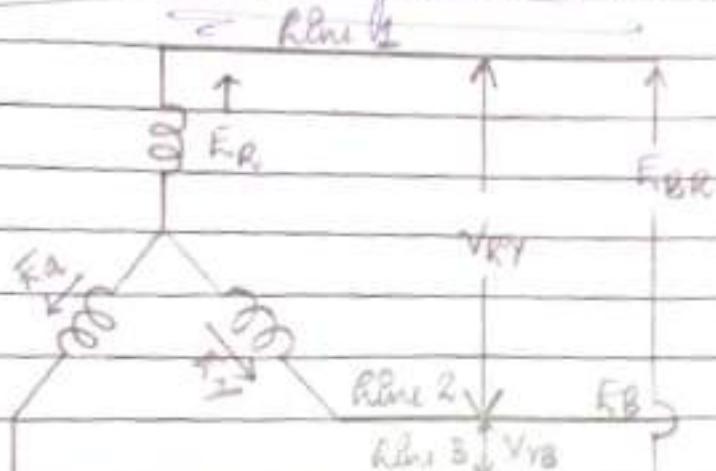

each line is in series with its individual phase winding, hence the line current in each line is the same as the current in the phase winding to which the line is connected.

Current in line 1 =  $I_R$

Current in line 2 =  $I_Y$

Current in line 3 =  $I_B$

Since  $I_R = I_Y = I_B$

Assume,  $I_{ph}$  be the phase current

$\therefore$  line current  $I_A = I_{ph}$

Power

The total active or true power in the circuit is the sum of the three phase powers. Hence, total active power = 3-phase power,

## Module - 1

### \* Gas Discharge Tubes :

#### Disadvantages :

- Higher response time.
- Lower discharge capacity.
- Lower lifespan.

### \* Vacuum Tubes :

#### Disadvantages :

- Bulky, hence less suitable for portable products.
- Higher operating voltages generally required.
- High power consumption ; needs heater supply that generates waste heat and yields low efficiency, notably for small-signal circuits.

\* After the development of vacuum tubes, electronics has gone through 3 major stages of development.

• Stage 1 : 1920 - 1950 Vacuum tubes ruled the world of electronics.

• Stage 2 : 1950 - 1960 Invention of Transistors

• Stage 3 : 1960 - present Invention of Integrated Circuits

### \* Transistors :

- Electrons flow through solid instead of vacuum - Solid State Devices.

- Semiconductor Device.
- Initially made of Germanium.
- Silicon almost entirely replaced Germanium
  - Easily available
  - Available in sand and rock.

#### Disadvantages:

- Cost is high
- Low performance.

#### \* Integrated circuits (IC chips):

##### Advantages:

- Extremely small in size.
- Low power consumption.
- Reliability
- Reduced cost
- Very small weight
- Easy replacement.

- \* It contains 100s or 1000s of transistors.

#### \* Nanoelectronics:

- Nanotechnology
- Special attention to transistors.
- Design is different from traditional transistors.

##### Limitations:

- High cost.
- Cannot be used for heavy loads.

- Different fields in nanoelectronics
- Nanofabrication
  - To design arrays or layers of nanoelectronic devices.
- Nanomaterials electronics
  - Dielectric property - high  
Dielectric s. If it is an electrical insulator than can be polarized by an applied electric field.
  - Electron or hole characteristics - high.
- Moore's law: The law states that the number of transistors in a dense integrated circuit doubles about every two years.
- Josephson Effect: Flow of electric current between two pieces of superconducting material separated by a thin layer of insulating material.
- Superconductivity: Below a certain temperature, materials enter a superconducting state and offer no resistance to the passage of electrical current.
- Quantum mechanic property: Science dealing with the behaviour of matter and light on the atomic and subatomic scale. These properties include the interactions of the particles with one

another and with electromagnetic radiation.  
(i.e. light, X-rays, and gamma rays).

- Nanolithography

It is the science of etching, writing or printing to modify a material surface with structures under 100 nm.

- Applications of Nanoelectronics

- Nanoradio
- Nanocomputers.

- Energy production

- Solar cells
- Bio-mano generators - work like a fuel cell.  
(converting glucose into energy artificially)

- Applications

- Entertainment and Communication
- Control and Instrumentation
- Applications in medical science
- applications in defence

- Electronic Components

- Resistor
- passive element : elements which do not generate power.


- Unit: ohm, kilo ohm, mega ohm

- ⇒ mega ohm is used for very high resistances.  
eg. insulation, earth resistance etc.
- ⇒ Device used to measure very high resistance is known as megger.

### \* Specifications of resistor

- Resistance value
- Tolerance (error): permissible plus or minus resistance deviation.
- Wattage rating (max power): Maximum power in Watts.
- Voltage rating:  $\frac{V^2}{R} = P$ ;  $V = \sqrt{P \cdot R}$
- Temperature coefficient of resistance: Ratio of change of nominal resistance as a function of temperature.
- Nominal resistance: The average of the minimum and the maximum allowed values.

### \* Colour coding of Resistor

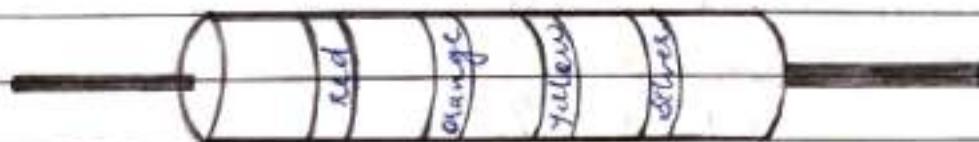

1<sup>st</sup> digit  
2<sup>nd</sup> digit  
multiplier  
Tolerance

→ Gold: 5%  
Silver: 10%  
None: 20%

color	Digit	Multiples	Tolerance (%)
Black	0	$10^0$	(1)
Brown	1	$10^1$	1
Red	2	$10^2$	2
Orange	3	$10^3$	
Yellow	4	$10^4$	
Green	5	$10^5$	0.5
Blue	6	$10^6$	0.25
Violet	7	$10^7$	0.1
Grey	8	$10^8$	
White	9	$10^9$	
Gold		$10^{-1}$	5
Silver		$10^{-2}$	10
(none)			20

Q1) Find the resistance from the following colour combination:

1) red, red, yellow, gold.

$$22 \times 10^4 \pm 5\%$$

2) blue green orange silver

$$65 \times 10^3 \pm 10\%$$

3) black violet green

$$7 \times 10^5 \pm 20\%$$

\* Fixed Resistors

## Wire-Wound Resistors

- a ceramic - core wound with a drawn wire having accuracy - controlled characteristics.
- Coils are made of alloys of copper and chromium.
- Materials must have high thermal stability, tensile strength and capacity to withstand high temperature.
- Insulating material used is nylon or baked enamel - Coated with entire wire.
- Exit - terminals are made of Cu.
- The material should have high resistance and resistivity.
- The winding should be perfect.

## Advantages

- Can withstand large power.
- Used in high temperature situation
- Carries very high current
- Can withstand mechanical shock and vibration.
- Can be used in high voltage circuits.

- \* Disadvantages
- Not suitable for high frequency applications.
- Cost is high.
- Large size and weight.

### Carbon Composition Resistors

- \* Two types of construction :
  - Slug : Carbon granules are mixed with an organic binder and molded into a pellet-shape around the terminal leads.
  - Second type : Carbon resistive material is deposited on a glass tube attached to the terminal leads by a conductive cement.
- A thick organic resin case ~~is~~ is molded around the assembly.

### Advantages :

- Small in size
- Cheap
- Wide resistance range

### Disadvantages :

- Not useful for above 5W applications
- Resistance vary with aging
- Resistors easily get heated.

- \* Carbon Film Resistors

- \* Depositing very thin film of carbon on to a substrate by vacuum sputtering.

→ vacuum sputtering :

- \* Thin and thick film resistors.

- \* Advantages

- \* Available for all resistive values
- \* Good frequency properties
- \* Available in every miniature size
- \* Can replace wire wound resistors in high voltage applications.

- \* Disadvantages

- \* Cannot withstand high temp.
- \* Chemically reactive and unstable.
- \* Have higher inherent inductance.

- \* Variable resistors

- \* Volume control type Potentiometer :

- \* Made of carbon
- \* long handle.

- \* Advantages

- Size is comparatively small
- Low weight
- Wide resistance range

- \* Timmer Potentiometer

- Shorter trimmer
- Central moving arm is spring loaded.

- \* Advantages

- Small size and weight
- Low cost
- Available for all resistance values.

- \* Rheostat

- Wire wound type

- \* Advantages

- Large current carrying capacity.
- Capable of handling high voltages
- Rheostats are precision resistors with low tolerance.

- \* Disadvantages

- Costly
- Bulky, weight is more

- \* Maintenance required - wires can easily be broken.

- \* Harmonics

A harmonics of such a wave is a wave with a frequency that is a positive integer multiple of the frequency of the original wave, known as the fundamental frequency. The original wave is called the 1<sup>st</sup> harmonic, the following harmonics are known as higher harmonics.

- \* Capacitor

A capacitor is a device that stores electrical energy in an electric field. It is a passive electronic component with two terminals. The effect of a capacitor is known as capacitance.

- Fixed capacitor
- Variable capacitor

- \* Capacitance

Capacitance is the ratio of the amount of electric charge stored on a conductor to a difference in electric potential. There are two closely related notions of capacitance.

- That are:
- Self Capacitance
- Mutual Capacitance

any object that can be electrically charged exhibits self capacitance.

- SI unit is Farad (F)  
Practical capacitors are in microfarads or pico-farads

### \* Fixed Capacitor

- Capacitance doesn't vary with external factors.
- Capacitor that stores fixed amount of electric charge.
- There are 4 types of fixed capacitors
- Paper capacitors
- Mica capacitors
- Ceramic capacitors
- Electrolytic capacitors

### \* Paper Capacitors

- Paper capacitor is a capacitor that uses paper as the dielectric to store electric charge.
- Muscle or cellulose paper called craft-paper
- Craft-paper is sandwiched between 2 aluminum foils.
- The entire unit is rolled to form a cylinder.
- The paper sheet is covered or soaked with oil or wax to protect from outside harmful environment.

- Used in the high voltage and high current applications.

### \* Mica Capacitors

- Mica is used as dielectric material.
- Muscovite mica is most frequently used for constructing the dielectric of mica capacitors.
- It consists of plates of aluminium foil separated by sheet of mica.

### \* Advantages

- Good mechanical strength.
- Can be used for high temperature.
- High voltage and high frequency applications.
- High insulation resistance.

### \* Disadvantages

- Chance of unavailability
- Silver migration occurs at high Dc voltages, high temperature and high humidity.

### \* Ceramic Capacitors

- Ceramic materials is used to construct the dielectric and conductive metals are used to construct the electrodes.
- Ceramic disc is coated on 2 sides with a metal, such as Cu or Ag.
- Lined wire is placed as leads.

- The entire unit is coated with plastic and marked with capacitor value.

#### \* Advantages

- Wide range of capacitance
- Cheap
- Light weight
- Highly reliable

#### \* Disadvantages

- High voltage capacitors are not available.
- High capacitors are not available.  
(capacitors)

#### \* Electrolytic capacitors

- Consists of aluminium foil electrode which has an aluminium oxide film covering on one side.
- Aluminium plate serves as positive plate. aluminium oxide acts as dielectric.

#### \* Advantages

- High capacity in small volume.
- lower cost per microfarad.

#### \* Disadvantages

- large leakage resistance
- Will work only in DC.

## \* Variable Capacitors

- Used for tuning
- Air gang capacitor
- Deimmer capacitor.

## \* Tantalum capacitors

- Another type of electrolytic capacitors.
- Tantalum is used instead of aluminium.
- Larger C in small size.
- Less leakage current.

## \* Inductors

- Long wires wound on insulating former.
- Fixed and Variable.

### \* Fixed


- Give constant inductance.
- No of turns do not change.

### \* Variabiles


- Inductance can be changed over a specified range.
- Inductance varied by changing the position of core.
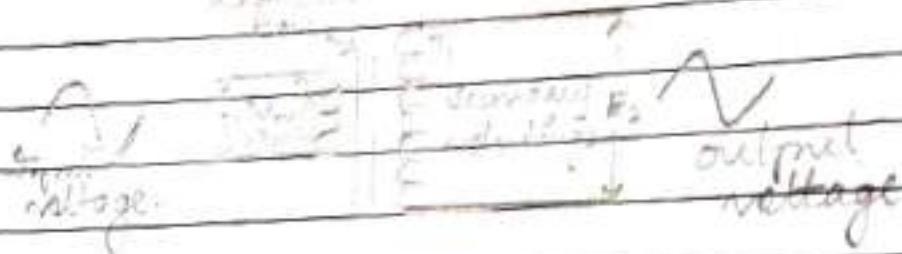
## \* Transformers

- Two inductors having same core.
- One is primary, the other is secondary.
- It transforms one or more electrical parameters from one circuit to another.
- There are 2 types of transformers &
- > Step up transformer
- > Step down transformer
- Step up transformer



- Step down transformer

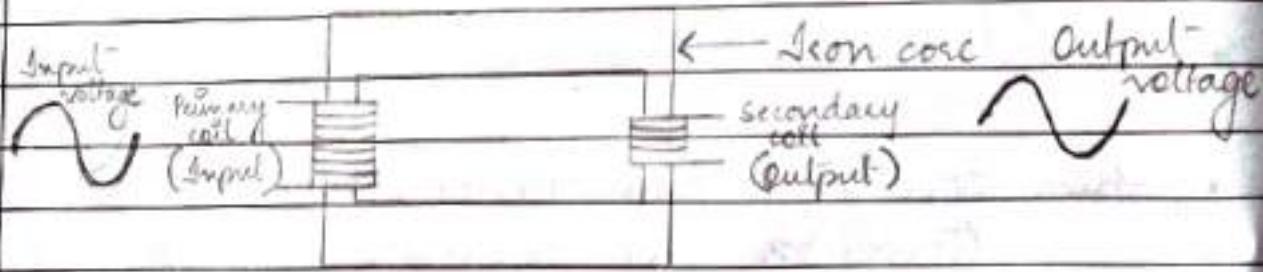

## ★ Classification of Transformers

- Based on their current-capacity and frequency range:

- > Power Transformers.
- > Audio frequency Transformers
- > Impedance Transformers
- > Pulse Transformers.

## \* Power transformers

- Operating frequency 50 Hz or 60 Hz.
- Handle large powers.

## \* Audio Frequency Transformers

- Transform electrical signals in audio frequency range.
- Application: Audio Amplifier.

## \* Impedance Transformers

- Transform impedance level.
- Transform the output impedance of one circuit in such a way that it matches input impedance of another circuit.

## \* Pulse Transformers

- Transform pulses.
- Transform pulses may have change in amplitude or polarity.
- Uses

- ⇒ Pulse generating circuit
- ⇒ Pulse amplifiers.

- Small leakage current and capacitance.
- $K$  greater than 99%.


## Semiconductors

- Energy band diagram
- Energy band : The range of energies possessed by electrons in a solid.
- Valence band :
  - Electrons have least binding energy, more orbital energy.
  - The range of energy possessed by valence electrons called valence band.
- Conduction band :
  - When certain energy applied to valence electrons, they will become conduction electrons.
  - The range of energy possessed by free electrons is called conduction band.
- Forbidden band or gap :
  - The separation between valence and conduct band in energy band diagram.
  - The energy required to lift the electron from valence to conduction band should


be greater than the energy gap  $E_g$

## \* Classification of materials


### • According to energy band diagram

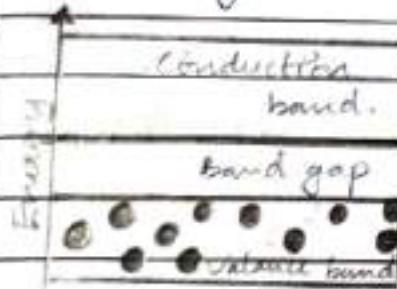

Insulator

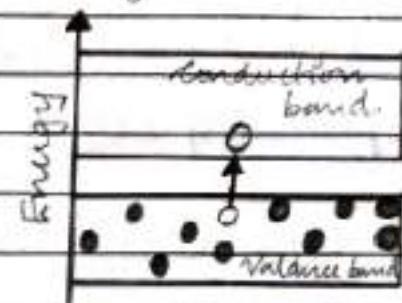

Semiconductor

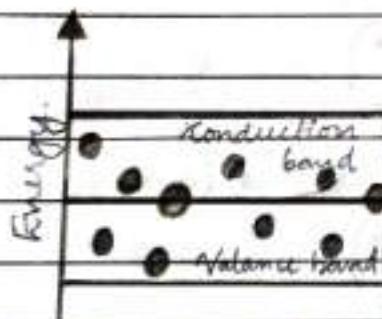


Conductor

## \* Classification of Semiconductors
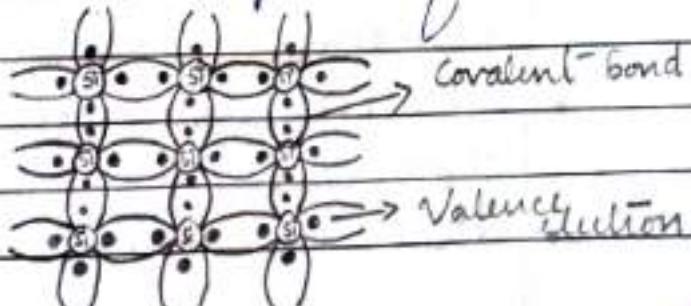
### • Intrinsic Semiconductors:

• Pure form of semiconductor.

• Impurity should be less than one part in - purity in 100 million ( $1/10^8$ ) parts of semiconductors.




## \* Extrinsic Semiconductor

- Impure form of semiconductor.
- Doping


- Conduction of semiconductor material is improved by doping.
- Doped by pentavalent atom - donor doping
- Doped by trivalent atom - acceptor doping

## \* N-type Semiconductor

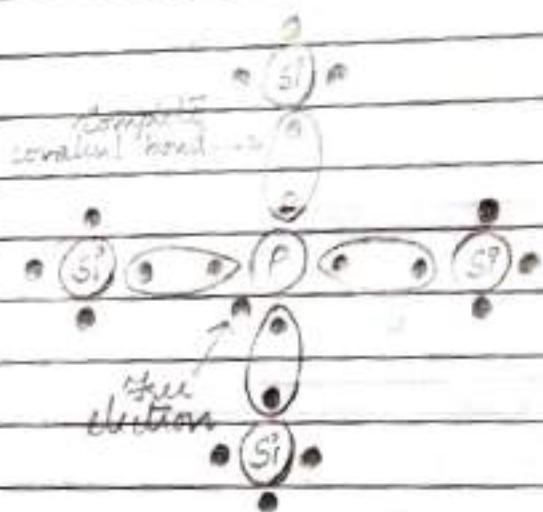

- The pentavalent atoms are As, P, Bi and Sb.
- These materials include five electrons in their outer shell.
- The four electrons will make covalent bonds using the adjacent atoms and the fifth electron will be accessible like a valence carrier.
- Electrons are the majority carriers in N-type semiconductor.
- Holes are minority carriers.


## \* P-type Semiconductors

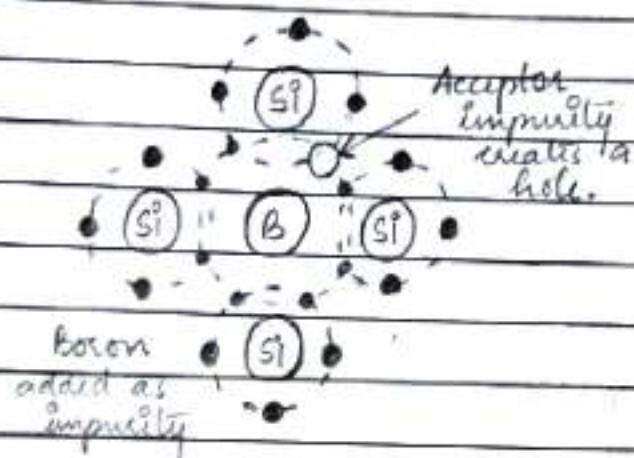

- When a trivalent impurity is added to a pure semiconductor a large number of holes are created in it.
- Trivalent impurities are boron, aluminium, thallium, gallium and indium.
- Major current carriers are holes.
- Minor current carriers are electrons.
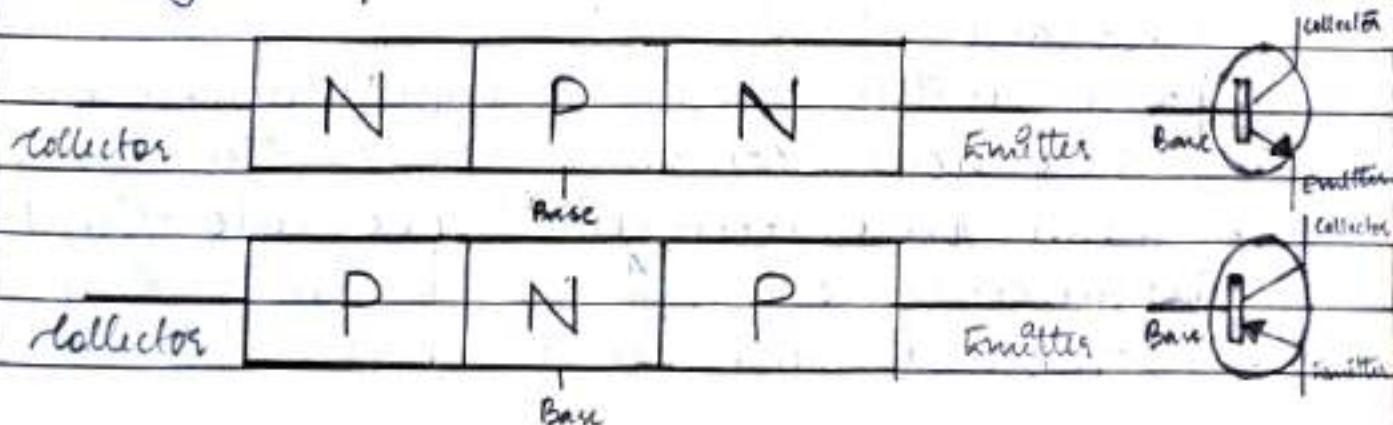
## \* Bipolar Junction Transistors (BJT)

- 3 doped semiconductor regions - Emitter, base, collector - provided with terminals.
- 2 pn junctions
- Base emitter junction and base collector
- Npn or pnp.



### \* Emitter

- Heavily doped
- Supply majority carriers to the base
- Always forward biased with respect to base.


### \* Base

- lightly doped
- very thin

### \* Collector

- Moderately doped
- Always reverse biased with respect to base.

### \* Working of PNP Transistor

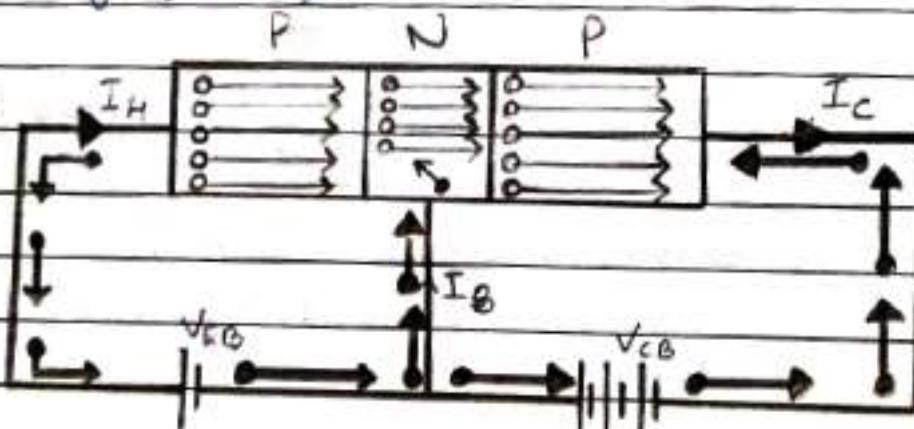

- The emitter-base junction is connected in forward bias.
- The emitter push the holes in the base region.
- These holes constitute the emitter current.
- When these electrons <sup>holes</sup> move into the N-type semiconductor material or base, they get combined with the electrons.

- The collector base region is connected in reverse biased.
- The holes which collect around the depletion region when coming under the impact of negative polarity collected or attracted by the collector. This develops the collector current.

### \* Working of NPN transistor




- The transistor in which one p-type material is placed between two n-type materials is known as NPN transistor.
- The NPN transistor amplifies the weak signal enter into the base and produces strong amplify signals at the collector end.
- In NPN transistor, the direction of movement of an electron is from the emitter to collector region due to which the current constitutes in the transistor.
- Such type of transistor is mostly used in the circuit because their majority charge carriers are electrons which have high mobility as compared to holes.
- The forward biased voltage  $V_{BE}$  is applied across the emitter-base junction, and the reversed biased voltage is applied across the collector-

base junction.

- The forward bias voltage  $V_{BE}$  is small as compared to the reverse bias voltage  $V_{CE}$ .
- When the forward bias is applied across the emitter, the majority charge carriers move towards the base.
- This causes the emitter current  $I_E$ . The electrons enter into the P-type material and combine with the holes.
- The base of the NPN transistor is lightly doped.
- Due to which only a few electrons are combined and remaining constitutes the base current  $I_B$ .
- This base current enters into the collector region. The reversed bias potential of the collector region applies the high attractive force on the electrons reaching collector junction.
- Thus attract or collect the electrons at the collector.
- The whole of the emitter current is entered into the base. Thus, we can say that the emitter current is the sum of the collector & the base current.
- Transistor Configurations
- Common Base Configuration

Emitter Base Collector

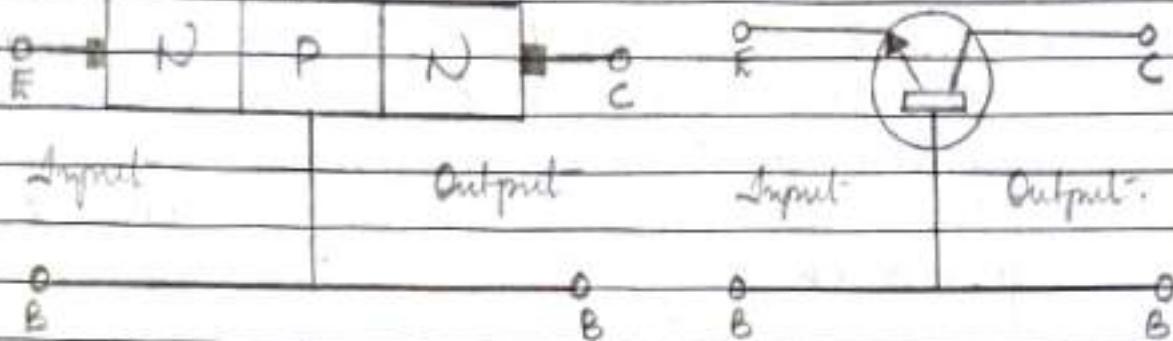

- The input is applied between the base and emitter terminals and the corresponding output signal is taken between the base and collector terminals with the base terminal grounded.
- The input parameters are  $V_{EB}$  and  $I_E$  and the output parameters are  $V_{CB}$  and  $I_C$ .
- The input current flowing into the emitter terminal must be higher than the base current and collector current to operate the transistor.

$$\text{current gain} = \frac{\text{output current}}{\text{input current}} = \frac{I_C}{I_E}$$

$\alpha$  is the common base current gain.  
It is also known as amplification factor.  
Its value is less than 1 (around 0.98).

$$\text{Voltage gain} = \frac{\text{output voltage}}{\text{input voltage}} = \frac{V_{CB}}{V_{EB}}$$

therefore the output collector current is less than the input emitter current.

- The current gain is equal or less than unity.

- In CB configuration, a positive input produces a positive output and hence input and output are in phase. So, there is no phase reversal between input and output in a CB amplifier.
- If CB configuration is considered for amplification, it has low input impedance and high output impedance.
- The input and output signals are in-phase in this configuration.
- The amplifier circuit configuration of this type is called as non-inverting amplifier circuit.
- The construction of this configuration circuit is difficult because this type has high voltage gain values.

### Characteristics

#### Input characteristics:

Between Input current ( $I_E$ ) and Input voltage ( $V_{EB}$ ) for different output voltage.


#### Output characteristics:

Between output current ( $I_C$ ) and output voltage ( $V_{CB}$ ) for different input currents.


# Input Characteristics

papergrid


Date: / /

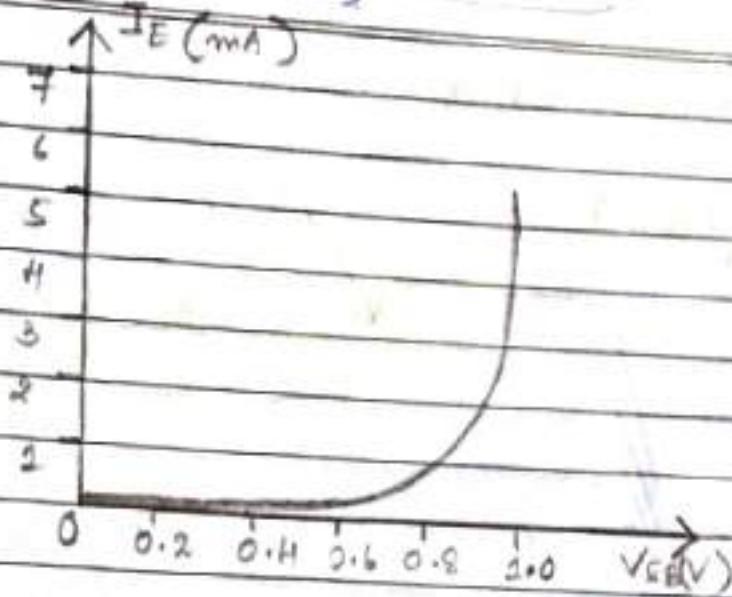

## Early Effect (Base width modulation)

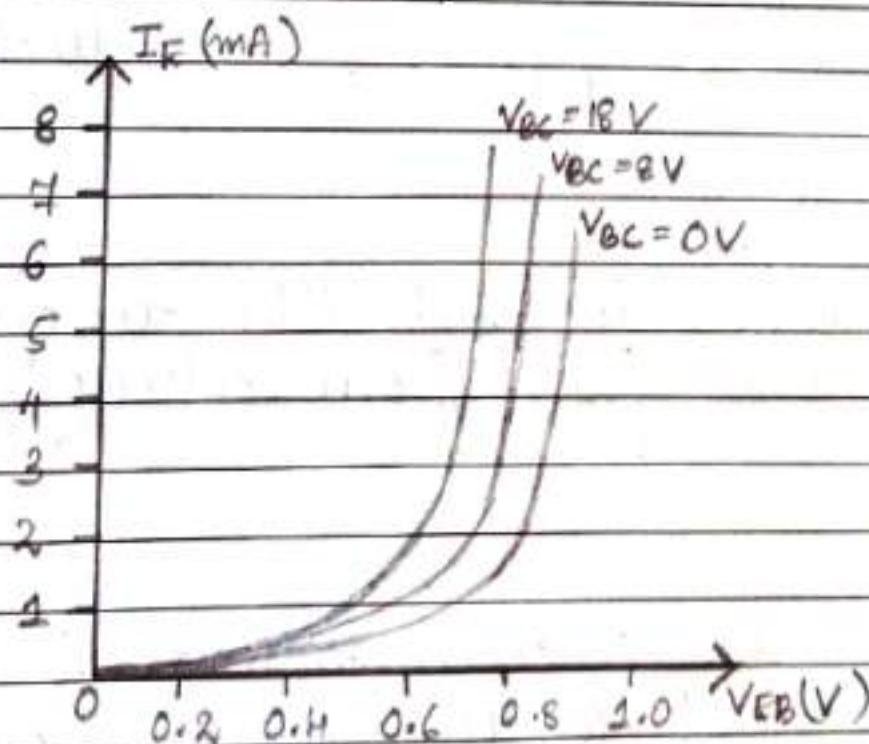

## Output Characteristics

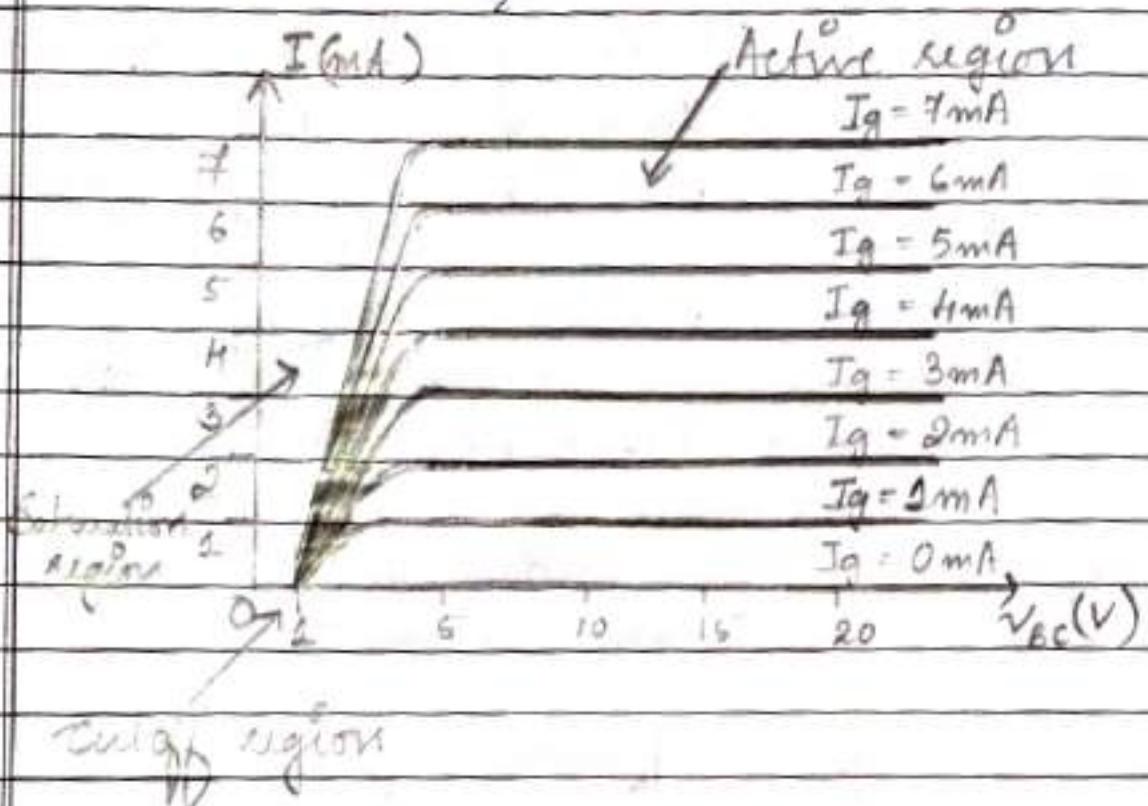

### Saturation :

The transistor acts like a short circuit.  
Current freely flows from collector to emitter.


### Cut-off :

The transistor acts like an open circuit.  
No current flows from collector to emitter.

### Active :

The current from collector to emitter is proportional to the current flowing into the base.

## Common Emitter Configuration

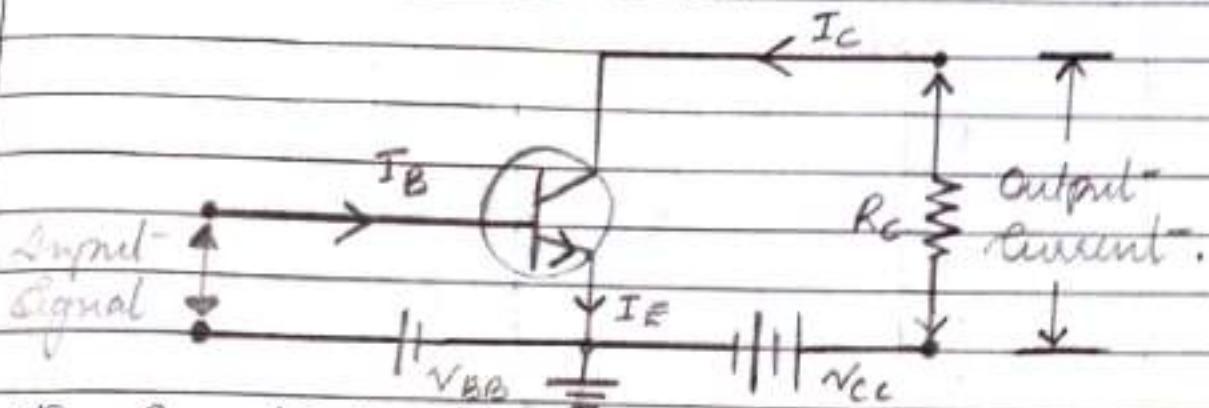

- \* The input circuit is connected between emitter and base, and the output circuit is taken from the collector and emitter.

### Common Emitter Current Gain ( $\beta$ )

Base current amplification factor is defined as the ratio of the output current and input current in a common emitter configuration.

$$\beta = \frac{I_C}{I_B} \quad \text{--- (1)}$$

$$\alpha = \frac{I_C}{I_E} \quad \text{--- (2)}$$

$$\begin{cases} I_E = I_B + I_C \\ I_B = I_E - I_C \end{cases}$$

From (1) & (2),

$$\beta = \frac{I_C}{I_E - I_C}$$

$$\frac{1}{\beta} = \frac{I_E - I_C}{I_C} \quad \text{--- (3)}$$


$$\frac{1}{\beta} = \frac{1}{\alpha} - 1$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

## Input Characteristics




## Output Characteristics

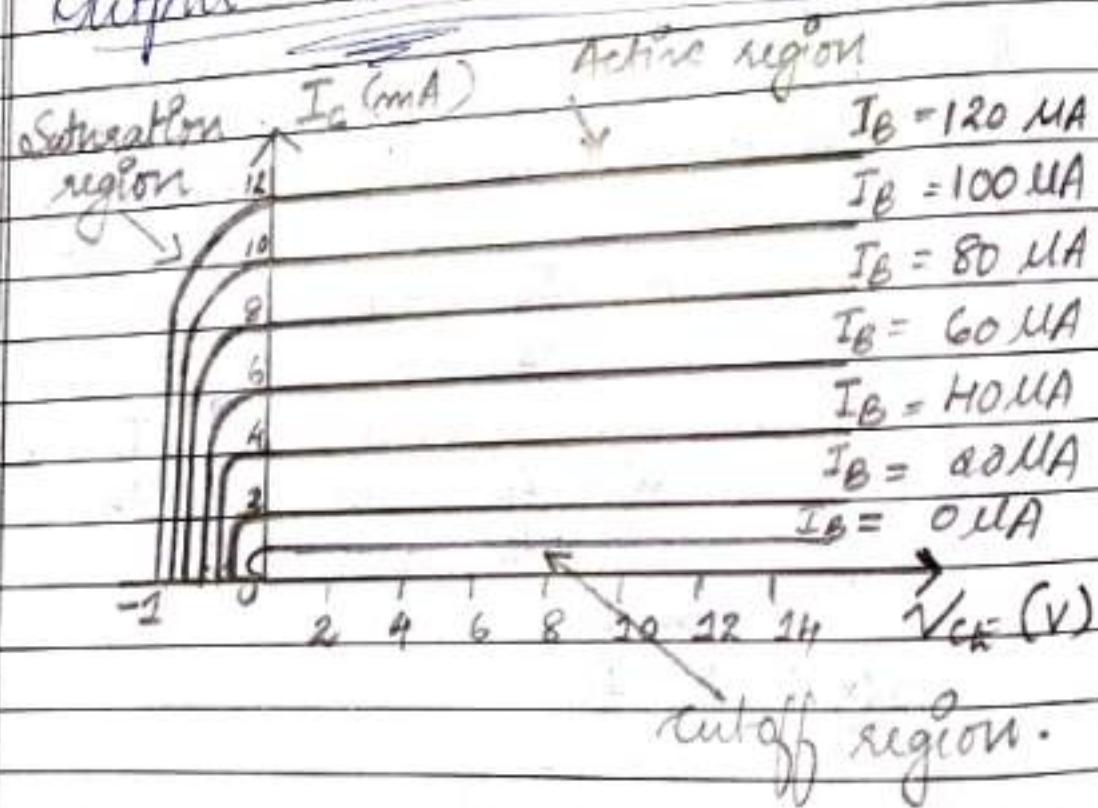

## Common Collector Configuration

- Input circuit is connected between emitter and base and the output is

taken from the collector and emitter.

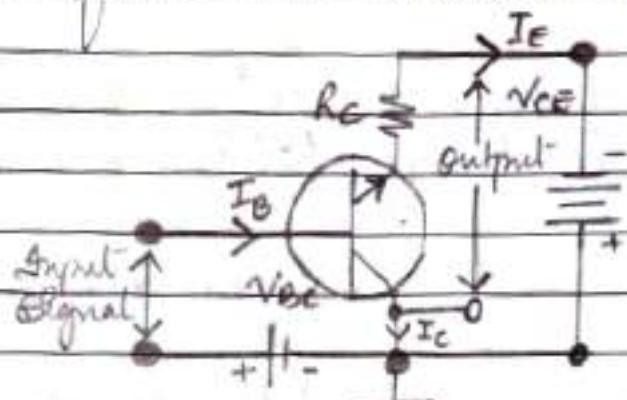


Current Gain

$$\gamma = \frac{I_E}{I_B}$$


$$I_B = I_E - I_C$$

$$\gamma = \frac{1}{1-\alpha}$$

Input Characteristics

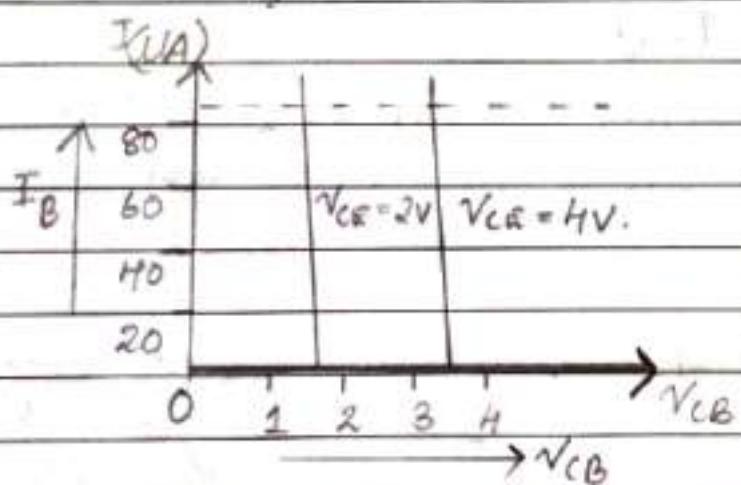

Output Characteristics


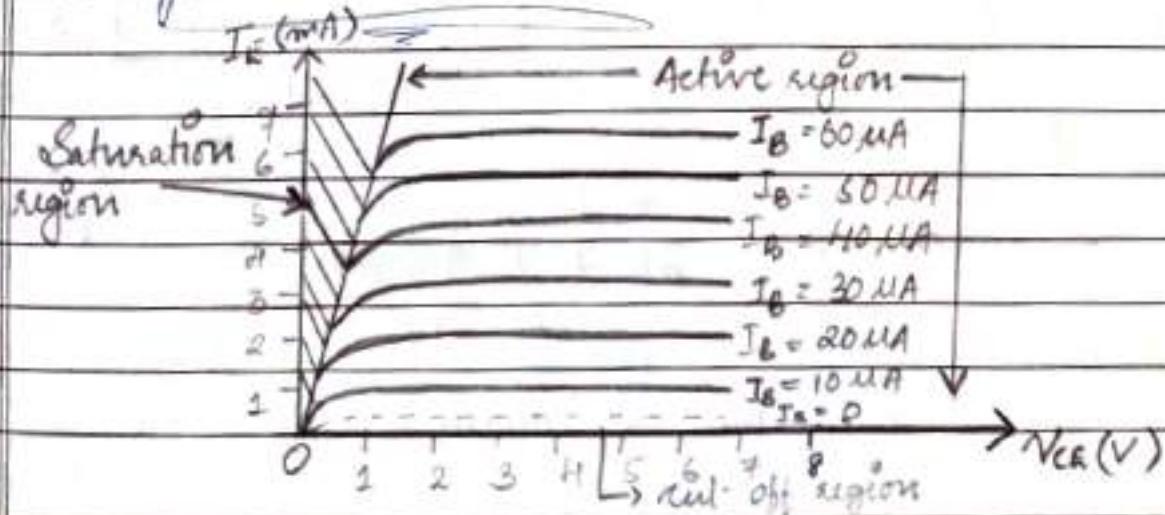



Module 5Basic Electronic Circuits and  
Instrumentation\* Rectifiers:

A rectifier is an electrical device that converts alternating current, which periodically reverses direction, to direct current, which flows in only one direction. The reverse operation is performed by the inverter. The process is known as rectification.

\* Power Supply

A power supply is an electrical device that supplies electric power to an electrical load.

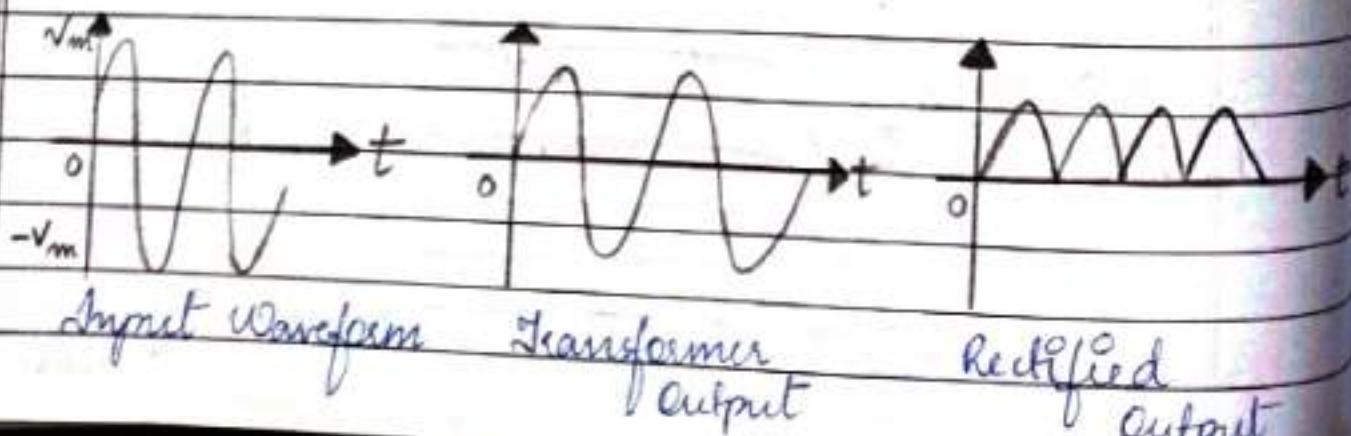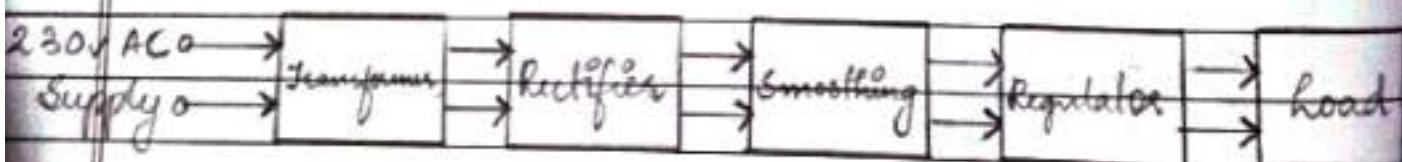
\* Block Diagram of DC Power Supply

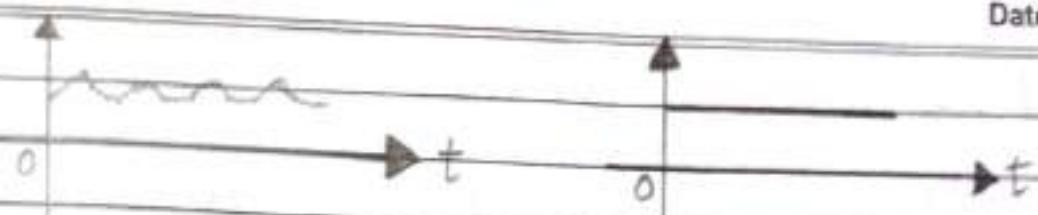


Filtred Output

Pure dc output


### \* Half wave Rectifier

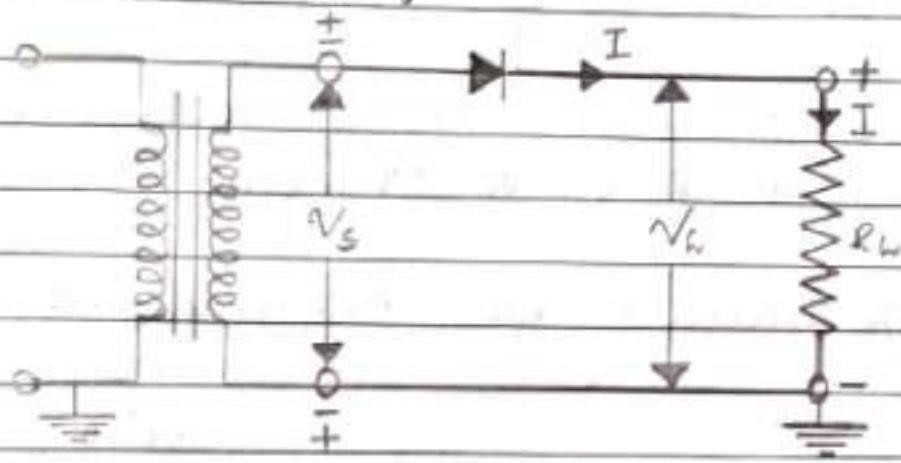

### Half-Wave Rectifier

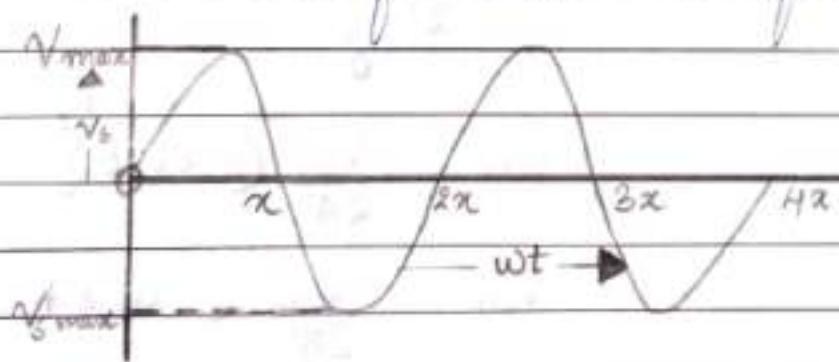

Input Voltage Waveform

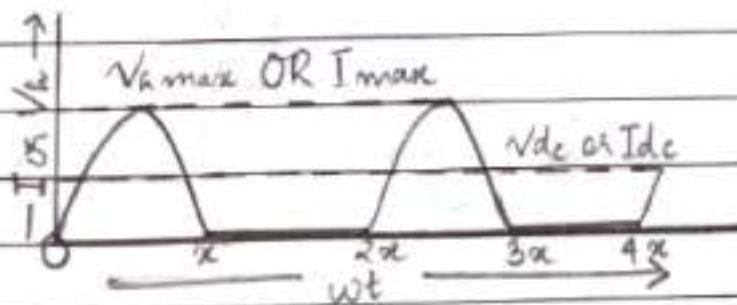

- \* Peak Inverse Voltage
- \* Maximum reverse biased voltage appears across the diode.
- \* Half wave rectifier, PIV =  $V_m$
- \* Average Values of Voltage & Current
- \* Let instantaneous input voltage be  
 $v = V_m \sin \omega t = V_m \sin \theta$
- \* Average value =  $V_{dc} = \text{Area under the wave in one cycle base}$

$$V_{dc} = \frac{1}{2\pi} \int_0^{\pi} V_m \sin \theta d\theta$$

$$V_{dc} = \frac{V_m}{2\pi} (-\cos \theta) \Big|_0^\pi$$

$$V_{dc} = \frac{V_m}{2\pi} (-\cos \pi + \cos 0)$$

$$= \frac{V_m}{2\pi} (1+1)$$

$$= \frac{2V_m}{2\pi}$$

$$V_{dc} = \frac{2V_m}{2\pi} = 0.637 V_m = 0.316 V_m$$

Similarly,

$$I_{dc} = \frac{2I_m}{2\pi} = 0.637 I_m = 0.316 I_m$$

$$I_{m} = \frac{V_m}{R_e}$$

RMS value of voltage & current

$$\text{RMS value} = \sqrt{\frac{1}{2\pi} \int_0^T (I_m \sin \omega t)^2 d(\omega t) + \frac{1}{2\pi} \int_0^T (d.c.)^2 d(\omega t)}$$

$$= \sqrt{I_m^2 \frac{1}{2\pi} \int_0^T \sin^2 \omega t d(\omega t)}$$

$$= \sqrt{I_m^2 \frac{1}{2\pi} \int_0^T 2 \sin^2 \omega t d(\omega t)}$$

$$= \frac{I_m}{2} \sqrt{\frac{1}{\pi} \int_0^T 1 - \cos(2\omega t) d(\omega t)}$$

$$= \frac{I_m}{2} \sqrt{\frac{1}{\pi} \left[ \int_0^T 1 d\omega t - \int_0^T \cos(2\omega t) d\omega t \right]}$$

$$= \frac{I_m}{2} \sqrt{\frac{1}{\pi} [\pi - 0]}$$

$$= \frac{I_m}{2} = 0.5 I_m$$

$$\text{Hence } V_{rms} = V_m/2$$

Ripple factor ( $r$ )

Ratio of rms value of ac component of load current to the average value of load current.

Ripple factor =  $\frac{\text{r.m.s. value of a.c. component}}{\text{value of d.c. component}}$

$$= \frac{I_{ac}}{I_{dc}}$$

By definition, the effective or r.m.s. value of total load current is given by:

$$\text{or } I_{\text{rms}} = \sqrt{I_{\text{dc}}^2 + I_{\text{ac}}^2}$$

$$I_{\text{ac}} = \sqrt{I_{\text{rms}}^2 - I_{\text{dc}}^2}$$

Dividing throughout by  $I_{\text{dc}}$ , we get

$$\frac{I_{\text{ac}}}{I_{\text{dc}}} = \sqrt{\frac{I_{\text{rms}}^2 - I_{\text{dc}}^2}{I_{\text{dc}}^2}}$$

But  $I_{\text{ac}}/I_{\text{dc}}$  is the ripple factor

$$\therefore \text{Ripple factor} = \frac{1}{I_{\text{dc}}} \sqrt{I_{\text{rms}}^2 - I_{\text{dc}}^2}$$

$$= \sqrt{\left(\frac{I_{\text{rms}}}{I_{\text{dc}}}\right)^2 - 1}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}, \quad I_{\text{dc}} = \frac{I_m}{\pi}$$

$$\text{Ripple factor} = \sqrt{\left(\frac{I_m \pi}{I_m \sqrt{2}}\right)^2 - 1}$$

$$= \sqrt{\frac{\pi^2 - 1}{4}}$$

$$= \sqrt{\frac{\pi^2 - 1}{4}} = \frac{\sqrt{\pi^2 - 1}}{2}$$



$$= \frac{\sqrt{9.8596 - 1}}{2} = \frac{2.42}{2} = 1.21$$

## Voltage regulation

Measure of variation of dc output voltage as a function of dc current.

$$\% \text{ regulation} = \frac{(V_{\text{no load}} - V_{\text{full load}}) \times 100}{V_{\text{full load}}}$$


## Full Wave Rectifier

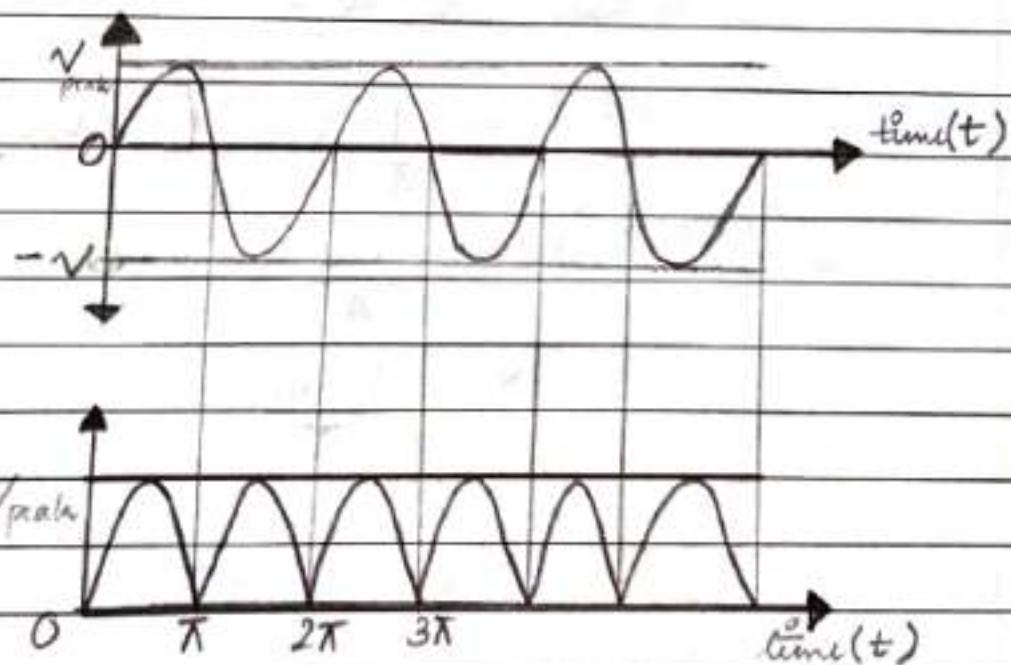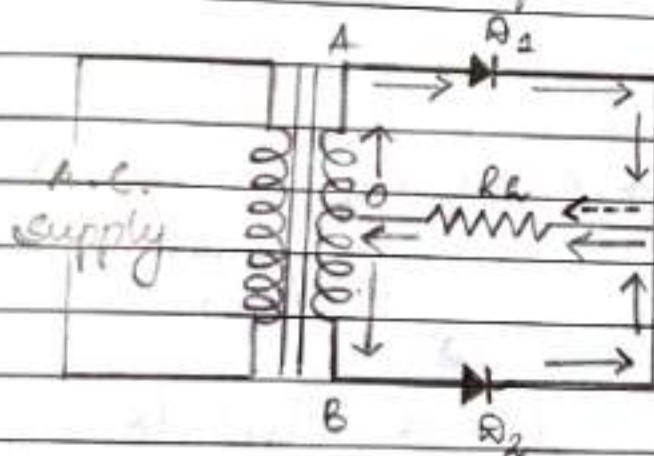

## Average value

$V_{\text{avg}} = \frac{\text{Area under the wave in one cycle}}{\text{base}}$

## \* Peak Anverse Voltage

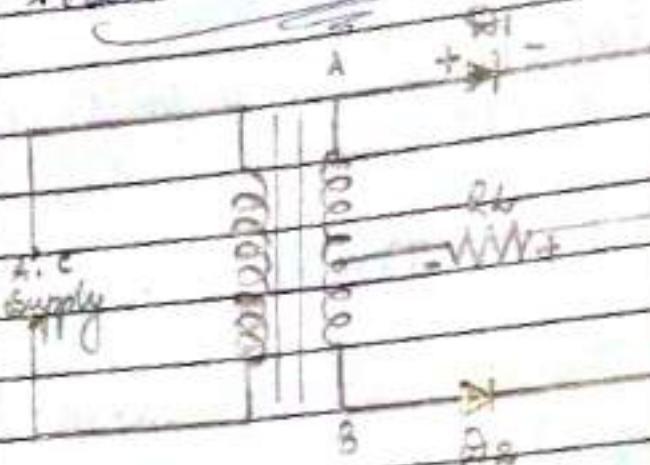

Applying KVL

$$-V_m - V_m - V_{RL} = 0$$

$$N_{RL} = 2V_m$$

$$PIV = 2V_m$$

## \* Average value

$V_{avg} = V_{dc}$  = Area under the wave in one cycle base

$$= \frac{1}{\pi} \int_0^{\pi} N_m \sin \theta \, d\theta \quad \{V = V_m \sin \theta\}$$

$$= \frac{1}{\pi} \times V_m \left[ -\cos \theta \right]_0^{\pi}$$

$$= \frac{V_m}{\pi} \left[ -\cos \pi + \cos 0 \right]$$

$$= \frac{2V_m}{\pi}$$

$$V_{dc} = 0.637 V_m$$

∴ Similarly,

$$I_{dc} = \frac{2 I_m}{\pi}$$

$$= 0.637 I_m$$

RMS value of voltage & current

$$\text{RMS value} = \sqrt{\frac{1}{\pi} \int_{-\pi}^{\pi} (I_m \sin \omega t)^2 dt + \frac{1}{\pi} \int_{-\pi}^{\pi} I_d^2 dt}$$

$$= \sqrt{\frac{I_m^2}{\pi} \int_0^{\pi} \sin^2 \omega t d(\omega t)}$$

$$= I_m \sqrt{\frac{1}{2\pi} \int_0^{\pi} 2 \sin^2 \omega t d(\omega t)}$$

$$= \frac{I_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \int_0^{\pi} (1 - \cos 2\omega t) d(\omega t)}$$

$$= \frac{I_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \int_0^{\pi} 1 d(\omega t) - \int_0^{\pi} \cos(2\omega t) d(\omega t)}$$

$$= \frac{I_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \times [\pi - 0]}$$

$$= \frac{I_m}{\sqrt{2}}$$

Similarly,

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

\* Ripple factor

$$R.F. = \sqrt{\left(\frac{I_{\text{rms}}}{I_{\text{dc}}}\right)^2 - 1}$$



$$= \sqrt{\left(\frac{I_m}{\sqrt{2}} \cdot \frac{\pi}{2}\right)^2 - 1}$$


$$= \sqrt{\left(\frac{\pi}{2}\right)^2 - 1}$$

$$= \sqrt{\frac{\pi^2 - 8}{8}} = \frac{1.363}{2\sqrt{2}}$$



$$= 0.492$$

### \* Bridge Rectifiers

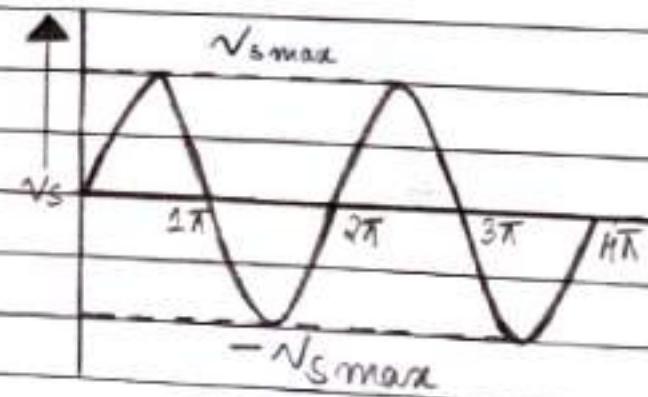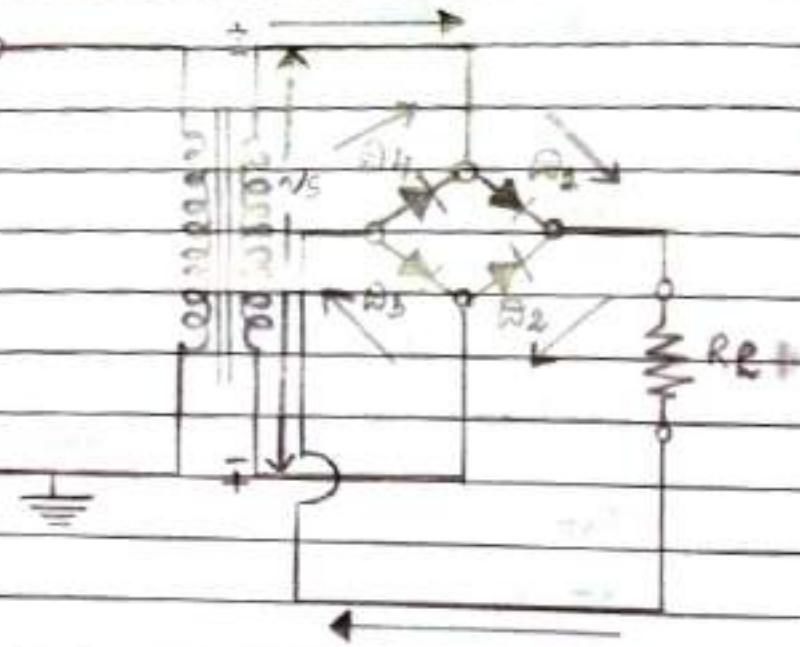

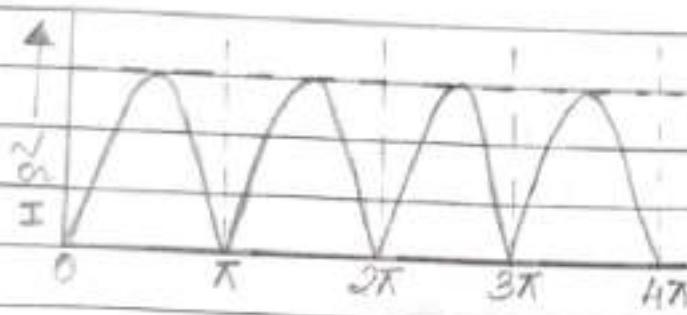

\* Peak Inverse Voltage

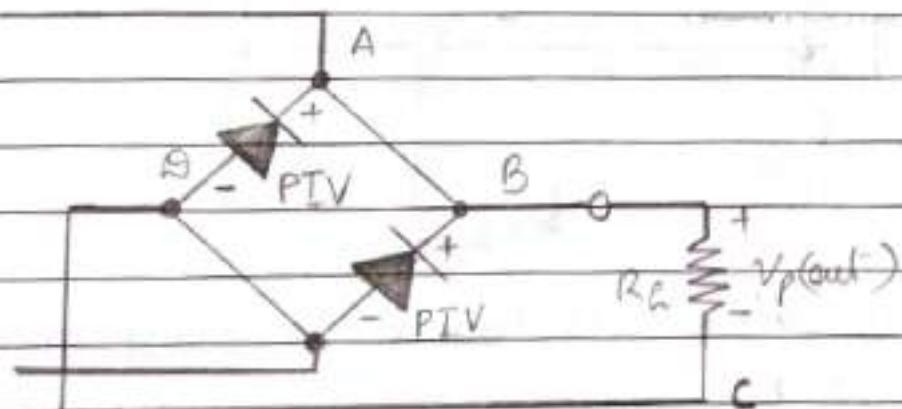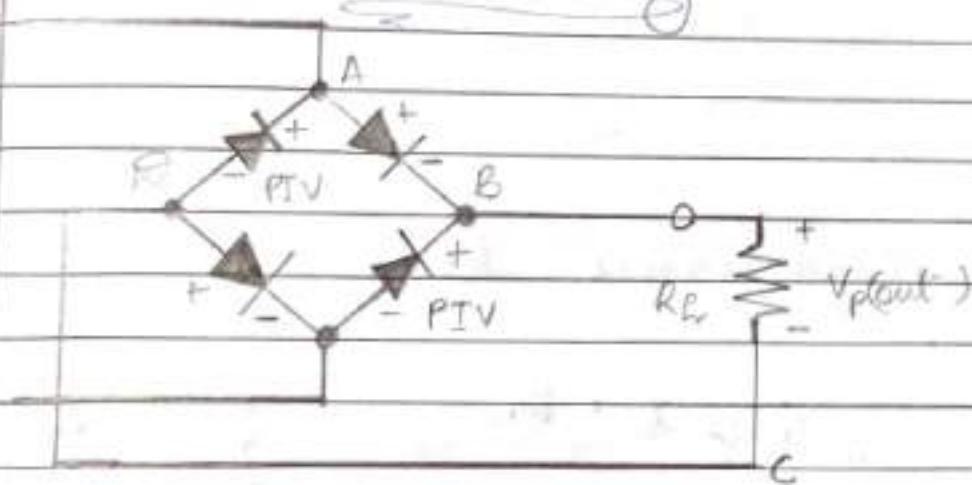

• Applying kvl

$$Nd - Vp = 0$$


$$Nd = Vp$$

$$Vdm = Vpm$$


$$PIV = Vpm$$

Filters


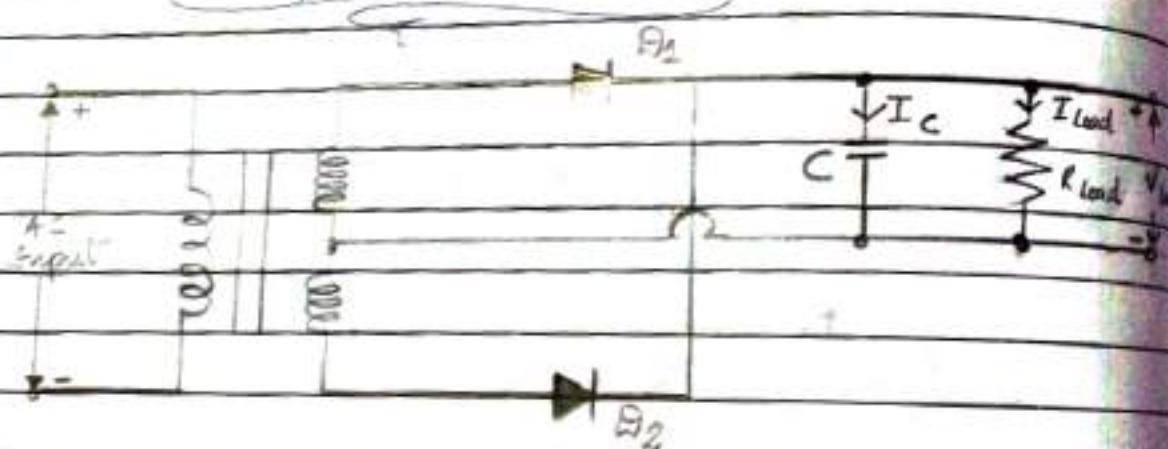
- Presents of AC component is the cause of fluctuation - ripple
- A circuit which removes the ripple from the output without affecting DC value
- Shunt capacitance
- Series inductance
- Shunt Capacitor Filter



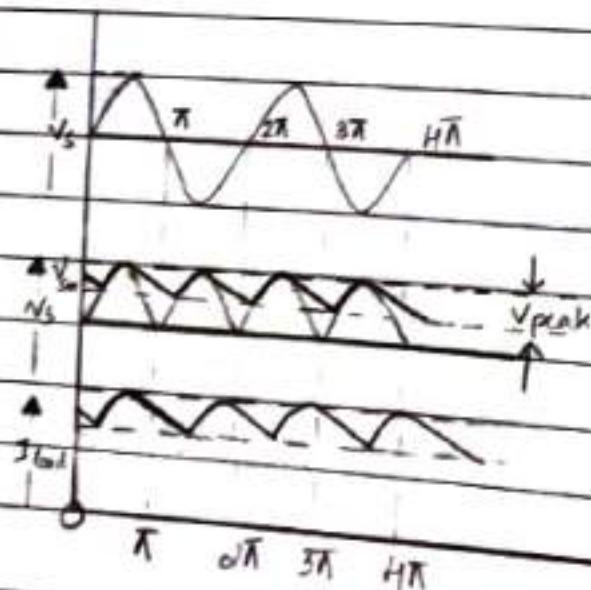
- Shunt capacitor reactance is very small than load resistance.





## \* Series Inductance Filter

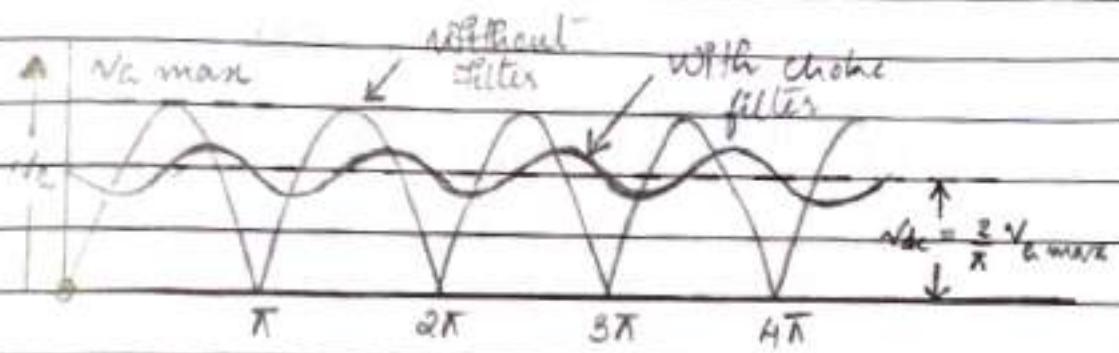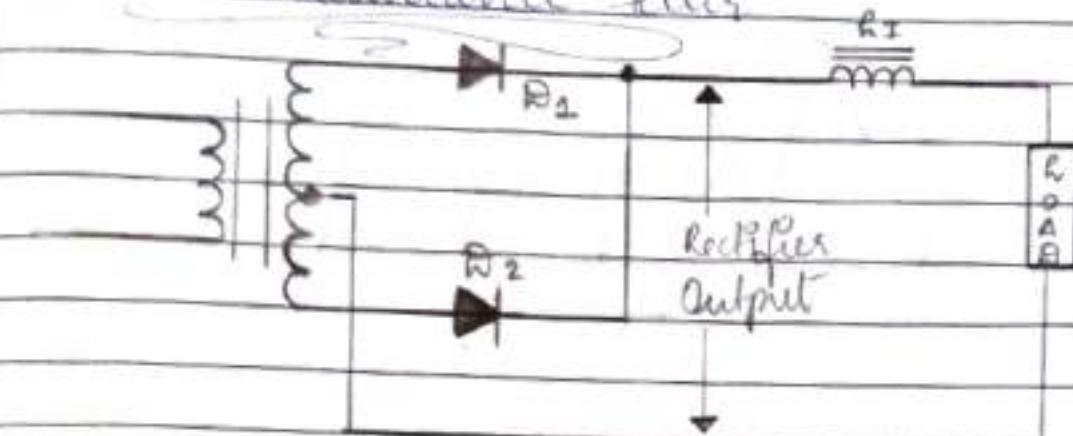


## \* Zener Voltage Regulator

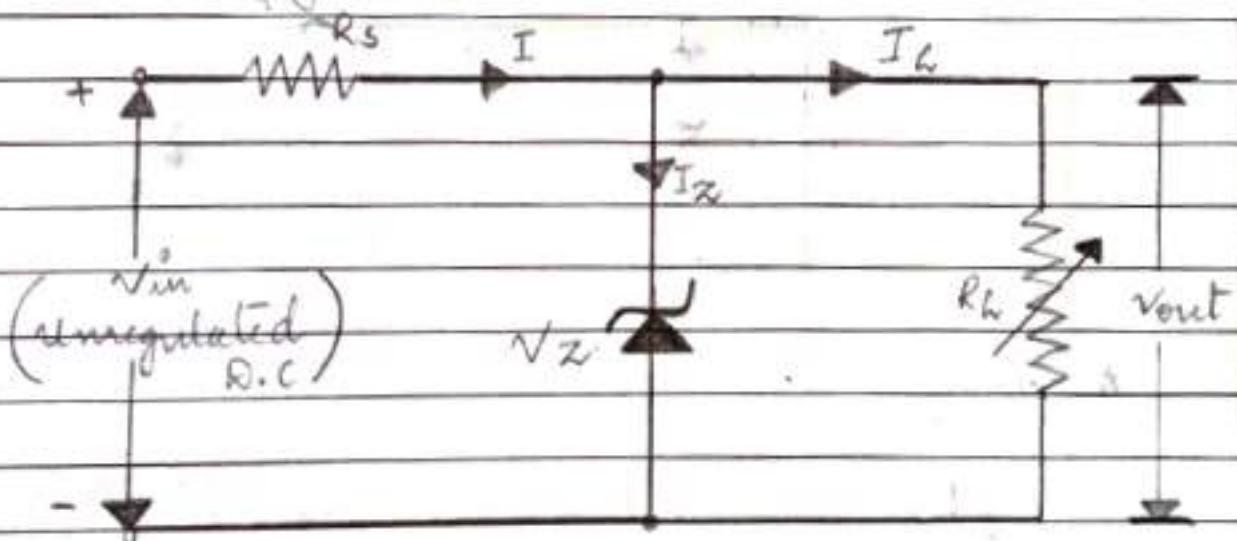


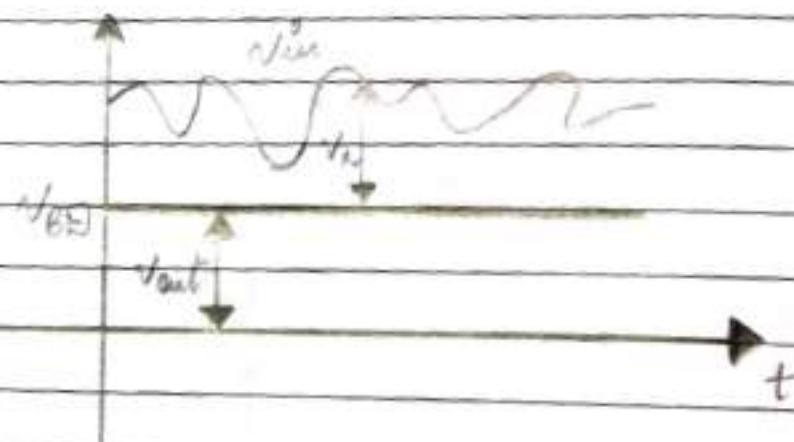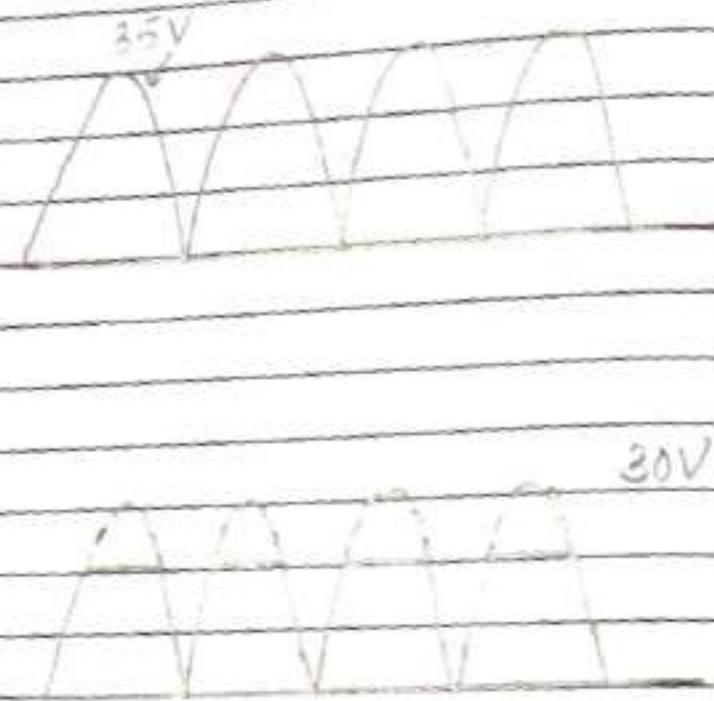
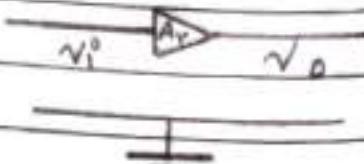
## \* Amplifiers

- Make the voltage or current of input signal large without changing the shape of signal.
- Output signal must be an exact replica of input signal.
- Earth point -



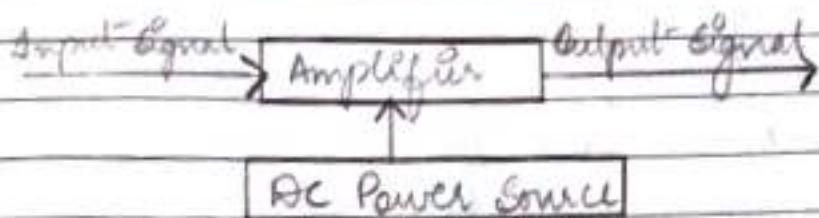

## \* Characteristics of amplifiers

- Input resistance: Effective resistance appears across input terminals.
- Output resistance: Effective resistance appears across output terminals.
- Voltage gain:  $A_v = V_o/V_i$

Voltage gain =  $\frac{\text{Output voltage}}{\text{input voltage}}$

$$A_v = \frac{V_o}{V_i}$$

- Current gain:

$$A_i = \frac{I_o}{I_i}$$

- Power gain:

$$A_p = \frac{P_o}{P_i}$$

- Decibels

- unit of gain

- No of bels =  $\log_{10} \frac{P_o}{P_i}$

- No of Decibels =  $10 \log_{10} \frac{P_o}{P_i}$

- \* Decibel power gain

$$A_p(\text{dB}) = 10 \log_{10} \frac{P_o}{P_i}$$

- \* Decibel voltage gain

$$A_v(\text{dB}) = 20 \log_{10} \frac{V_o}{V_i}$$

- \* Decibel current gain

$$A_i(\text{dB}) = 20 \log_{10} \frac{I_o}{I_i}$$

- \* Ideal amplifier

- The amplifiers gain, ( $A$ ) should remain constant for varying values of input signal.

- Gain is not affected by frequency. Signals of all frequencies will be amplified by exactly the same amount.

- The amplifiers gain must add noise to the output signal. It should remove any noise that already exists in

The input signal.

- The amplifiers gain should not be affected by changes in temperature giving good thermal stability.
- The gain of the amplifier must remain stable over long period of time.

### \* Classification of amplifiers

#### • Based on inputs

##### • Small signal amplifiers

These are designed to amplify very small signal voltage levels of only a few micro-volts (uv) from sensors or audio signals.

##### • Large signal amplifiers (audio power amplifiers or power switching amplifiers).


Large signal amplifiers are designed to amplify large input voltage signals or switch heavy load currents as you would find driving loudspeakers.

#### • Based on biasing condition

• Class A


• Class B

- > Class AB
- > Class C.
- > Class A
- > The most commonly used type of power amplifier configuration is the class A amplifier.
- > The class A amplifier is the simplest form of power amplifier that uses a single switching transistor in the standard common emitter circuit configuration as seen previously to produce an inverted output.
- > The transistor is always biased "ON" so that it conducts during one complete cycle of the input signal waveform producing minimum distortion and maximum amplitude of the output signal.
- > Operates over a linear portion of characteristics - Q point at the centre of linear portion of characteristics.

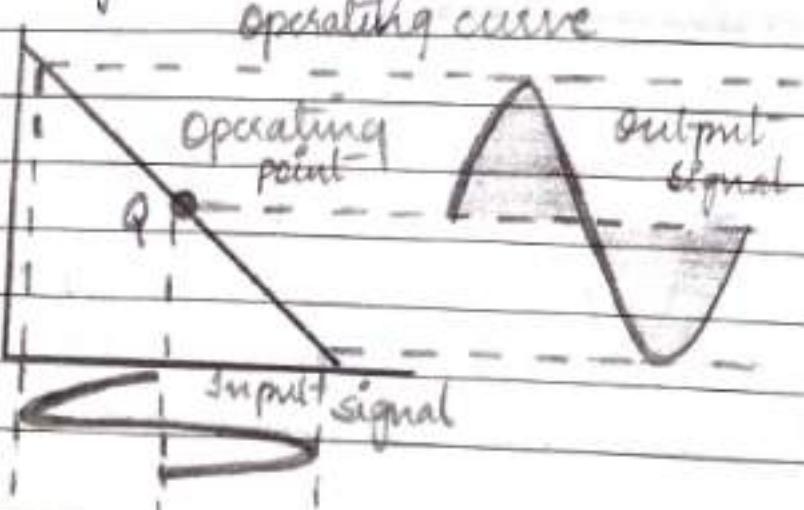
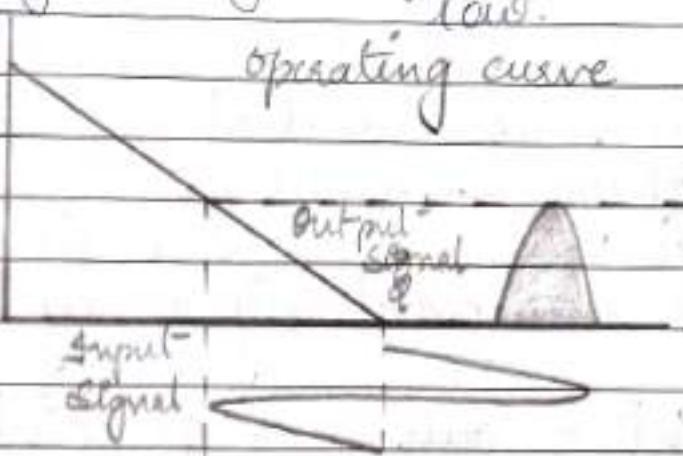
## Class B


- .) A point is in cut-off region.
- .) Output current is only for half cycle.
- .) Efficiency is high - power dissipation is low.



## Class AB

- .) Combination of the "class A" and the "class B" type amplifiers.
- .) The AB classification of amplifier is currently one of the most common used types of audio power amplifier design.
- .) Conduction angle of a class AB amplifier is somewhere between  $180^\circ$  and  $360^\circ$  depending upon the chosen bias point.


Operating curve

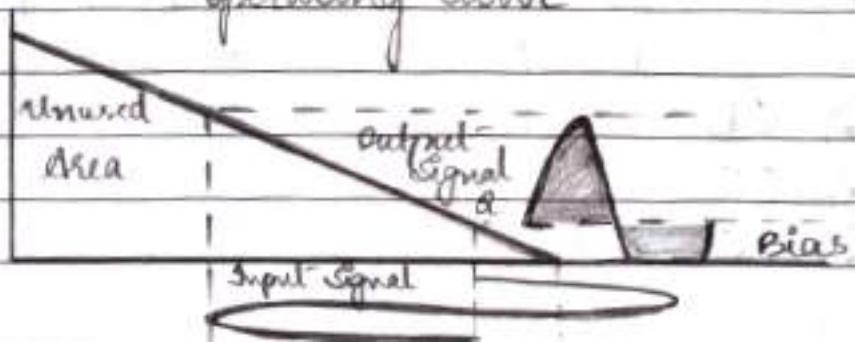

Class C

- Current flow as short pulses.
- The greatest efficiency but the poorest linearity.
- Heavily biased so that the output current is zero for more than one half cycle of an input sinusoidal signal cycle.
- Q point - cut off point
- Conduction angle for the transistor is significantly less than 180 degrees.

Operating curve

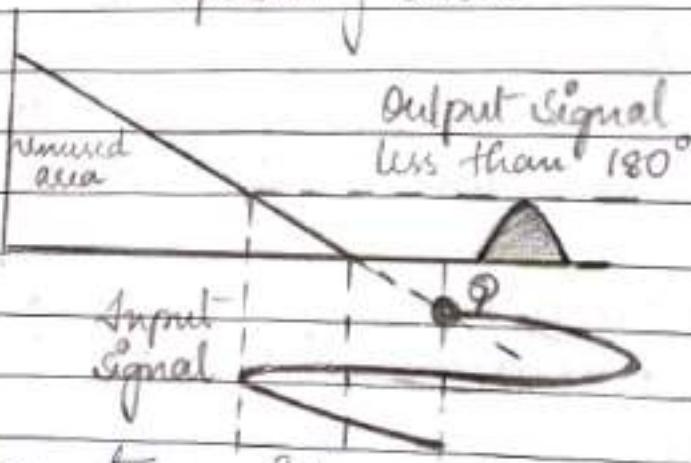

- Based on transistor configuration
  - CB
  - CE
  - CC

## \* Based on coupling

### ..) Resistance - Capacitance coupling



Individual stages of the amplifier are connected together using a resistor - capacitor combination.

### ..) Transformer coupling - impedance matching

### ..) Direct coupling

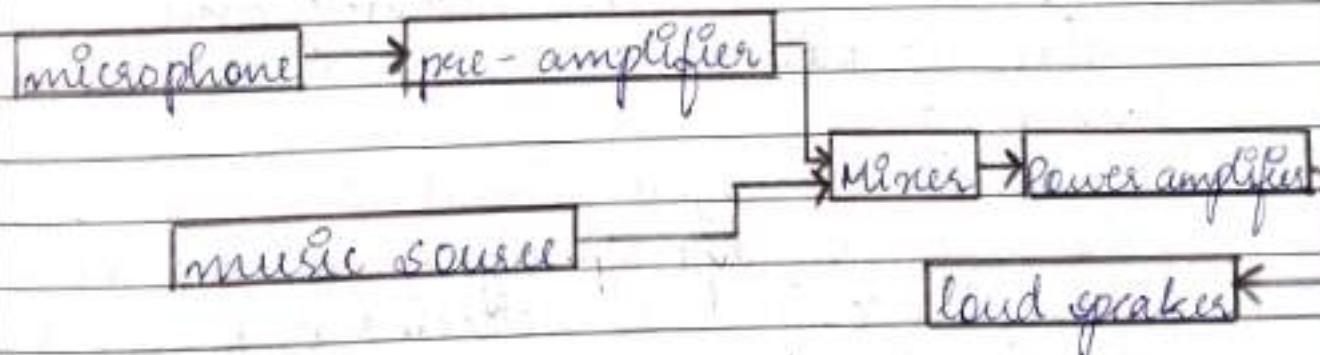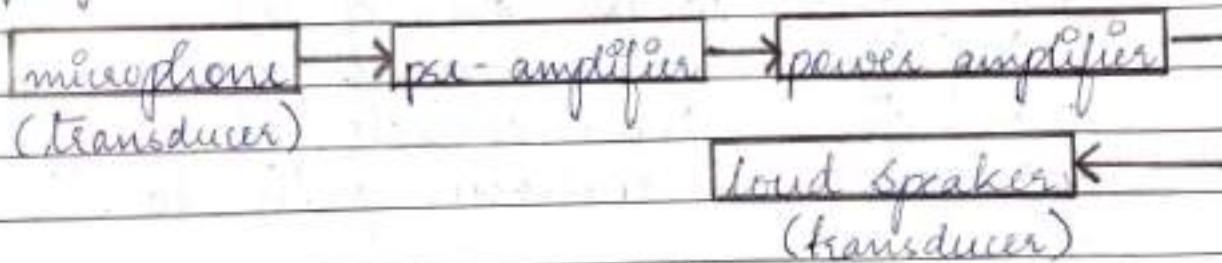
## \* Public Address System

System that amplifies sound, so more people can hear it.


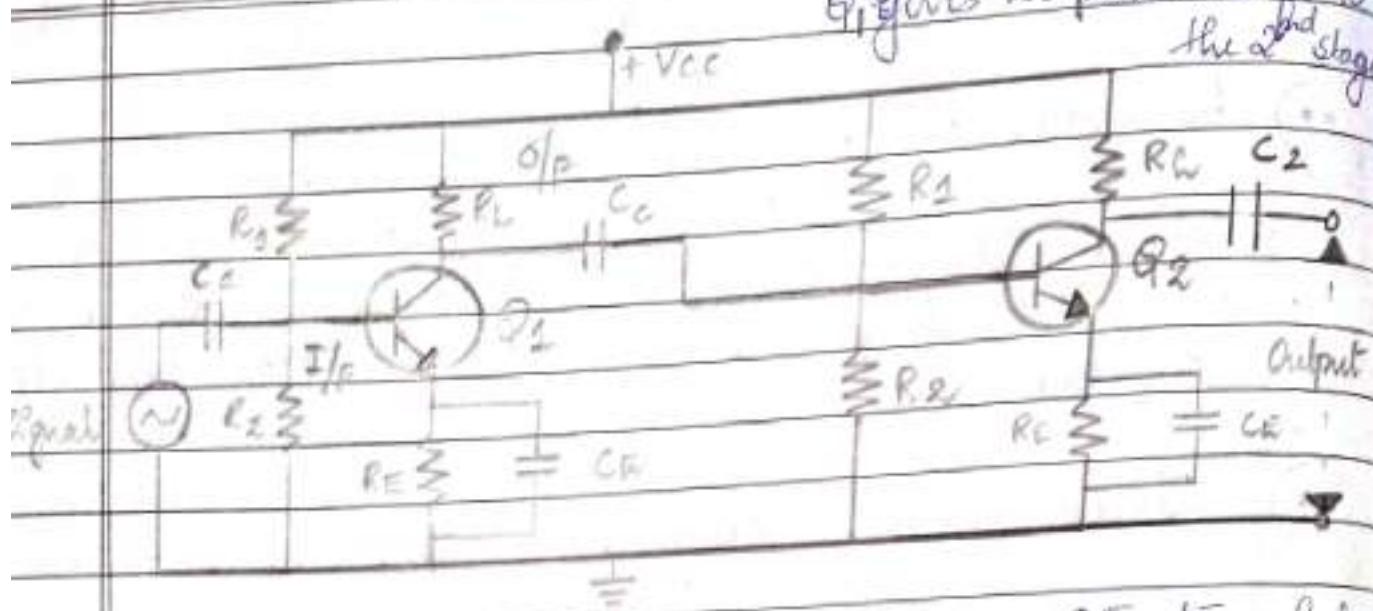
## \* RC Coupled Transistor Amplifiers

$Q_1$  gives 180° phase shift to  
the 2<sup>nd</sup> stage.



Construction of Single stage CE transistor amplifier.

Specification:

CE amplifier: invert amplifier

$C_c$  (coupling capacitor): connects 1<sup>st</sup> and 2<sup>nd</sup> stage

$C_1$ : Input coupling capacitor used to couple input signal to the base of  $Q_1$ .

$C_2$ : Output coupling capacitor used to couple output signal from collector to load.

$C_E$ : gives low resistance path to the emitter signal.

$R_1, R_2, R_f$ : give proper biasing and stabilization to network.


Working:

When an input signal is passed through  $C_1$  it couples the i/p signal to the base  $Q_1$ .

Then the output is collected by  $R_f$  and given to the coupling capacitor ( $C_c$ ). This is then converted to the input signal of the 2<sup>nd</sup> stage.

Hence the output output received at  $R_f$  is passed through the  $C_2$ , which couples the o/p from collector to the load.
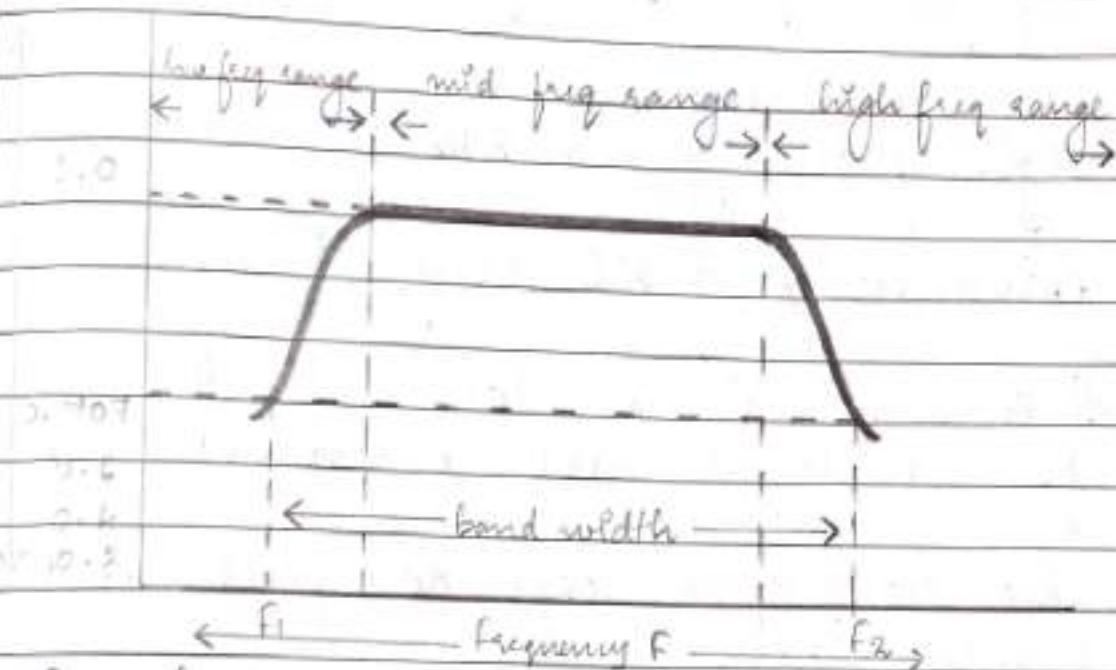
# Frequency Response of R C coupled amplifier



Low frequency region : low gain

- \*  $C_C$  in series ; Impedance is considered

$$X_C = \frac{1}{i\omega C}$$

$$= \frac{1}{2\pi FC}$$

$$\{\omega = 2\pi F\}$$

- \* As  $F$  increases gain increases.

High frequency Region : high gain

- \* Impedance low
- \* Capacitor acts as a short circuit
- \* Output voltage  $\downarrow$ es gain  $\uparrow$ es

- \* Cut off frequency is used to choose the band width.

Lower frequency :  $f_1$

Higher frequency :  $f_2$

\* band width:  $f_2 - f_1$

\* half power point -  $\frac{1}{\sqrt{2}} = 3\text{dB point}$

lower frequency = 50 Hz

higher frequency = 20 KHz

### Advantages of RC coupled amplifier

- \* It uses the resistor and the capacitor which are not expensive so the cost is low.
- \* The circuit is very compact and extremely light.
- \* The frequency response of RC coupled amplifier is excellent.
- \* It offers a constant gain over a wide frequency band.

### Disadvantages of RC coupled amplifier

- \* It has low voltage and power gain.
- \* It is unsuitable for low frequency application.
- \* It has poor impedance matching because its output impedance is several times larger than the device, at its end terminals.
- \* It has the tendency to become noisy with time.
- \* It has narrow bandwidth.

## Transistor Biasing

- DC biasing is a static operation.
- Bias establishes the DC operating point for proper operation of an amplifier.

Mode	EBJ	CBJ	Applications
Cutoff	Reverse	Reverse	Switching applications in digital circuits
Saturation	Forward	Forward	
Active	Forward	Reverse	Amplifier
Reverse active	Reverse	Forward	Performance degradation.

## Voltage Divider Biasing

- The operating point  $Q$  is independent of beta - good stabilization.
- Beta depends on doping concentration.

## Electronic Instrumentation System

### \* Measurement

The process of determining the amount, degree or capacity (by comparison with the accepted standards of the system units being used).

### \* Electronic Instrument

It is a device for determining the value or magnitude of a quantity or variable such as voltage, current or resistance.

## Performance Parameters

### accuracy

It is the degree of closeness with which the instrument reading approaches the true value of the quantity to be measured.

### Precision

It is a measure of consistency or reproducibility of measurement. This means when a quantity is measured repeatedly, the instrument should give the same value i.e., successive readings do not differ.

### Resolution

The smallest change in a measurement variable to which an instrument will respond.

### Sensitivity

It is the ratio of change in the output (response) of the instrument to a change of input or measured variable.


### Expected Value

It is the desired value of measured quantity or the most probable value that is expected to obtain.


### Errors

It is the deviation of the true value from the desired value.

## Electronic Instrumentation System

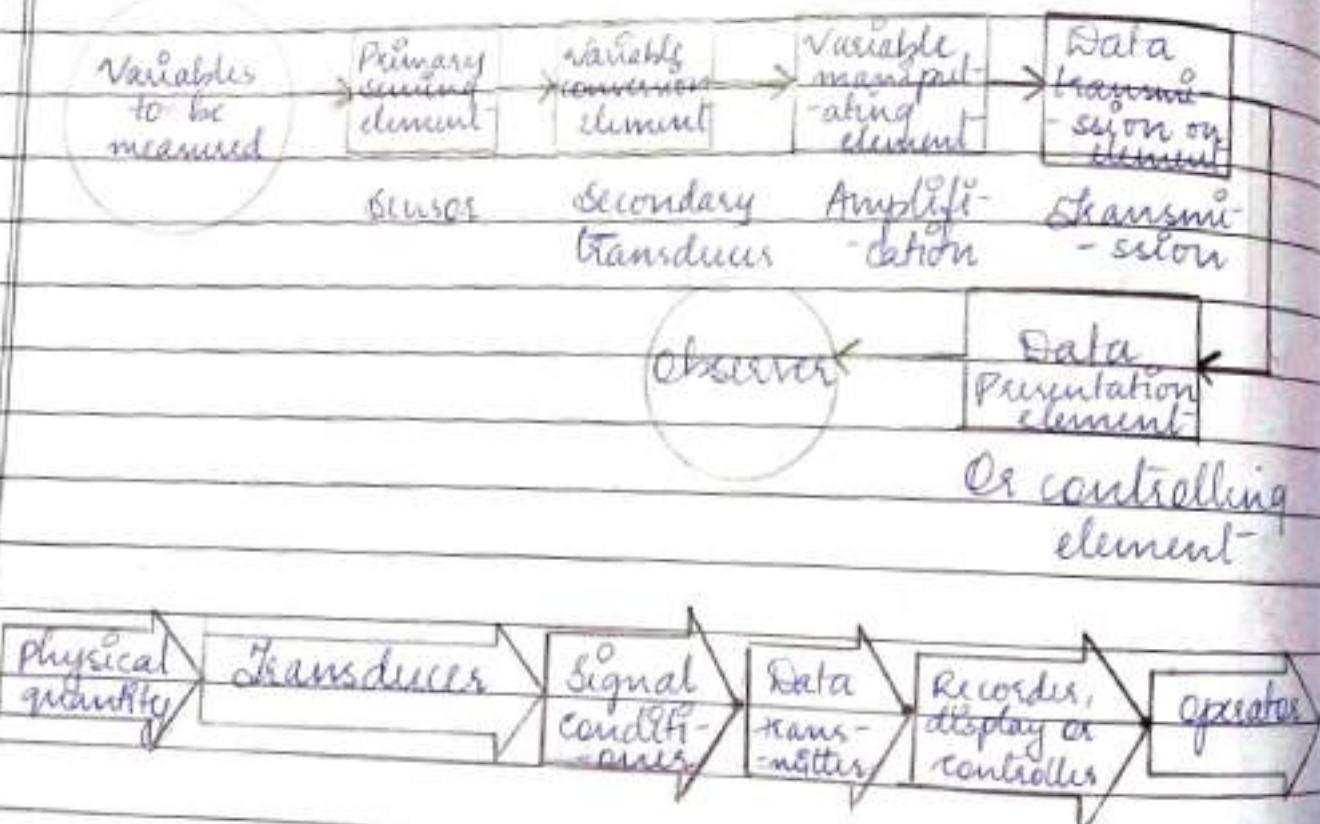

# Electronic communication

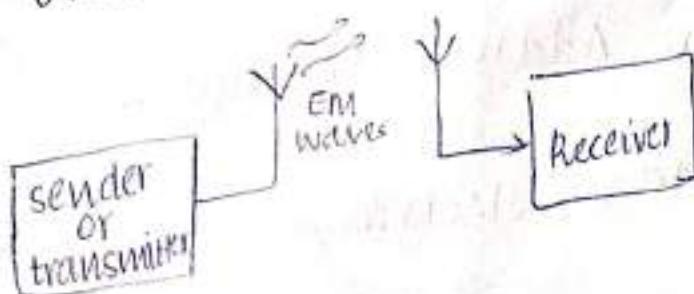

## Modulation

changing amplitude, frequency, phase of carrier wave

- Base band signal will be enclosed in carrier messages are usually in low freq.  
(20 Hz - 3 KHz)

## Need for modulation

$$E = h\omega$$

when  $\omega$  is  $\downarrow$ ,  $E \downarrow$   
modulat<sup>n</sup> is done to high freq.

(i) Radiation is efficient only at high freq.

(ii) radiation can only be done with antennae  
if no modulation, then  $\ell$  will be  $\uparrow$

low freq. is modulated with high freq.

thus freq., amplitude, phase of carrier wave is  
changed to <sup>that of</sup> modulating wave

freq. change  $\rightarrow$  frequency modulation

amplitude change  $\rightarrow$  amplitude modulation

so if  $f \uparrow$ ,  $\lambda = \frac{c}{f}$  so  $\lambda$  will be less

$\lambda/4$  : quarter wave antennas

antennae height should be less

all freq. <sup>were</sup> lie in same band. so frequency gets mixed  
when different freq. is used for modulation, they will  
never mix so lie in diff. freq.  
so receiver can tune in station they wish

$$v_c = V_c \sin(\omega_c t + \phi)$$

$V_c$ : peak value (amplitude)

$\phi_c$ : phase

$v_c$ : voltage of carrier

## Analog modulation / continuous wave modulation

2 types

Amplitude modulation (AM) UDSP GECT

Angle modulation

(a) Frequency modulation (FM)




(b) Phase modulation (PM)

Digital modulation

- (i) ASK: amplitude shift keying
- (ii) FSK: Frequency shift keying
- (iii) PSK: phase shift keying
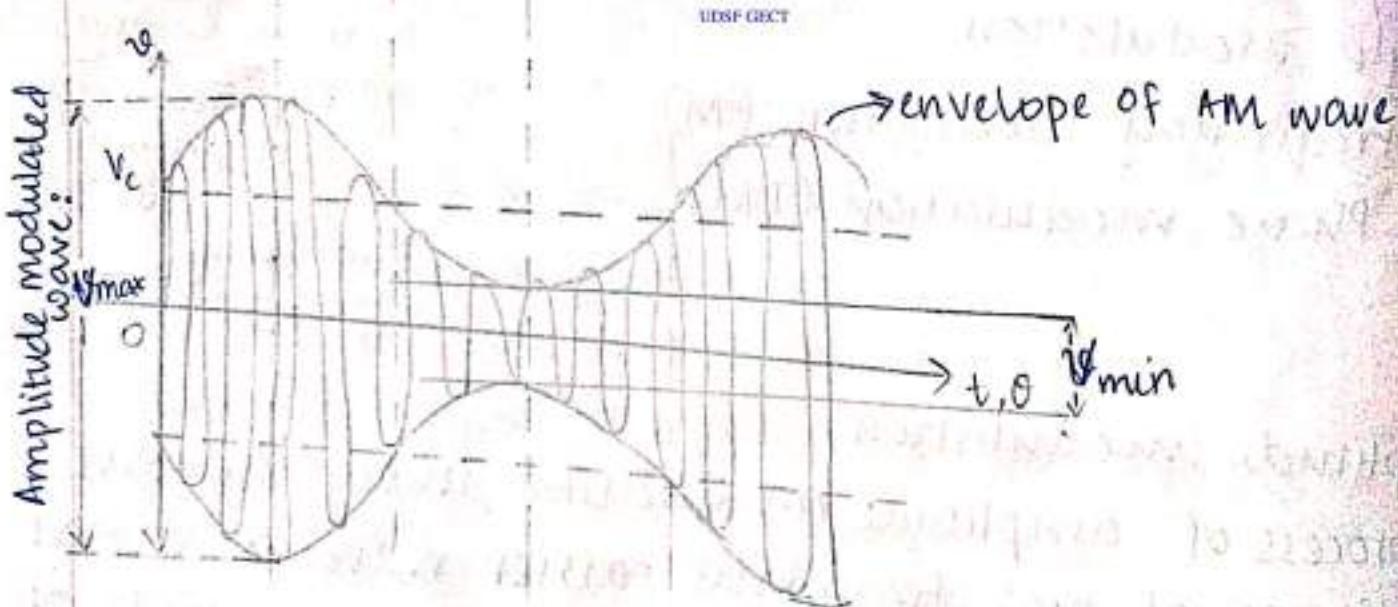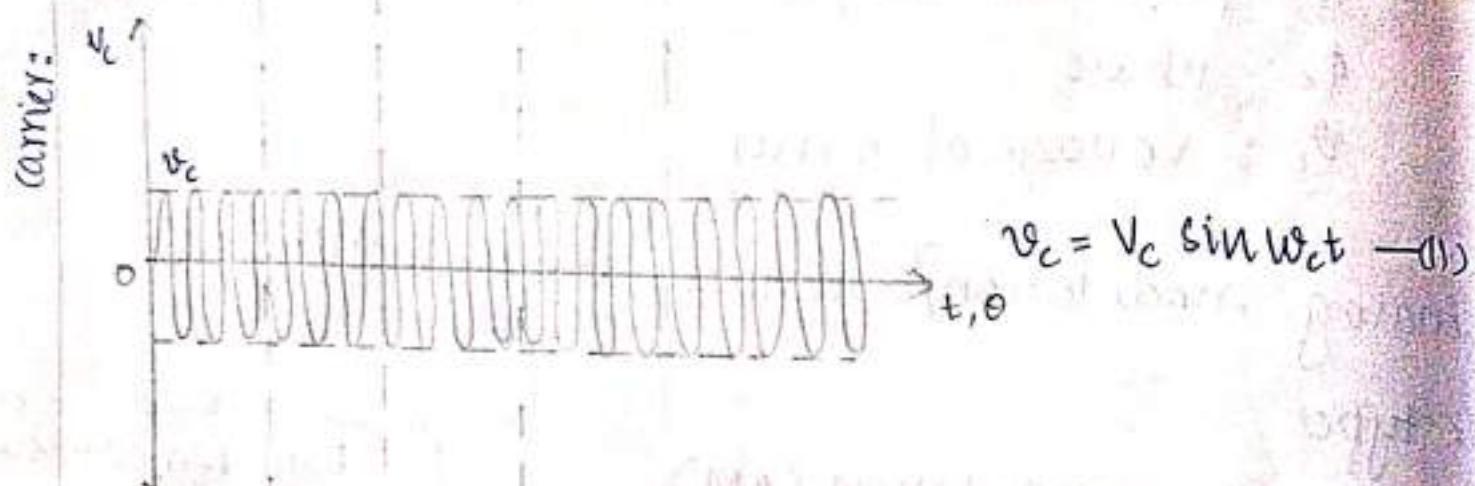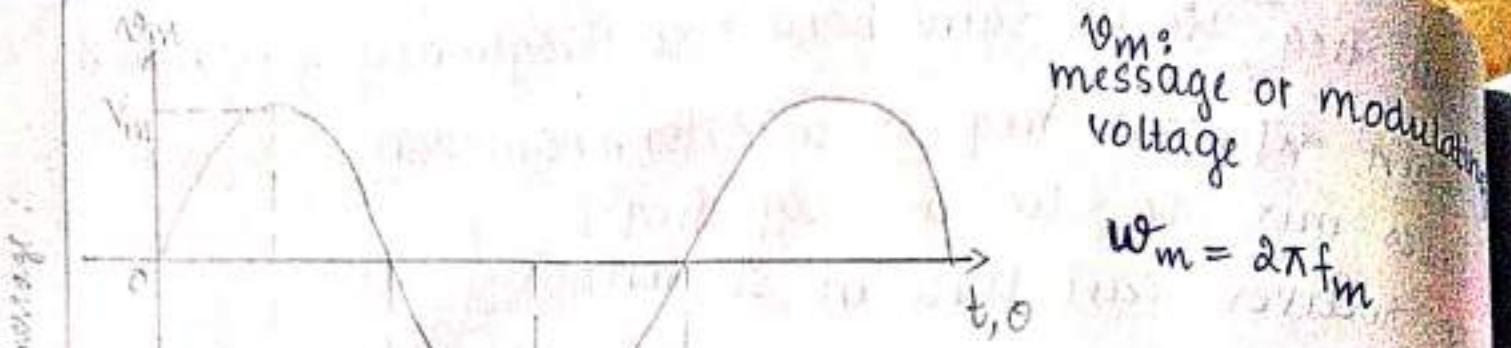
## Amplitude modulation

In process of amplitude modulation, instantaneous amplitude of high frequency carrier wave is varied in proportion to the instantaneous amplitude of the message voltage value, keeping frequency and phase of carrier wave a constant.



- only instrument which displays electrical waveform is CRO
- AM index : also called depth of A.M.  
 $m = \frac{V_m}{V_c}$

$$m = \frac{V_{\max} - V_{\min}}{V_{\max} + V_{\min}} \quad 0 \leq m \leq 1$$

when message wave voltage is 0,  $m=0$

when  $m=1$ ,  $V_m=V_c$

when  $m > 1$ , no signal is received by receiver

this ~~case~~ is called over modulation distortion

implies when message amplitude overlaps carrier amplitude

$$v_m = V_m \sin \omega_m t \quad \text{---(1)}$$

$$v_c = V_c \sin \omega_c t \quad \text{---(2)}$$

AM wave is,

$$v = A \sin \omega_c t$$

$$\text{where } A = V_c + v_m$$

$$A = V_c + V_m \sin \omega_m t$$

$$v = (V_c + V_m \sin \omega_m t) \sin \omega_c t$$

$$v = V_c \underbrace{\sin \omega_c t}_{\text{full carrier}} + V_m \sin \omega_m t \sin \omega_c t$$

$$= \frac{1}{2} [\sin(A-B) - \sin(A+B)]$$

$$v = V_c \sin \omega_c t + \frac{V_m}{2} \cos(\omega_c - \omega_m)t - \frac{V_m}{2} \cos(\omega_c + \omega_m)t$$


$$m = \frac{V_m}{V_c} \quad \therefore V_m = m V_c$$

$$v = V_c \sin \omega_c t + \frac{m V_c}{2} \cos(\omega_c - \omega_m)t - \frac{m V_c}{2} \cos(\omega_c + \omega_m)t$$

Full carrier

LSB

USB

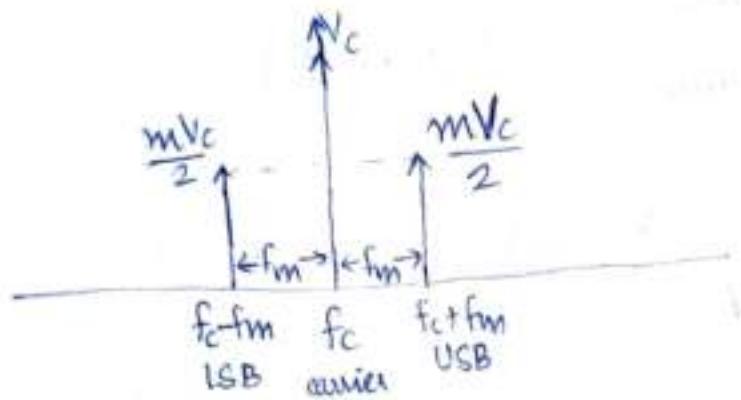


LSB : lower side band

USB : upper side band

$$\text{Bandwidth of AM} = 2 \times f_m$$

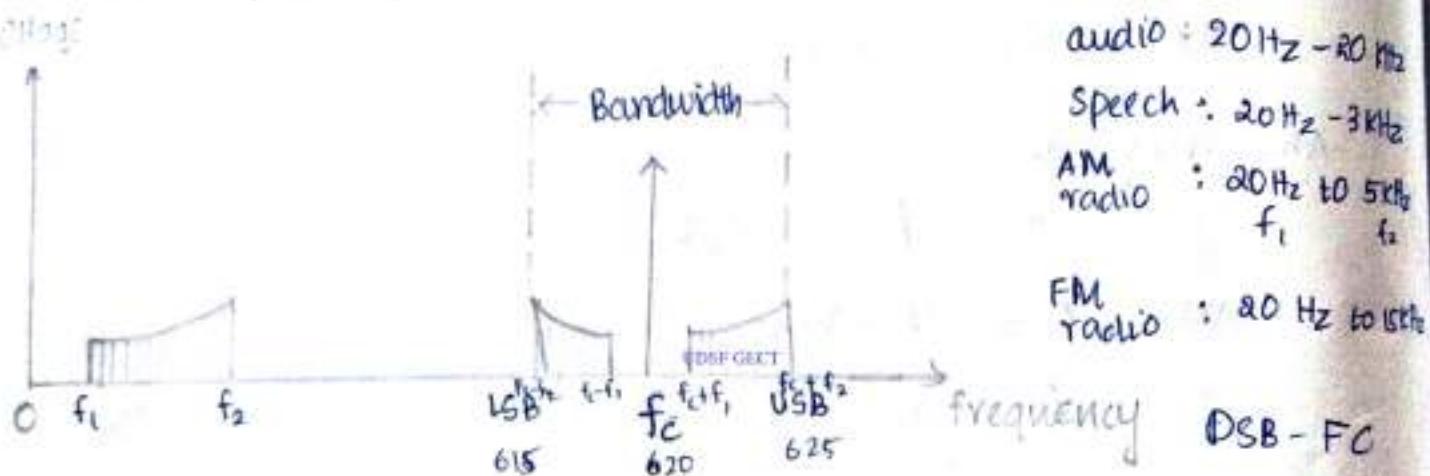Frequency spectrum of AM when modulated by a base band of  $f_1$  to  $f_2$



audio : 20 Hz - 20 kHz

Speech : 20 Hz - 3 kHz

AM radio : 20 Hz to 5 kHz  
 $f_1$        $f_2$

FM radio : 20 Hz to 15 kHz  
 DSB - FC

$$\text{Bandwidth} = 2 \times f_2 = 2 \times \text{highest modulating frequency}$$

- For different voltages  $v_1, v_2, v_3, \dots, v_n$ , modulation index will be  $m_1, m_2, m_3, \dots, m_n$

Then,  $m_{\text{effective}} = \sqrt{m_1^2 + m_2^2 + m_3^2 + \dots + m_n^2}$

Power in A.M.

$$v = V \sin \omega t$$

$$P = \frac{\left(\frac{V}{\sqrt{2}}\right)^2}{R}$$

$$v = V_c \sin \omega_c t + \frac{mV_c}{2} \cos(\omega_c - \omega_m)t - \frac{mV_c}{2} \cos(\omega_c + \omega_m)t$$

carrier LSBUSB

$$P_t = P_c + P_{LSB} + P_{USB}$$

$$P_c = \frac{\left(\frac{V_c}{\sqrt{2}}\right)^2}{R} = \frac{V_c^2}{2R}$$

$$P_{LSB} = \frac{\left(\frac{mV_c}{2\sqrt{2}}\right)^2}{R} = \frac{m^2 V_c^2}{8R}$$

$$P_{USB} = \frac{\left(\frac{mV_c}{2\sqrt{2}}\right)^2}{R} = \frac{m^2 V_c^2}{8R}$$

∴ Total power,

$$P_t = \frac{V_c^2}{2R} + \frac{m^2 V_c^2}{8R} + \frac{m^2 V_c^2}{8R}$$

$$= \frac{V_c^2}{2R} + \frac{m^2 V_c^2}{4R}$$

$$P_t = \frac{V_c^2}{2R} \left[ 1 + \frac{m^2}{2} \right]$$

$$P_t = P_c \left[ 1 + \frac{m^2}{2} \right]$$

- \* calculate total power transmitted from an ordinary AM radio transmitter whose carrier frequency is 800kHz at 100W power and modulated to a depth of
- (i) 0%.
  - (ii) 10%.
  - (iii) 50%.
  - (iv) 100%.

$$\rightarrow f_c = 800 \text{ kHz}$$

$$P_c = 100 \text{ W}$$

$$(i) P_{t1} = P_c \left(1 + \frac{m^2}{2}\right) \quad \text{given } m=0$$

$$P_{t1} = 100 (1+0)$$

$$P_{t1} = \underline{\underline{100 \text{ W}}}$$

$$(ii) P_{t2} = P_c \left(1 + \frac{m^2}{2}\right) \quad m = \frac{10}{100}$$

$$= 100 \times \left(1 + \frac{1}{200}\right)$$

$$= 100 \times \frac{201}{200} = \underline{\underline{100.5 \text{ W}}}$$

$$(iii) P_{t3} = P_c \left(1 + \frac{m^2}{2}\right) \quad m = \frac{50}{100} = \frac{1}{2}$$

$$= 100 \left(1 + \frac{1}{8}\right)$$

$$= 100 \times \frac{9}{8} = \underline{\underline{112.5 \text{ W}}}$$

$$(iv) P_{t4} = P_c \left(1 + \frac{m^2}{2}\right) \quad m = \frac{100}{100} = 1$$

$$= 100 \left(1 + \frac{1}{2}\right)$$

$$= 100 \times \frac{3}{2} = \underline{\underline{150 \text{ W}}}$$

balanced modulation

carrier wave will be zero

therefore, only LSB and USB will be there

PSB - SC



here same signal is send twice.

so a filter is used.

filter will select either LSB or USB.

this is called Single side band (SSB).

SSB has only one band.

when bandwidth is less, we can save power and we can include more channels.

disadvantages of SSB

UNIF GECT

- High cost
- some information may be cut


HAM : Hobby amateurs

In T.V., U.S.B + a part of L.S.B is used for signal.


This is called <sup>vestige</sup> vestigial side band

Frequency modulation (FM)

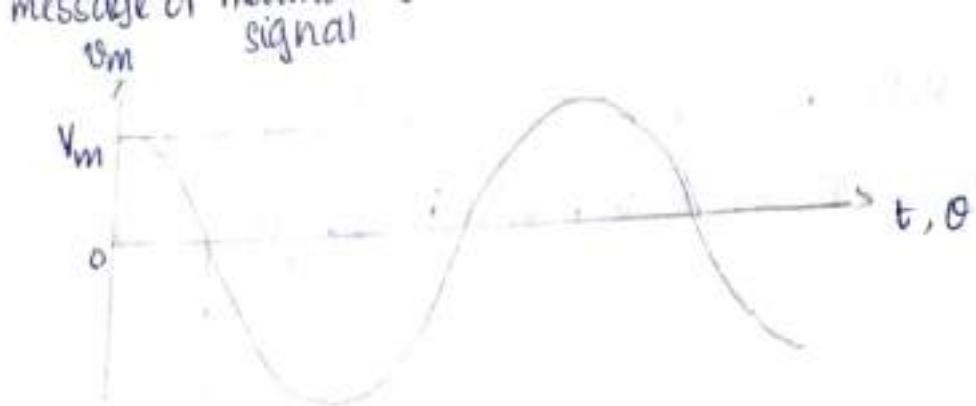
- In the process of frequency modulation, the instantaneous frequency of a high frequency carrier is varied in proportion to the instantaneous amplitude of the message/modulating voltage, keeping the amplitude and phase of the carrier a constant.



v<sub>c</sub> carrier

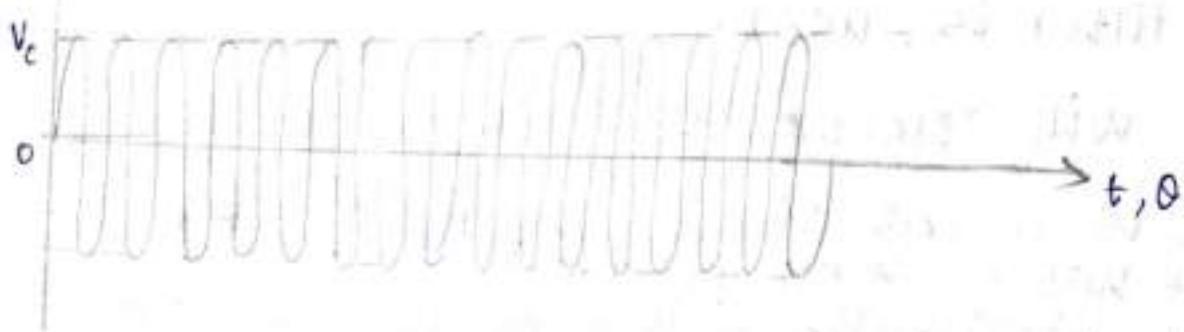

FM wave

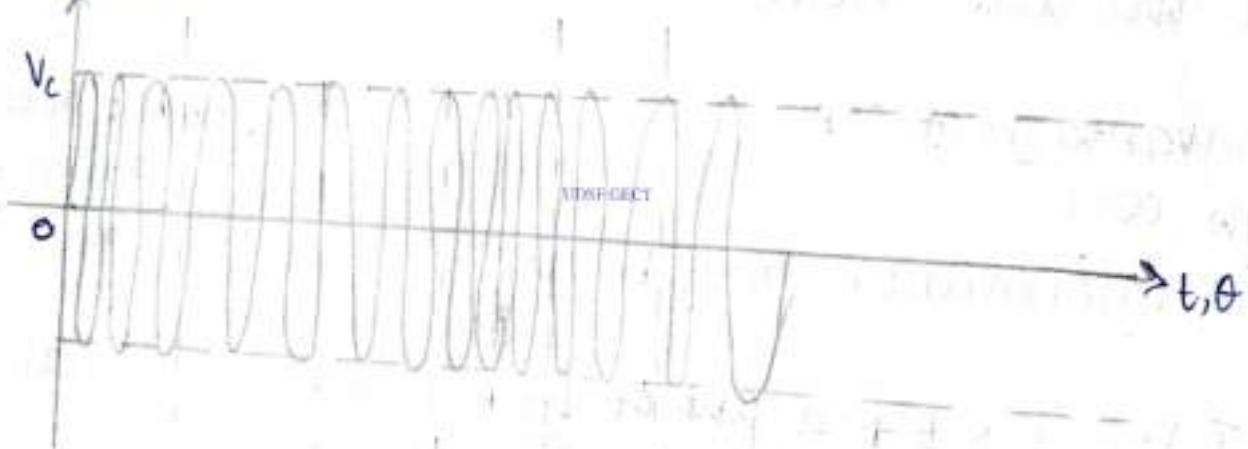

- Message signal is  $v_m = V_m \cos \omega_{mt}$  —(i)
- Carrier signal is  $v_c = V_c \cos \omega_c t$  —(ii)
- Frequency deviation  $f = f_c + k \theta_m f_c$ ; frequency deviation
- FM wave is  $v = V_c \sin \theta$  —(iii)
- $\theta = \int \omega \cdot dt$
- $\omega = \omega_c + k \theta_c V_m \cos \omega_{mt}$

$$\theta = \int [\omega_c + k\omega_c V_m \cos \omega_m t] dt$$

Maximum frequency deviation,

$$\delta = kV_m f_c$$

$$\theta = \omega_c t + \frac{k\omega_c V_m \sin \omega_m t}{\omega_m}$$

$$\theta = \omega_c t + \frac{(k f_c V_m)}{f_m} \sin \omega_m t$$

$$\theta = \omega_c t + \frac{\delta}{f_m} \sin \omega_m t \quad \rightarrow \quad m_f = \frac{\delta}{f_m}$$

$\frac{\delta}{f_m}$  = modulation index of FM wave

FM index =  $\frac{\text{Max. freq. deviation}}{\text{modulating frequency}}$

compare m of AM and FM

UDNFRCT

A.M.	FM
$m = \frac{V_m}{V_c}$	$m_f = \frac{\delta}{f_m} = \frac{k f_c V_m}{f_m}$
$0 \leq m \leq 1$	$m_f > 0$
	<ul style="list-style-type: none"> <li>If <math>m_f &lt; 1</math>, it is called narrow band F.M. → used for point to point communication</li> <li>If <math>m_f &gt; 1</math>, wide band F.M. → used for music, radio broadcasting</li> </ul>

∴ (A)  $\Rightarrow$

$$\theta = \omega_c t + m_f \sin \omega_m t$$

FM wave is.

$$v = V_c \sin(\omega_c t + m_f \sin \omega_m t)$$

Bessel function : sine of sine wave

- \* A wave is defined as  $v = 10 \sin(10^8 t + 8 \sin 300 t)$   
Estimate amplitude, frequency of carrier,  $m_f$ , max freq. deviation
- and modulating frequency

→

$$v = 10 \sin(10^8 t + 8 \sin 300 t) \text{ V}$$

$$v = V_c \sin(\omega_c t + m_f \sin \omega_m t)$$

$$V_c = 10 \text{ V}$$

$$\omega_c = 10^8 \quad \Rightarrow f_c = \frac{10^8}{2\pi} = 1.59 \times 10^7 \text{ Hz} = \underline{\underline{15.9 \text{ MHz}}}$$

$$m_f = 8$$

$$\frac{\omega_c}{f_m} = m_f$$

$$\omega_m = 300$$

$$\delta = m_f \times f_m$$

$$f_m = \frac{300}{2\pi} = \underline{\underline{47.7 \text{ Hz}}}$$

$$\frac{\delta}{f_m} = m_f$$

$$\delta = 47.7 \times 8 = 381.6 \text{ Hz}$$


$$v = v_c \sin(\omega_c t + m_f \sin \omega_m t)$$

Bessel function.

$$\begin{aligned} &= I_0 \sin \omega_c t \pm I_1 \sin (\omega_c \pm \omega_m) t \\ &\quad \pm I_2 \sin (\omega_c \pm 2\omega_m) t \\ &\quad \pm I_3 \sin (\omega_c \pm 3\omega_m) t \end{aligned}$$

$I_0, I_1, \dots \Rightarrow$  Jacobians.

varies for all  $m_f, f_m$

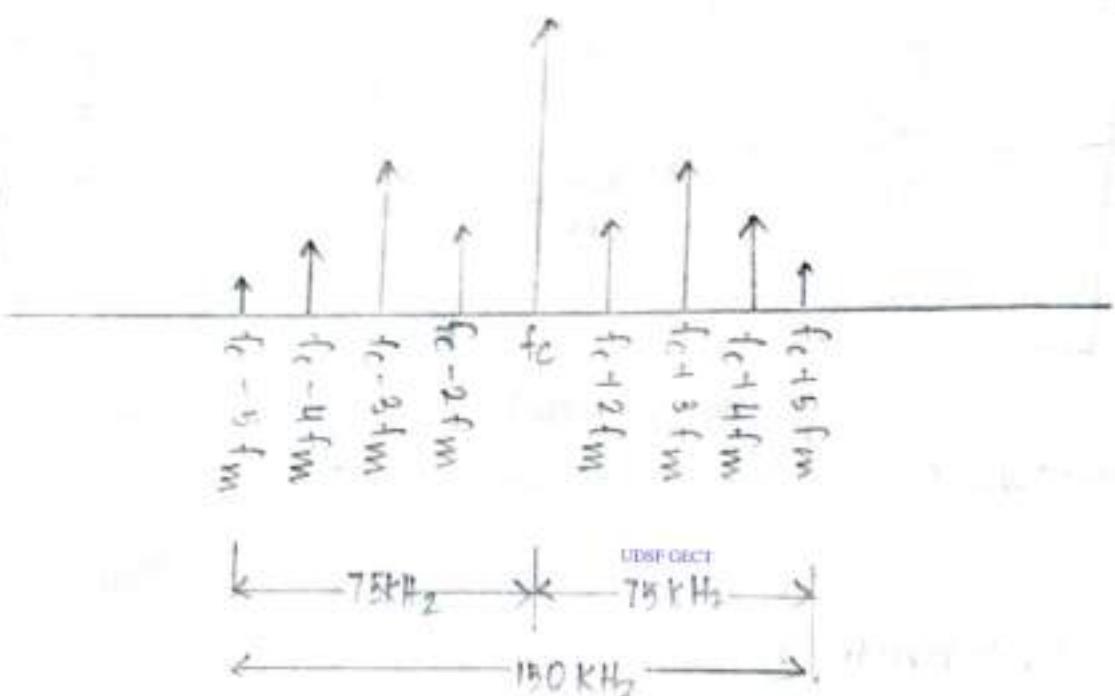

### COMPARISON OF FM AND AM

- FM  $\Rightarrow$  highly quality because FM is highly noise immune  
amplitude is constant  $\rightarrow$  noise is clipped  
carrier wave is of high frequency range, thus, noise do not get in it  
all power is useful  $\rightarrow$  signals can be taken out
- Frequency re-usage  $\rightarrow$  FM freq. range 30 MHz - 300 MHz  
frequency do not go out of frequencies won't interfere  
loss (line of sight), thus


; same frequencies can be FM (reused) without  
 interference  
 fm. fidelity  $\uparrow \rightarrow$  quality high



space wave propagation

- limitation:
  - high bandwidth
  - amplifying circuits are complicated
  - stations  $\downarrow$
  - space wave propagation: Range of distance from antenna to station
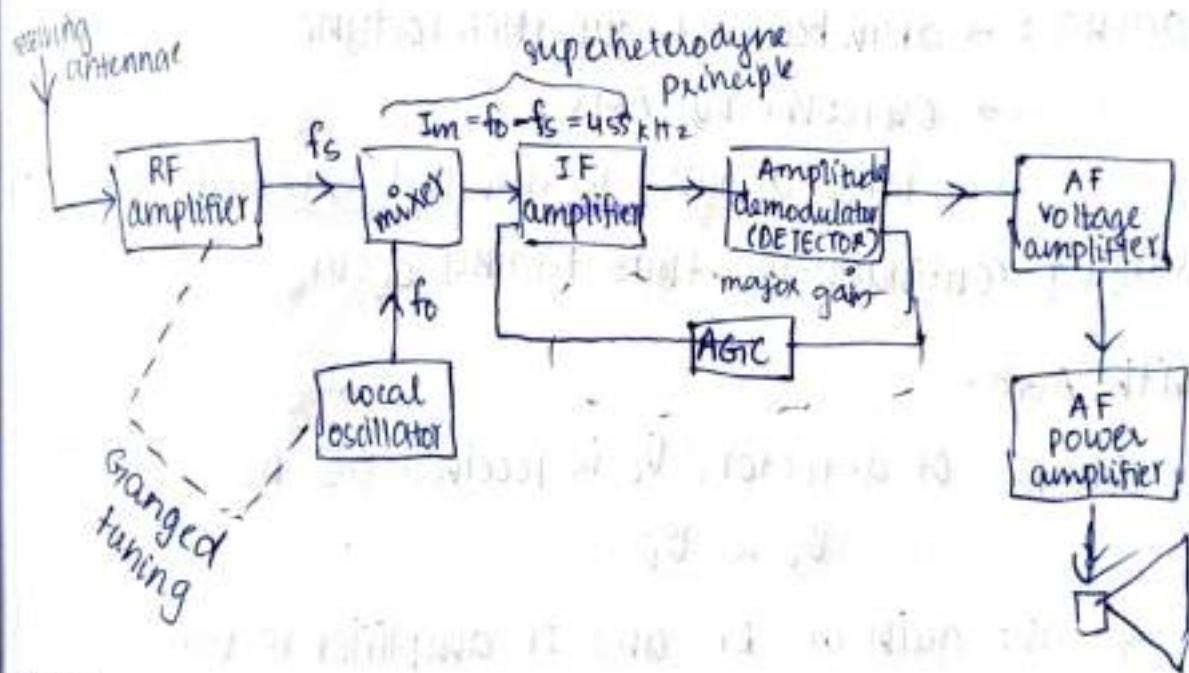
### super heterodyne AM radio receiver (mix)



receiving antennae: based on principle of faraday's law of EMI


AM  $\rightarrow$  medium wave 620 - 1650 kHz  
 short wave 1650 kHz - 3 MHz { Band

10 kHz : bandwidth


FM  $\rightarrow$  88 MHz - 108 MHz; band

150 kHz: bandwidth

- Mixer (local oscillator): IM:  $f_o - f_s \Rightarrow$  intermediate frequency  
 $f_o - f_s$  is constant  
AM  $\rightarrow f_o - f_s = 455 \text{ kHz}$   
FM  $\rightarrow f_o - f_s = 10.7 \text{ MHz}$
- Audio frequency voltage amplifier  $\rightarrow$  gain in this stage changes (voltage)  
 $v_o = Av_i \Rightarrow$  if fluctuates, then output also varies  
 $\therefore$  as  $v_i \uparrow$ , A should be decreased  $\Rightarrow v_o$  become steady  
This reducing A is called Automatic gain control [AGC]
- Fading:  $\rightarrow$  drawback of superheterodyne  
 $\rightarrow$  overcome by AGC  
 $\rightarrow$  as large distance is travelled, intensities are varying continuously, thus fading occur
- With AGC:  
At output of detector,  $v_o$  is received as DC level  
 $v_o \propto v_i$   
 $\therefore$  the gain of RF and IF amplifier is varied  
 $\rightarrow$  as  $v_i \uparrow$ , A is  $\downarrow$   
 $\rightarrow$  automatic gain control
- AGC produce control signal that control gain of IF amplifier (also RF amplifier)  
thus controlling  $v_o$  of detector/discriminator

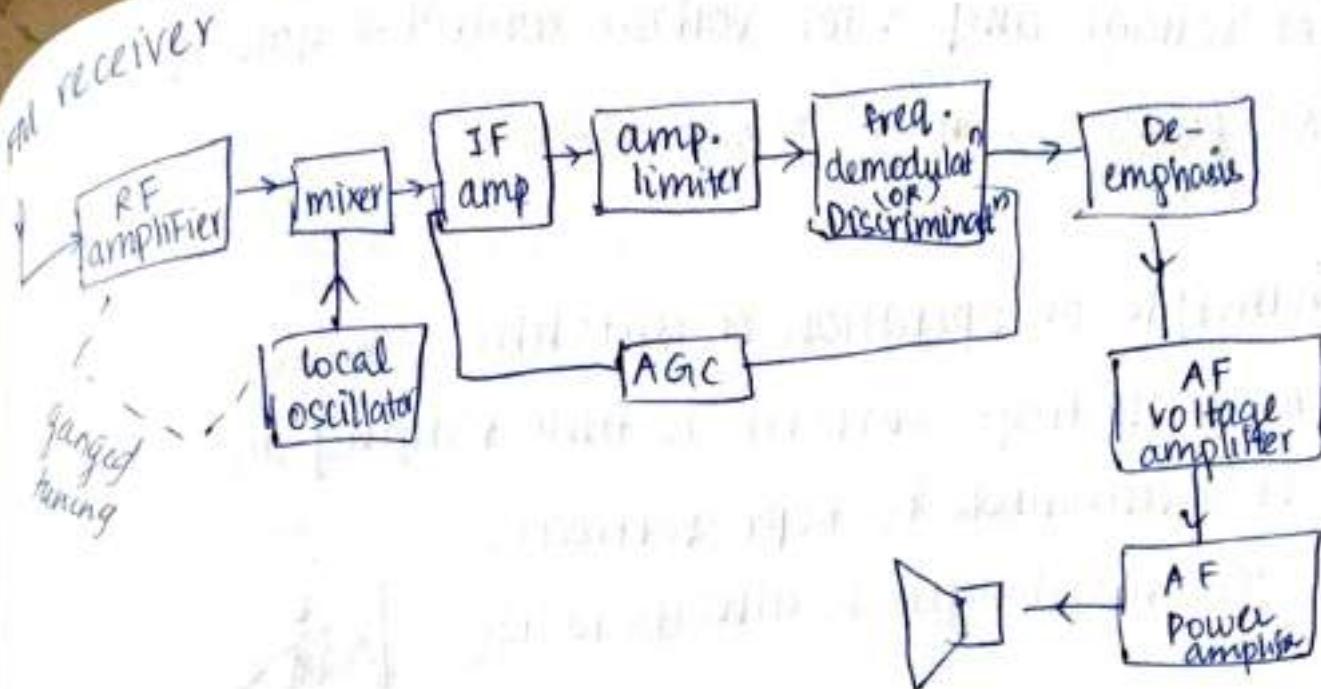

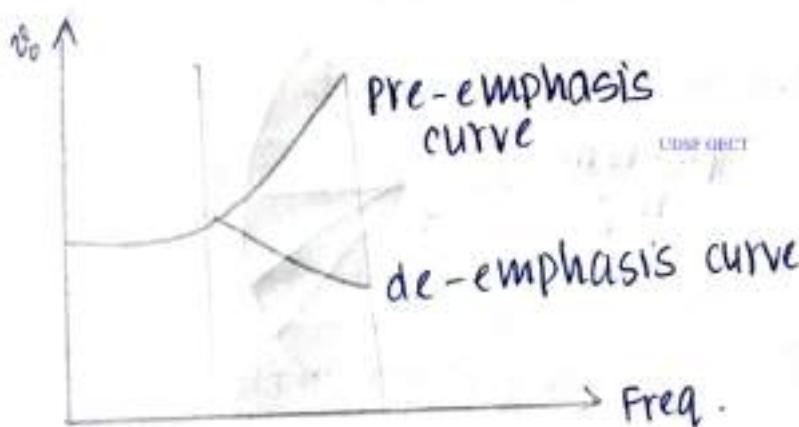De-emphasis  $\rightarrow$  smaller gain at receiver  
 $\Rightarrow$  actual signal can be taken




- ANTENNAE : EMF induced  $\rightarrow$  current produced
- RF amp. : selects freq. (150 kHz) and amplify if other frequency gets it, it is tuned
- Mixer : Sender frequencies are mixed with a loca<sup>l</sup> freq.  $s \quad f_0 - f_s = 1M = 10.7 \text{ MHz}$
- Amplitude limiter : extra noises are taken out with high amplitude
- Discriminator : audio freq. are separated, gain is made strong


- AF voltage amp. : for voltage control  $\rightarrow$  gain changes
- AF power : high power signal
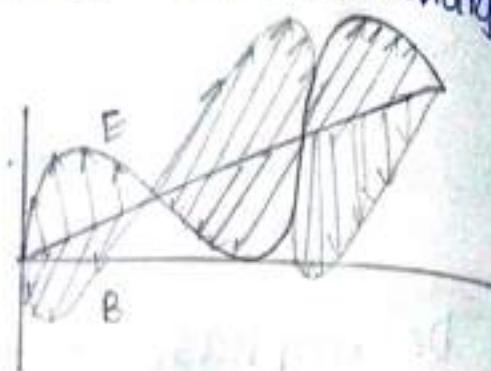
## Principle of operation of antenna

- At high freq., current is time varying accelerated charge  
It's antennae is kept vertical.  
 $\lambda/4$  wavelength is always radiated



## Parabolic reflector (dish)

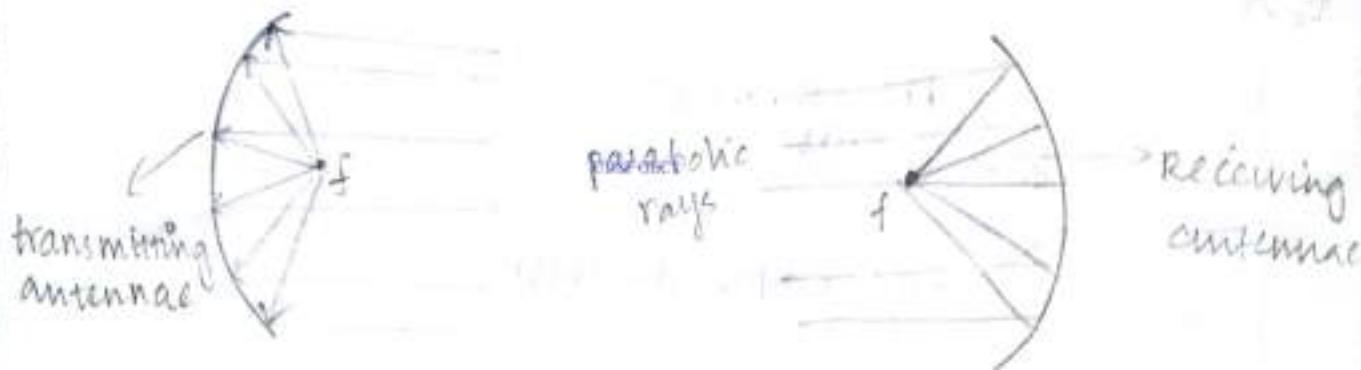


## Applications

- microwave tower
- telephone
- television
- DTH (direct to home)
- wireless LAN and WAN
- radio telescope (weather forecast)
- RADAR
- To navigate
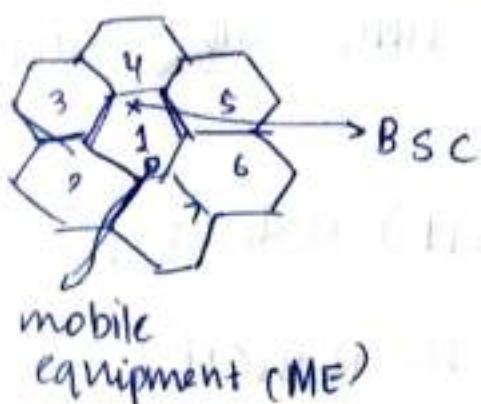
# GSM and mobile communication

GSM : Global system for mobile communication

There is a base station controller (BSC) at each centre



MSC : mobile switching centre

SIM : subscriber identify module : it is unique for each mobile

code from ME  $\rightarrow$  BSC  $\rightarrow$  threshold limit

freq. band is fixed for each service provider

VLR : visiting location register

HLR : Home location register

All BSC's are connected to an MSC

Authentic centre(AC)

GSM

M.E.

BSC

MSC

satellite

OPTIC  
fibre  
(OFC)

PSTN

transmitter receiver

MSC

carrier frequency is allotted by BSC

PN code : Pseudo random Noise

CDMA : code deficient multiple access

Here, many signals can be passed <sup>in same medium</sup> without any interference  
→ Time division multiple access (TDMA)

→ Frequency " " " (FDMA) ; many freq can be passed at same time. Since diff. freq., they do not mix

- Subscriber ~~TRUNK~~ dialling (STD) code :
- PSTN : Public switched telephone network

### Advantages

- only communication when persons are in motion
- SMS, MMS, videos, pictures can be shared
- Teleconference, videoconference ..

### Drawbacks

- emit radiations which is hazardous

### Range of Frequencies

Telegraphy	marine navigation	AM radio broadcast	FM radio broadcast			microwave radar satellite
VLF	LF	MF	HF	VHF	UHF	SHF, EHF

10kHz 30kHz 300kHz 3000kHz (or) 3MHz 900MHz 3GHz 30GHz

VLF : very low frequency

- Morse code

LF : low frequency

MF : medium frequency

HF : high frequency (for long distance communication)

above 1 MHz : sky wave propagation

VHF : very high frequency

FM radio broadcast : 88 MHz - 108 MHz

UHF : ultra high frequency

SHF : super high frequency

EHF : extra high frequency

Bands and ranges  
L band  $\rightarrow$  1 GHz - 2 GHz (satellite, mobile, radar, microwave)

S band  $\rightarrow$  2 to 4 GHz

C band  $\rightarrow$  4 to 8 GHz

X band  $\rightarrow$  8 to 12 GHz

Ku band  $\rightarrow$  12 to 18 GHz

K band  $\rightarrow$  18 to 27 GHz

Ku : under K

Ka band  $\rightarrow$  27 to 40 GHz

Ka : above K

Block diagram of an electronic instrumentation system

Transducer: convert energy of one form to electrical energy

